

The Open University of Sri Lanka  
Faculty of Engineering Technology  
Department of Mechanical Engineering



Study Programme	: Bachelor of Technology Honours in Engineering
Name of the Examination	: Final Examination
<b>Course Code and Title</b>	<b>: DMX3572/MEX3272 – Applied electronics</b>
Academic Year	: 2017/18
Date	: 25 <sup>th</sup> January 2019
Time	: 0930-1230hrs
Duration	: <b>3 hours</b>

**General Instructions**

1. Read all instructions carefully before answering the questions.
2. This question paper consists of **Eight (8)** questions in **Seven (7)** pages.
3. Answer any **Five (5)** questions only. All questions carry equal marks.
4. Answer for each question should commence from a new page.
6. This is a Closed Book Test (CBT).
7. Answers should be in clear hand writing.
8. Do not use Red colour pen.

**Q1.**

- (a) Write the equations needed to solve for the node voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure Q1-a. [06 marks]

 


Figure Q1-a.

- (b) Determine Thévenin and Norton equivalent circuits of the circuit illustrated in Figure Q1-b. [06 marks]

 


Figure Q1-b

- (c) A Wheatstone bridge is illustrated in Figure Q1-d.  $R_1 = 12\text{ k}$ ,  $R_3 = 240\text{ k}$ , and  $R_2 = 2\text{ k}$ . If  $i_g = 0$ , determine  $R_x$ . [04 marks]

 


Figure Q1-d

- (d) It is model a certain battery as a voltage source in series with a resistance. The open circuit voltage of the battery is 12V. When a  $150\Omega$  resistor is placed across the terminals of the battery, the voltage drops to 9V. Find the Thevenin resistance (internal resistance) of the battery. [04 marks]

## Q2.

- (a) A double diode clipper circuit shown in Figure Q2-a can be used to limit the peaks of both half cycles of the 10V AC input signal. Sketch the output signal (You should indicate the magnitudes of the signal). [06 marks]

 


Figure Q2-a

- (b) A Zener circuit shown in figure Q2-b. Given that  $v_i = 10\sin\omega t$ ,  $V_{Z1} = V_{Z2} = 5V$ , explain the operation of the circuit and sketch the  $V_o$  waveform. Assume that both zener diodes have a voltage drop of  $0.7V$  when forward bias. [06 marks]

 


Figure Q2-b

- (c) Explain the functions of following diode types. [04 marks]
- Varactor diodes
  - Catch diode (freewheeling diode)
- (d) Briefly explain any two applications of FET. [04 marks]

### Q3.

- (a) Briefly explain the function of any four types of filter circuits. [04 marks]
- (b) A simple Amplifier system is shown in figure Q3 –b.

 


Figure Q3-b

- Suggest a suitable filter circuit for the Filter-1 and justify your suggestion. [03 marks]
- Now, you want to add another filter to the woofer. Suggest a most suitable filter for the woofer and give reasons. [03 marks]

- (c) Suppose that  $R = 5000 \, \Omega$  and  $C = 1 \, \mu\text{F}$  in the circuit of figure Q3-c. The capacitor charged to  $V_i$  prior to  $t=0$ . Find the time at which the voltage across the capacitor reaches 36.8% of its initial value ( $V_i$ ). [05 marks]

 


Figure Q3-c

- (d) Find  $v_x$  and  $i_x$  for the circuit shown in figure Q3-d for  $t \gg 0$  (After the switch has been closed for a long time, we expect the transient response to have decayed to zero. Then the circuit is operating in dc steady-state conditions). [05 marks]

 


Figure Q3-d

## Q4.

- (a) A dc bias circuit is shown in Figure Q4 has  $R_B = 200 \, \text{k}$ ,  $R_C = 1 \, \text{k}$ , and  $V_{CC} = 15\text{V}$ . Gain of The transistor is 100. Determine  $I_C$  and  $V_{CE}$ . [06 marks]

 


Figure Q4-a

- (b) Draw the output load line for the circuit shown in Figure Q4-b, If  $V_{CC} = 10V$  and  $R_C = 2k$ . Repeat for  $V_{CC} = 15V$ . [06 marks]

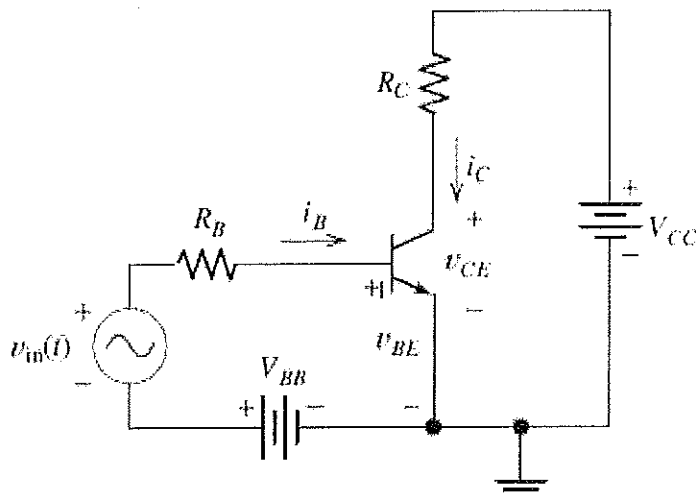


Figure Q4-b

- (c) The dc current gain of the transistor of the circuit shown in Figure Q4-c is 100.  $V_{CE} = 8V$ ,  $R_B = 360k$  and  $R_C = 2k$ . Determine Q point and draw the dc load line. [08 marks]

 


Figure Q4-c

Q5.

- (a) What are the characteristics of an ideal op-amp? List any three characteristics. [03 marks]
- (b) Name any real op amp IC known by you. Name the probable function for at least five terminals of the IC. [03 marks]

- (c) Determine the  $V_o$  of the operational amplifier shown in Figure Q5-c.  $V_1=2V$ ,  $V_2=1V$ ,  $R_1=10k$ ,  $R_2=5k$ . [05 marks]

 


Figure Q5-b

- (d) Determine the  $V_{out}$  of the operational amplifier shown in Figure Q5-d.  $V_{in}=2V$ ,  $R_1=10k$ ,  $R_2=5k$ . [5 marks]

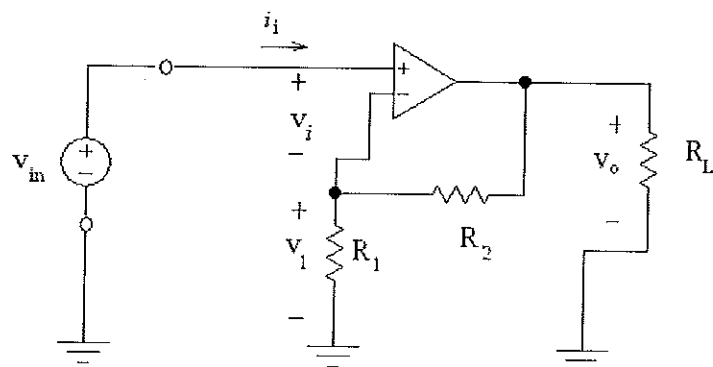


Figure Q5-d

- (e) A differential amplifier with a voltage gain of 50 has a common input signal of 2V to both terminals. This results in an output signal of 20 mV. Determine the common-mode gain and the CMRR. [4 marks]

### Q6.

- (a) Perform the following conversions between number systems with clearly showing the necessary steps.
- $16.2_8$  to decimal, binary and hexa-decimal
  - $1100.1_2$  to decimal and octal
- [05 marks]
- (b) Two's complement representation of an 8 bit binary number is given as 11111010. Determine the decimal value of the number. [03 marks]
- (c) Sign magnitude representation of an 8 bit binary number is given as 10000101. Determine the decimal value of the number. [03 marks]
- (d) Determine one's complement (8 bit) representations of the  $-16_{10}$ . [03 marks]

- (e) Briefly explain the operation of the half adder circuit. Draw the logic circuit of it. [06 marks]

### Q7.

- (a) Rewrite the following Boolean expression using De-Morgan's theorem and implement the logic circuit using **NAND** gates only. [4 marks]

$$Q = \overline{X + Y}$$

- (b) Simplify the following Boolean expression using Boolean Theorems. [4 marks]

- i.  $A + AB$
- ii.  $A + \bar{A}$
- iii.  $\bar{\bar{A}} + A$
- iv.  $(A+1) \bullet (A \bullet A)$

- (c) Simplify the following Boolean function using K-maps.

$$f(A, B, C, D) = \sum m(0, 2, 3, 4, 5, 7, 9, 13, 15)$$

[4 marks]

- (d) Determine the minimal sum of product (SOP) and minimal product of sums (POS) of the following Boolean expression using k-maps.

$$f(A, B, C, D) = \sum m(1, 2, 3, 5, 6, 7, 8, 13)$$

[4 marks]

- (e) What are the universal gates? Briefly explain. [4 marks]

### Q8.

- (a) Draw a circuit diagram of a SR latch and explain the operation. [5 marks]
- (b) Complete the corresponding timing diagram of the circuit shown in figure Q8-b

 


Figure Q8-a

[5 marks]

- (c) Design a counter to count in the following sequence: 0, 1, 2, 3, 4, 5, 6, and 7. Use JK flip-flops and logic gates. Show the state transition diagram, present state-next state table, K-map, logic expressions and the circuit implementation clearly.

[10 marks]

-END-

1

1

1