

The Open University of Sri Lanka  
Faculty of Engineering Technology  
Department of Mechanical Engineering



Study Programme	: Bachelor of Technology Honours in Engineering
Name of the Examination	: Final Examination
Course Code and Title	: DMX3574/MEX3274 Electronics, sensors and actuators
Academic Year	: 2017/18
Date	: 25 <sup>th</sup> January 2019
Time	: 0930hrs-1230hrs
Duration	: 3 hours

### General Instructions

1. Read all instructions carefully before answering the questions.
2. This question paper consists of **Eight (8)** questions in **Eight (8)** pages.
3. Answer **five** questions only, selecting at least **two questions each from part A and part B**. only. All questions carry equal marks.
4. Answer for each question should commence from a new page.
5. This is a Closed Book Test (CBT).
6. Answers should be in clear hand writing.
7. Do not use Red colour pen.

**Part A****Q1.**

- (a) What are the characteristics of an ideal op-amp? List any three characteristics. [03 marks]
- (b) An operational amplifier is shown in Figure Q1-b.  $V_1=2V$ ,  $V_2= 1V$ ,  $R_1= 10k$ ,  $R_2=5k$ .
- Identify the type of operational amplifier
  - Determine  $V_o$  of the operational amplifier

[04 marks]

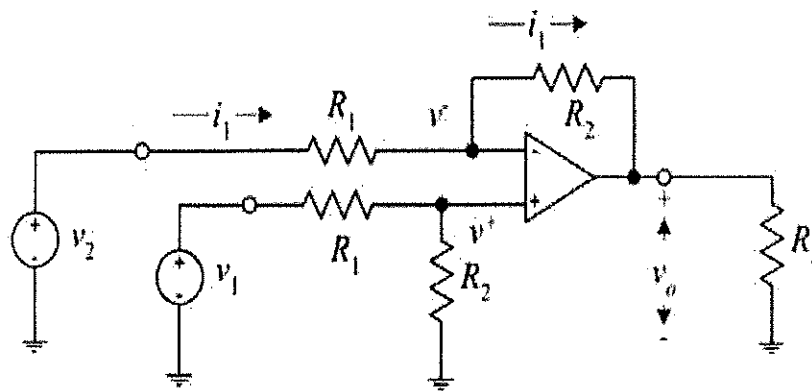


Figure Q1-b

- (c) i. Identify the type of the operational amplifier shown in figure Q1-c.
- ii. Determine the gain of the operational amplifier shown in figure Q1-c
- iii. If the input of the circuit is connected to an AC source with  $V_p= 50mV$ , ( $V_{pp}=100mV$ ), draw the input and output waveforms.

[09 marks]

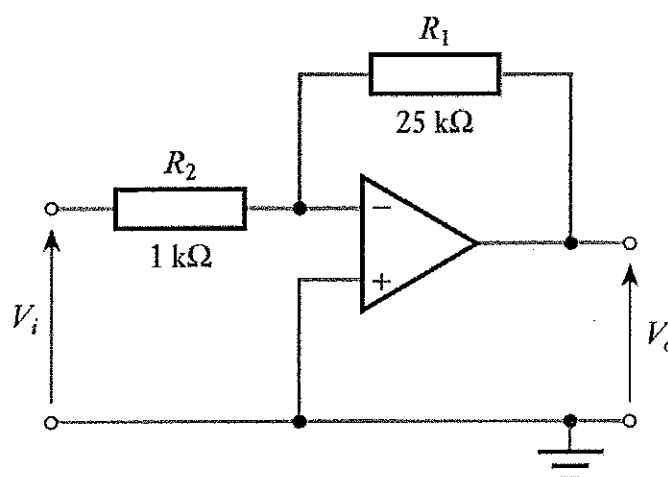


Figure Q1-c

- (d) Determine the  $V_{out}$  of the operational amplifier shown in Figure Q1-d.  $V_1=V_2=3V$ ,  $R_1=30k$ ,  $R_2=15k$ . [04 marks]

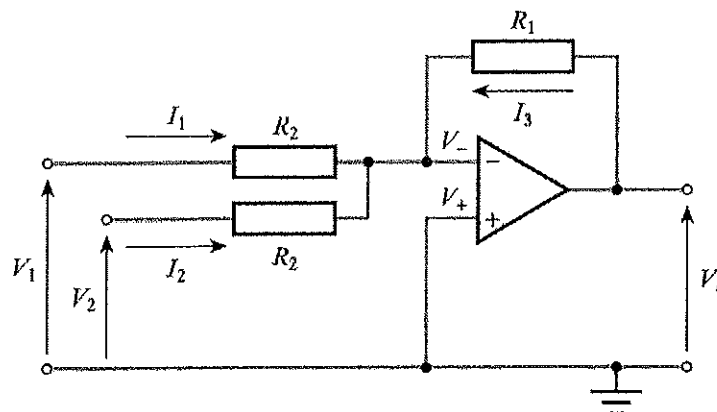


Figure Q1-d

## Q2.

- (a) Determine Thévenin and Norton equivalent circuits of the circuit illustrated in Figure Q2-a. [04 marks]

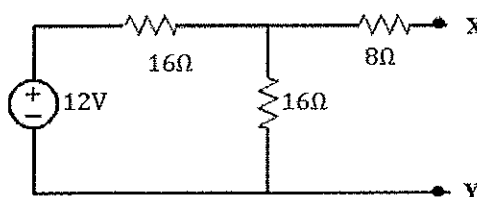


Figure Q2-a

- (b) Determine Thévenin equivalent circuit of the circuit illustrated in Figure Q2-b. [04 marks]

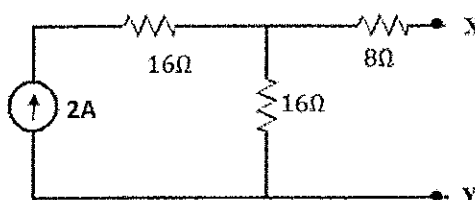


Figure Q2-b

- (c) Suppose that  $R = 5000 \Omega$  and  $C = 1 \mu F$  in the circuit of figure Q2-c. Find the time at which the voltage across the capacitor reaches 63.2% of its initial value.

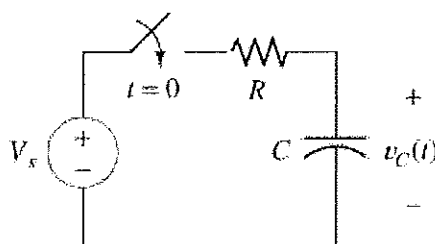


Figure Q2-c

- (d) A Wheatstone bridge is illustrated in Figure Q2-d.  $R_1 = 12\text{ k}$ ,  $R_3 = 240\text{ k}$ , and  $R_2 = 2\text{ k}$ . If  $I_g = 0$ , determine  $R_x$ . [04 marks]

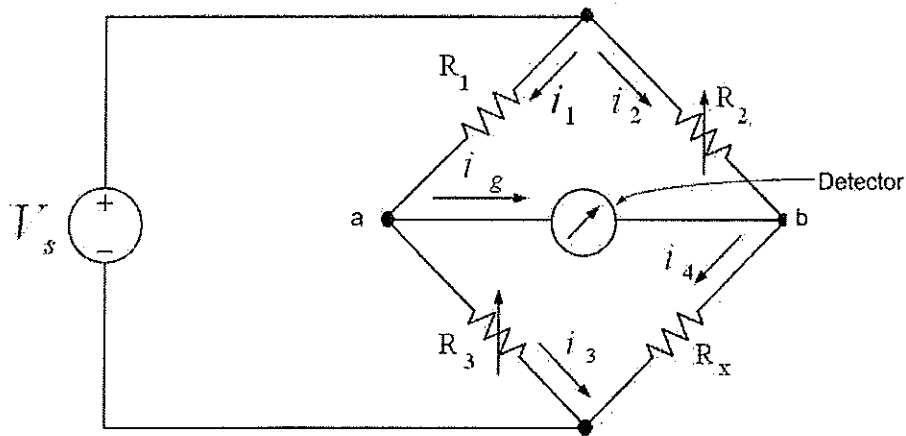


Figure Q2-d

## Q3.

- (a) Simplify the following Boolean expression using Boolean Theorems. [02 marks]
- $A + \bar{A}$
  - $(A+1) \cdot (A \cdot A)$
- (b) 2's complement representation of an 8 bit binary number is given as 11111010. Determine the decimal value of the number. [03 marks]
- (c) Sign magnitude representation of an 8 bit binary number is given as 10000101. Determine the decimal value of the number. [03 marks]
- (d) Determine two's complement (8 bit) representations of the  $-16_{10}$ . [03 marks]
- (e) Simplify the following Boolean function using K-maps.

$$f(A, B, C, D) = \sum m(0, 2, 3, 4, 5, 7, 9, 13, 15)$$

[04 marks]

- (f) Perform the following conversions between number systems with clearly showing the necessary steps.

- $16.2_8$  to decimal, binary and hexa-decimal
- $1100.1_2$  to decimal and octal

[05 marks]

Q4.

- (a) Determine  $V_B$ ,  $V_E$ ,  $I_E$ ,  $I_C$  and  $V_o$  of the BJT amplifier circuit shown in figure Q4-a.

[10 marks]

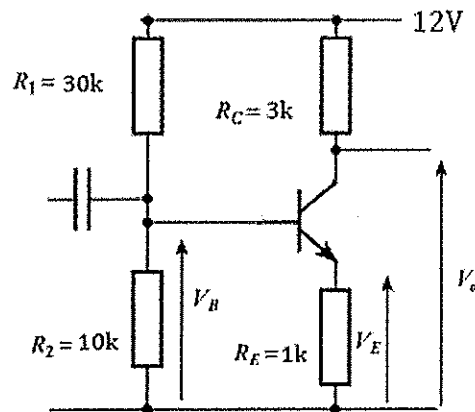


Figure Q4-a

- (b) The dc current gain of the transistor of the circuit shown in Figure Q4-b is 100. Determine Q point and draw the dc load line.

[05 marks]

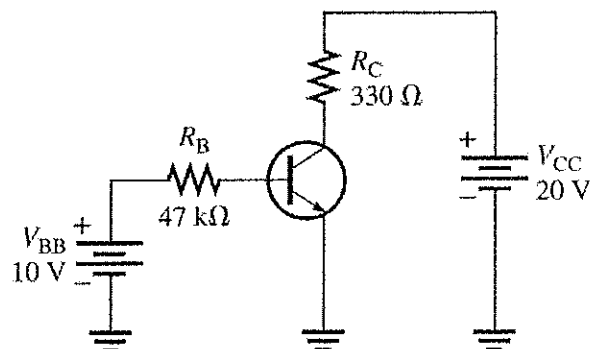


Figure Q4-b

- (c) A double diode clipper circuit shown in Figure Q4-c can be used to limit the peaks of both half cycles of the 10V AC input signal. Sketch the output signal (You should indicate the magnitudes of the signal).

[05 marks]

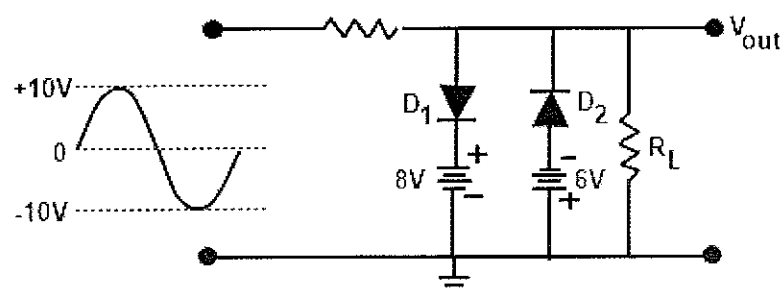


Figure Q4-c

**Part B****Q5.**

- (a) Identify the type of optical encoder disk shown in the Figure Q5. [03 marks]

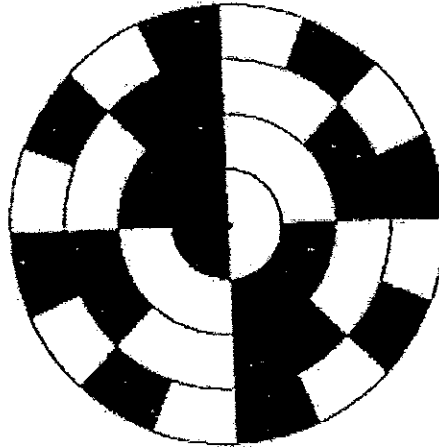


Figure Q5

- (b) Determine the angular resolution of the encoder shown in the Figure Q5. [04 marks]
- (c) How do you improve the resolution of this encoder to 5.625 degrees? Explain. [04 marks]
- (d) Briefly explain following static characteristics of the sensors. [09 marks]
- i. Resolution
  - ii. Accuracy
  - iii. Precision

**Q6.**

- (a) Draw a simple schematic diagram of a linear variable differential transformer (LVDT) and explain the operation briefly. [07 marks]
- (b) Name any three types of temperature sensors. [03 marks]
- (c) A stepper motor is working in the full step mode and the step angle is  $3.6^\circ$ . Calculate the rotational speed of the stepper motor (in rpm) if stepping rate is 200 pulses/sec. [03 marks]
- (d) What are the three common types of stepper motors? [03 marks]
- (e) Single stack three phase variable reluctance stepper motor is illustrated in Figure Q6-e. Number of rotor teeth ( $n_r$ )=8 and number of stator teeth ( $n_s$ )=12. If the switching sequence of the phase winding is **1-2-3-1**. Determine the direction of rotation. [04 marks]

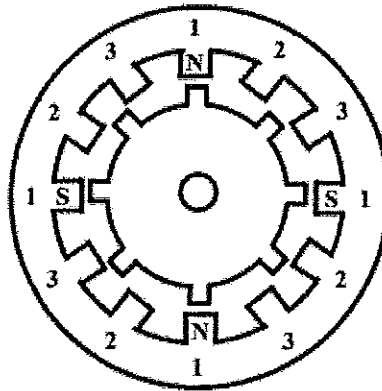


Figure Q6-e

Q7.

- (a) Draw the symbols of following pneumatic components. [06 marks]
- 2/2 way push button valve
  - 5/2 push button valve
  - Double acting cylinder
- (b) What are the main three parts of an air service unit? [03 marks]
- (c) An object has to move using a single acting cylinder. The piston rod is to extend when a push button is pressed and return to the start position when the push button is released.
- Draw a pneumatic circuit to perform the operation. [07 marks]
  - Draw a hydraulic circuit to perform the same operation. [04 marks]

Q8.

- (a) A three-phase induction motor is wound for four poles and supplied from a 50Hz source. The slip is 2%. Determine the synchronous speed and the speed of the rotor. [04 marks]
- (b) An induction motor (220Vrms, 60-Hz three phase Y-connected) draws 25A at a power factor of 80% lagging. The total stator copper loss is 300W, the total rotor copper loss is 100W. Determine the input power, the power crossing the air gap and the developed power. [08 marks]

- (c) The magnetization curve of a machine is shown as Figure Q8-c. It is operating as a motor at a speed of 800 rpm with  $I_A = 30$  A and  $I_F = 2.5$  A. The armature resistance is  $0.5 \Omega$  and the field resistance  $R_F = 10 \Omega$ . Determine the

- voltage  $V_F$  applied to the field circuit,
- voltage  $V_T$  applied to the armature,
- developed torque, and
- developed power.

[08 marks]

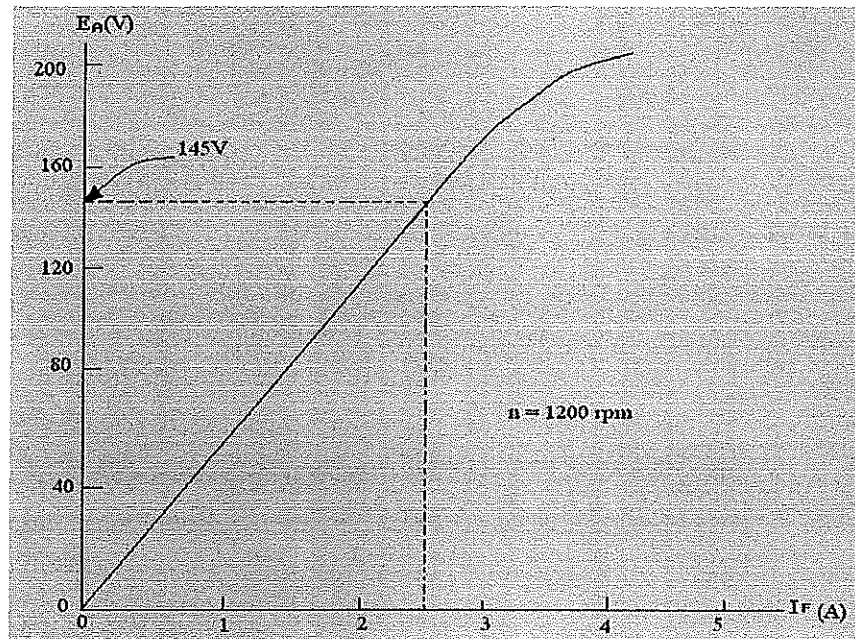


Figure Q8-c(i)

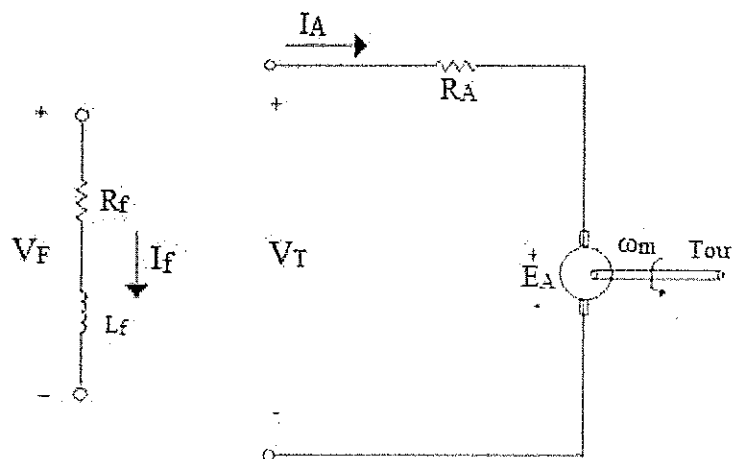


Figure Q8-c(ii)

-END-