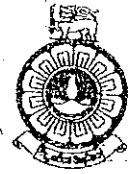


23
00155

THE OPEN UNIVERSITY OF SRI LANKA
DEPARTMENT OF COMPUTER SCIENCE
B. SC. DEGREE PROGRAMME 2016/2017
FINAL EXAMINATION
CPU3141: DIGITAL COMPUTER FUNDAMENTALS
DURATION: TWO HOURS (2 HOURS)



Date: 27.12.2017

Time: 1.30 pm – 3.30 pm

Answer Four (04) Questions

Q1.

- (i) Briefly explain how a particular number can be represented in different Number Systems with the use of an **example**.
- (ii) Convert the following numbers into **Decimal** (Clearly show the steps).
 - a) $C52F_{16}$
 - b) 796_8
 - c) 100101_2
- (iii) Write -27_{10} using following **binary representations** for **negative numbers**.
 - a) Sign Magnitude
 - b) One's Complement
 - c) Two's Complement
- (iv) What is the importance of **Binary Numbers** to the digital systems. ?
- (v) **Calculate** the following. (Clearly show the steps)
 - a) $1011_2 + 10111_2$
 - b) $1101_2 - 1010_2$
 - c) $10111_2 * 1011_2$
 - d) $1111_2 / 101_2$

Q2.

(i) Write short descriptions about the following **Binary Codes**.

- a) Error- Detection code
- b) Gray Code
- c) BCD

(ii) What is the difference between **1 + 1 in Binary** and **1 + 1 in Boolean Logic**?

(iii) Prove the two **De Morgan's Theorems**. (Clearly Show the steps)

(iv) Briefly describe the following **Logic Families**.

- a) TTL Logic Family
- b) CMOS Logic Family

(v) Convert following **Gray code** value into **binary**. (Show the steps)

100100100

Q3.

(i) Derive the **Truth Table** of a **JK Flip flop** and draw the corresponding **circuit diagram** (Consider a **NAND implementation**).

(ii) Draw the **logic circuit** of a **4 – to – 1 Multiplexer**.

(iii) List **three (03)** uses of the **Multiplexer**.

(iv) Draw the **timing diagram (pulse waveform diagram)** of the following circuit (Fig.1) with given inputs (Fig 2).

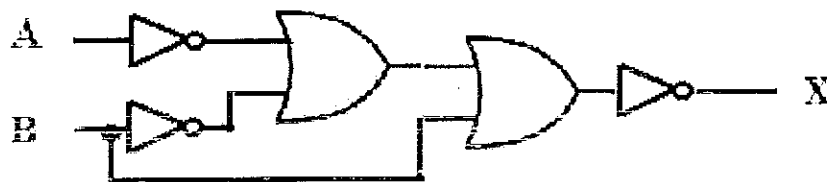


Figure 1: Logic Circuit

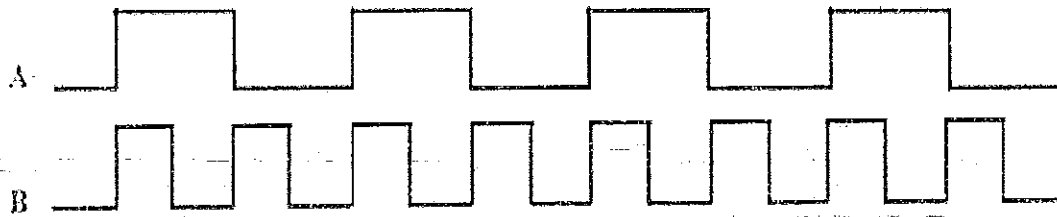


Figure 2: Inputs A and B

(v) Draw a **Full Adder circuit** for **3-bit addition** operation. (Use block diagrams)

Q4.

Consider the following **PoS Boolean Expression**;

$$(A+B+C+D')(A+B+C'+D)(A'+B'+C+D')(A+B'+C'+D)(A'+B'+C'+D) \\ (A'+B+C+D')(A'+B+C'+D)(A'+B'+C'+D)$$

- Draw the **K'Map** for the above expression.
- Simplify the K'Map and derive the simplified **SoP** expression.
- Simplify the K'Map and derive the simplified **PoS** expression.
- Draw the **simplified circuits** for both expressions in (ii) and (iii).
- Discuss about **Maxterm** and **Minterm** representations.

Q5.

- Draw the **logic diagram** of a **4 – bit Ring Counter** with **timing diagram**.
- Compare **Asynchronous** and **Synchronous counters**.
- Draw the **Asynchronous Circuit** described by the following **State Table**.

Present State		Next State			
		X = 0		X = 1	
0	0	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	1	1	1	0	1

- (iv) Determine whether there is/are **Race Conditions** in the above (iii) Asynchronous Circuit. (Clearly show the steps)
- (v) Explain about a **Circuit Hazard** using an **example**.

Q6.

- (i) What are the **components** of the **CPU of a digital system**? Write short descriptions about the components.
- (ii) Briefly describe following terms related to **Digital Memory**.
 - a) Data
 - b) Address
 - c) Random Access
 - d) Sequential Access
- (iii) Why do we need **Digital Memory**? Discuss.
- (iv) Draw **Block Diagrams** of three (03) **PLD configurations**.
- (v) What are the **design considerations** in designing a **RAM with PAL**?

***** All Rights Reserved *****