

THE OPEN UNIVERSITY OF SRI LANKA

Faculty of Engineering Technology

Department of Electrical & Computer Engineering

Bachelor of Technology Honours in Engineering – Level 6

FINAL EXAMINATION – (2014/2015)



ECX6151 – Digital Electronic Systems

Time Allowed: 3 hours

Date: 18th September 2015

Time: 0930 – 1230 hours

INSTRUCTIONS TO CANDIDATES

1. This question paper contains one (1) question in **SECTION A** and four (4) questions in **SECTION B** on four (4) pages.
2. Answer **ALL PARTS** in **SECTION A**. [70 Marks]
3. Answer any **TWO (2)** questions from **SECTION B**. [30 Marks]
4. Refer the Annexure of the VHDL syntax given in page five (5) to write VHDL code.
5. Clearly state your assumptions if any

SECTION A: Answer ALL questions. [70 Marks]

Digital Electronic Filter Unit (DEFU)

The following scenario is about a Digital Electronic Filter Unit (DEFU) which is used for filtering unwanted noise in the optical encoder's outputs of a motor due to electromagnetic coupling and vibration in the operating environment. A pair of DEFUs, one for the channel A and the other one for the channel B, are required to filter out the noise on the incoming signals. Figure Q1 depicts the architecture of the DEFU.

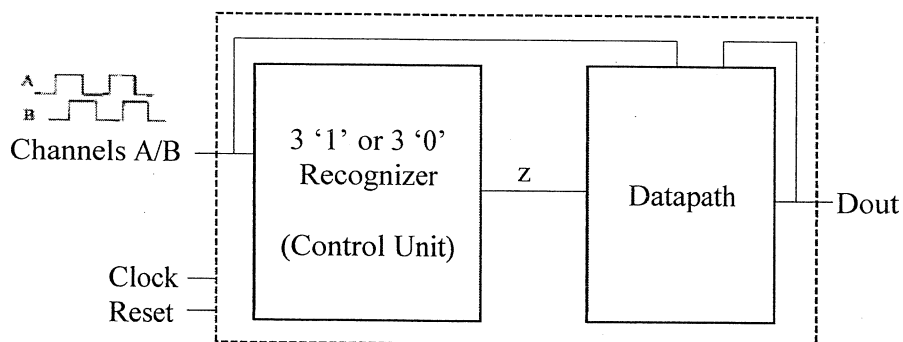


Figure Q1: Digital Electronic Filter Unit

The DEFU consists of a Control unit and a Datapath on each channel of the optical encoder. The Control unit is a recognizer that checks if the input from the optical encoder (Channel A/B)) has short duration pulses and then controls the input data to flow through the datapath, which consists of a 2: 1 multiplexer and a D flip-flop. If the input level has the same value (1 or 0) on at least three (3) consecutive clock cycles, then the input is not considered as a noise. In this case the output of the recognizer (z) is active high, which then allows the input data (Channels A/B) to flow through the datapath. The data value, thus becomes the new output of the DEFU. Otherwise the input is considered as a noise and the datapath output (Dout) of the DEFU remain the same.

Reference: Ming-Fa Tsai; Chien-Pang Chen, "Design of a quadrature decoder/counter interface IC for motor control using CPLD," in *IECON 02 [Industrial Electronics Society, IEEE 2002 28th Annual Conference of the]*, vol.3, no., pp.1936-1941 vol.3, 5-8 Nov. 2002

Clearly state your assumptions (if any).

[Q1]

- (i) Draw a circuit diagram for the Datapath of the DEFU. [05 Marks]
- (ii) Draw a waveform of the DEFU. Clearly show the Channel A/B, z, Dout, and the Clock signals. [05 Marks]
- (iii) Draw a state diagram for the Recognizer of the DEFU. [10 Marks]
- (iv) Draw an ASM chart for the Recognizer of the DEFU. [10 Marks]
- (v) Draw a state transition table for the Recognizer of the DEFU. [10 Marks]
- (vi) Draw complete circuit diagram of the DEFU using D Flip-Flops and necessary digital logic gates. [20 Marks]
- (vii) Write behavioral/structural VHDL code for the DEFU. [10 Marks]

SECTION B: Answer any TWO questions. [30 Marks]

[Q2] The internal connection diagram of a PLA is shown in the Figure Q2.

- (i) Write the equations realized by the PLA. [06 Marks]
 (ii) Specify the truth table for a ROM which would realize the same function. Clearly show the size of the ROM. [04 Marks]
 (iii) Implement the ROM circuit of the truth table above (ii) using digital logic devices. [05 Marks]

 


Figure Q2

- [Q3] (i) Derive the equations for 1 bit full adder. [03 Marks]
 (ii) Implement the 1 bit full adder circuit using above (i). [04 Marks]
 (iii) Write structural VHDL code of the 1 bit full adder circuit implemented in above (ii) [08 Marks]
- [Q4] Consider the Boolean function $F(x, y, z) = \Pi(0, 3, 4, 5, 7)$.
- (i) Draw the K-map for the function (F) and find a optimize expression for function (F). [08 Marks]
 (ii) Implement the function (F) using 2 to 1 Multiplexers. [07 Marks]
- [Q5] Consider the state table (Table Q5) given below.

- (i) Reduce the state table (Table Q5) to a minimum number of states. [08 Marks]
 (ii) Draw the reduced state table and state diagram. [07 Marks]

Table Q5

Present state	Next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

Annexure

Syntax of selected instructions of the VHDL

- ✕ **ARCHITECTURE** *architecture_name* **OF** *entity_name* **IS**
 [declaration part]
BEGIN
 Concurrent statements part
END *architecture_name*
- ✕ **CASE** *expression* **IS**
 WHEN *value=>* *statements*;
 WHEN *value=>* *statements*;
 WHEN OTHERS *statements*;
END CASE;
- ✕ **COMPONENT** *component_name*
 PORT (*port1_name* : *port1_type*;
 port2_name : *port2_type*;
 ...);
END COMPONENT [*component_name*];
- ✕ **ENTITY** *entity_name* **IS**
 PORT (*port1* : *port1_type*;
 port2 : *port2_type*;
 ...);
END *entity_name*;
- ✕ **IF** *condition* **THEN**
 Sequence of statements
 {**ELSIF** *condition* **THEN**
 Sequence of statements}
 [**ELSE**
 Sequence of statements]
END IF;
- ✕ **LIBRARY** *library_name*;
- ✕ *Instance_label*: *component_name* **PORT MAP** (*first_port*, *second_port*,
 third_port, ...);
Instance_label: *component_name* **PORT MAP** (*formall=>* *actuell*,
 formall=> *actuell*,
 formall=> *actuell*, ...);
- ✕ [*process_label*:] **PROCESS** (*signal1*, *signal2*, ...)
 [declaration part]
 BEGIN
 Sequential statements part
 END PROCESS;
- ✕ **SIGNAL** *signal_name* : *signal_type*;
- ✕ **TYPE** *type_name*;
- ✕ **USE** *library_name.type_expression.inclusion*;
- ✕ **WAIT FOR** *time_expression*;
- ✕ **WAIT ON** *signal1*, *signal2*, ...;
- ✕ **WAIT UNTIL** *condition*;
- ✕ **WHILE** *condition* **LOOP**
 Sequential statements
END LOOP;