

The Open University of Sri Lanka  
Faculty of Engineering Technology  
Department of Electrical & Computer Engineering




Study Programme	: Bachelor of Technology Honours in Engineering
Name of the Examination	: Final Examination
<b>Course Code and Title</b>	<b>: EEX6550 / ECX6250 Analog Electronic Systems</b>
Academic Year	: 2019/2020
Date	: 23 <sup>rd</sup> January 2021
Time	: 1330-1630hrs
Duration	: <b>3 hours</b>

### General Instructions

1. Read all instructions carefully before answering the questions.
2. This question paper consists of **Seven (7)** questions in **Six (6)** pages.
3. Answer any **Five (5)** questions only. All questions carry equal marks.
4. Answer for each question should commence from a new page.
5. Relevant charts / codes are provided.
6. This is a Closed Book Test (**CBT**).
7. Answers should be in clear hand writing.
8. Do not use red colour pens.

Q1. Consider the circuit diagram in Figure-Q1.

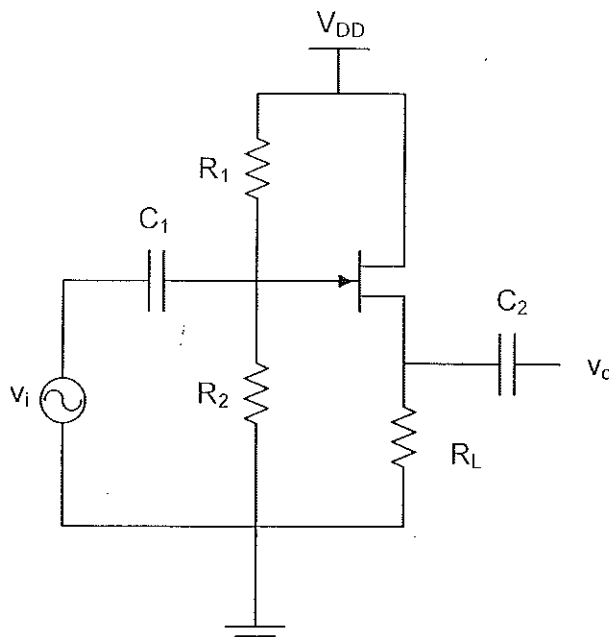

**Figure-Q1**

- (a) Draw the high frequency equivalent circuit for the single stage amplifier shown in Figure-Q1. **(7Marks)**
- (b) Clearly stating all your assumptions, find an expression for the voltage gain,  $A_v$ . **(8Marks)**
- (c) Hence show that the low frequency voltage gain for this amplifier is  $\frac{\mu}{\mu+1}$ , where  $\mu = \frac{g_m}{g_d}$ . **(5Marks)**

Q2. Let the transistor in the amplifier circuit in Figure-Q2 has the following hybrid- $\pi$  parameters with the usual notation.  $r_{be} = 1k\Omega$ ,  $r_{bc} = 4M\Omega$ ,  $r_{ce} = 80k\Omega$ ,  $C_{bc} = 3pF$ ,  $C_{be} = 100pF$  and  $g_m = 50mAV^{-1}$ . Assume the effect of all the other unmentioned parameters to be negligible.

- (a) Draw the high frequency equivalent circuit for this amplifier circuit. **(6Marks)**
- (b) Using Miller's theorem, simplify the equivalent circuit model. **(6Marks)**
- (c) Hence, find the voltage gain of the same amplifier. **(8Marks)**

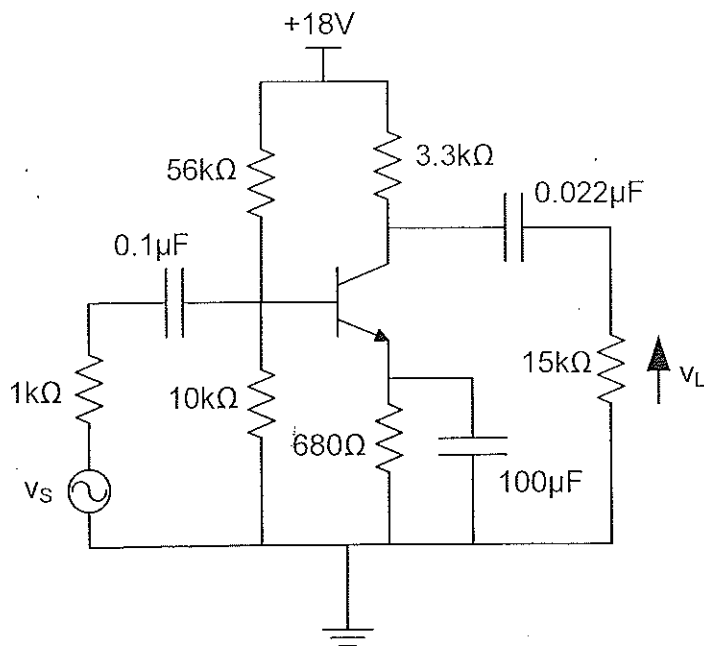


Figure-Q2

Q3. Consider the circuit in the Figure-Q3.

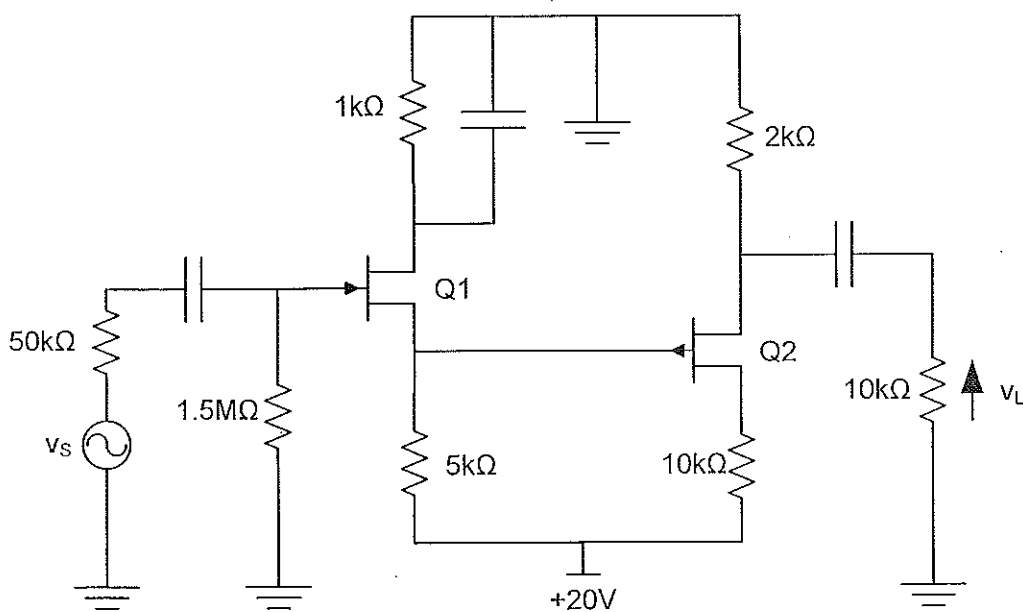


Figure-Q3

Assume that  $r_{d1} = r_{d2} \rightarrow \infty$ ,  $g_m = 1.6 \text{ mA V}^{-1}$  for both Q1 and Q2.

(a) Draw the low frequency equivalent circuit.

(8Marks)

Hence find,


(b) Input impedance.

(4Marks)

(c) Mid band voltage gain  $\frac{v_L}{v_s}$ .

(8Marks)

Q4.

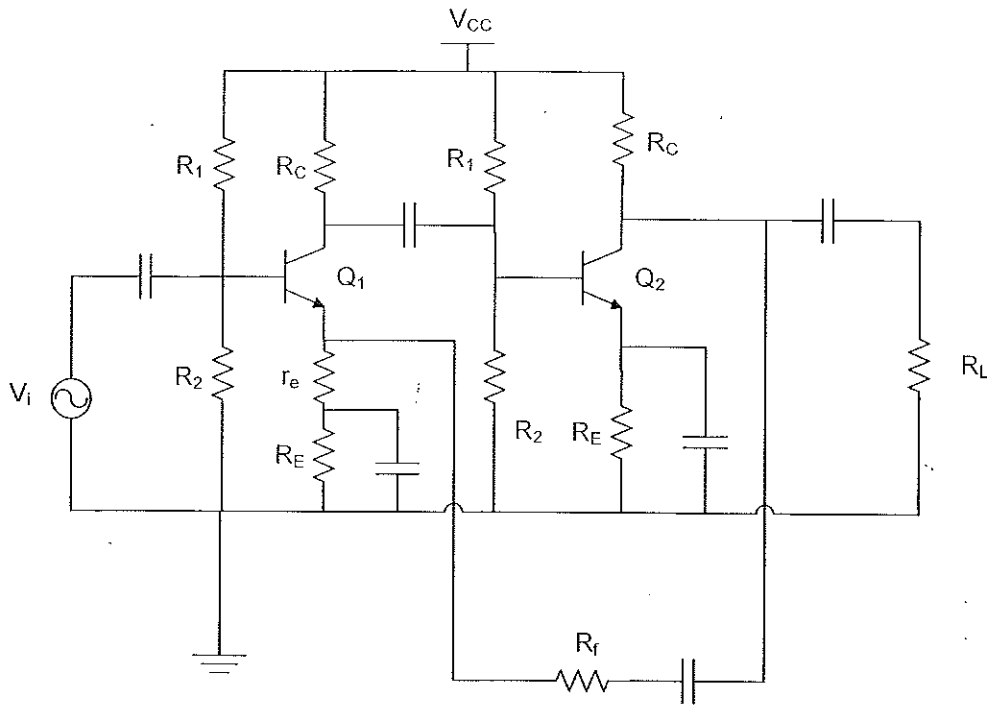**Figure-Q4**

For the amplifier circuit shown in Figure-Q4,  $V_{CC} = 10\text{ V}$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 2.2\text{ k}\Omega$ ,  $R_C = 3.6\text{ k}\Omega$ ,  $R_E = 1\text{ k}\Omega$ ,  $r_e = 100\Omega$ ,  $R_L = 10\text{ k}\Omega$  and  $R_f = 4.7\text{ k}\Omega$ . Both transistors Q1 and Q2 are identical and have  $h_{fe} = 100$ ,  $h_{ie} = 1.2\text{ k}\Omega$ .

- Identify the type of feedback used. **(2Marks)**
- Consider the circuit in Figure-Q4 without the feedback. Calculate the voltage gain and the input impedance. **(10Marks)**
- Calculate the feedback ratio. **(4Marks)**
- Hence calculate the overall voltage gain with feedback. **(4Marks)**

Q5.

- Starting from the first principles, derive the Barkhausen criteria for oscillations to occur. **(4Marks)**
- Stating all your assumptions, derive an expression for the feedback factor for the circuit in Figure-Q5. **(4Marks)**
- Derive an expression for the forward gain. **(6Marks)**
- Hence find the frequency of oscillation ( $C = 100\mu\text{F}$ ,  $L_1 = L_2 = 10\text{ mH}$ ,  $R_1 = R_2$ ). **(6Marks)**

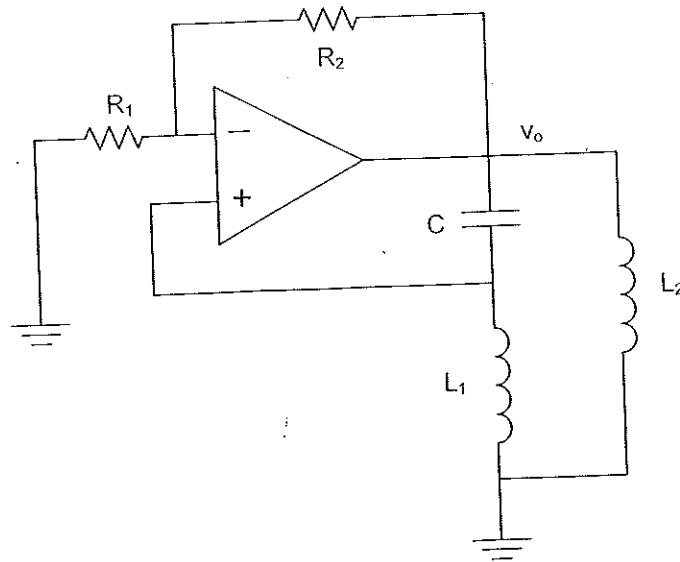


Figure-Q5

Q6. A low-pass filter circuit is shown in Figure-Q6. Assume that the op-amp is ideal.

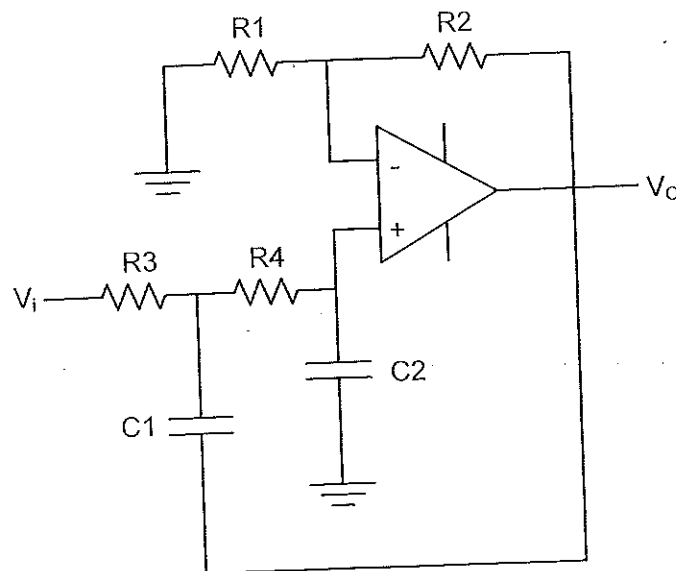


Figure-Q6

- (a) For the circuit in Figure-Q6, derive the transfer function  $H(s)$ . (8 Marks)
- (b) Transfer function for a second order Butterworth filter is given by,


$$A(s) = A_0 \frac{1}{\left(\frac{s}{\omega_c}\right)^2 + \sqrt{2}\left(\frac{s}{\omega_c}\right) + 1}$$

Hence show that the bandwidth of the above filter is given by  $\frac{1}{2\pi\sqrt{R_3R_4C_1C_2}}$ . (4 Marks)


- (c) Let  $R_3 = R_4$  and  $C_1 = C_2$ . Design a second order Butterworth filter with a bandwidth of 20Hz. (4 Marks)
- (d) Calculate the pass band gain of the filter. (4 Marks)

Q7.

- (a) Starting from the diode characteristic equation  $I_D = I_S \left( e^{\frac{V_D}{\eta V_T}} - 1 \right)$  derive an expression for the intrinsic resistance,  $r_e$  of the diode junction. (4 Marks)
- (b) Figure-Q7(b) shows a diode-based log amplifier. Show that  $V_o \propto \ln(V_{in})$ . (8 Marks)

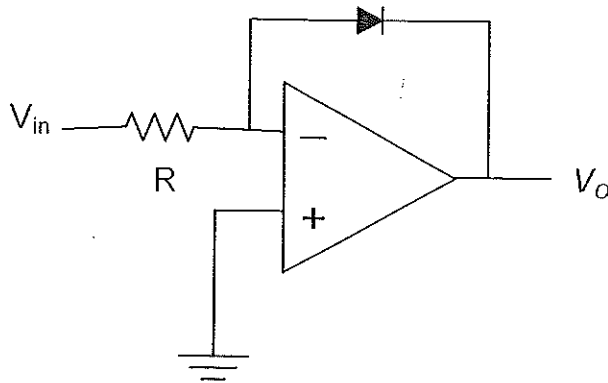Figure-Q7 (b)

- (c) Explain the operation of the precision rectifier arrangement shown in Figure-Q7 (c). (8 Marks)

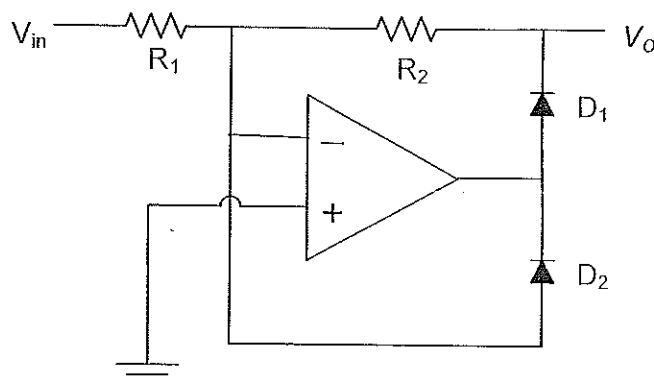Figure-Q7 (c)