

The Open University of Sri Lanka
Faculty of Engineering Technology
Department of Electrical & Computer Engineering



Study Programme	: Bachelor of Technology Honours in Engineering
Name of the Examination	: Final Examination
Course Code and Title	: EEX4331 Circuit Theory and Design
Academic Year	: 2019/2020
Date	: 25 th September 2020
Time	: 0930-1230hrs
Duration	: 3 hours

General Instructions

1. Read all instructions carefully before answering the questions.
 2. This question paper consists of Seven (7) questions in **Five (05)** pages.
 3. Answer any **Five (5)** questions only. All questions carry equal marks.
 4. Answer for each question should commence from a new page.
 5. This is a Closed Book Test (CBT).
 6. Answers should be in clear hand writing.
 7. **Do not** use a red colour pen.
 8. Adhere to usual notations.
-

Q1. (a). Consider the circuit shown in Figure 01-(a).

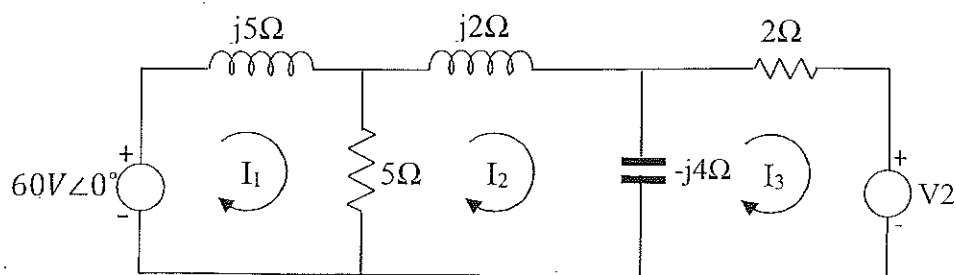


Figure 01-(a)

- Apply mesh analysis method to obtain the matrix equation. [03 Marks]
- Use above matrix equation to determine the value of V_2 such that $I_3 = 0$. [07 Marks]

(b). Use Millman's theorem to simplify the circuit given in Figure 01-(b).

Hence or otherwise determine the current through Z_L .

[10 Marks]

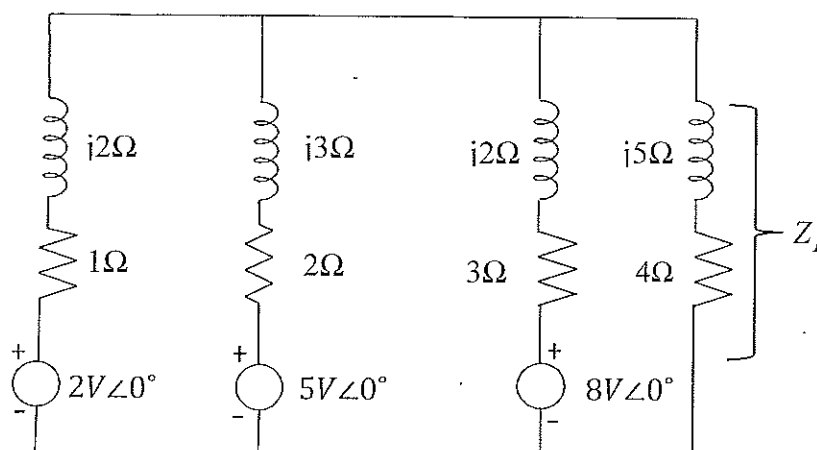


Figure 01-(b)

Q2. A circuit having a capacitor and a resistor is shown in Figure 02. Switch S_1 is used to connect sources either E_1 or E_2 ($E_2 > E_1$) to the RC branch of the circuit. Initially the switch S_1 is at position X and the capacitor is fully discharged.

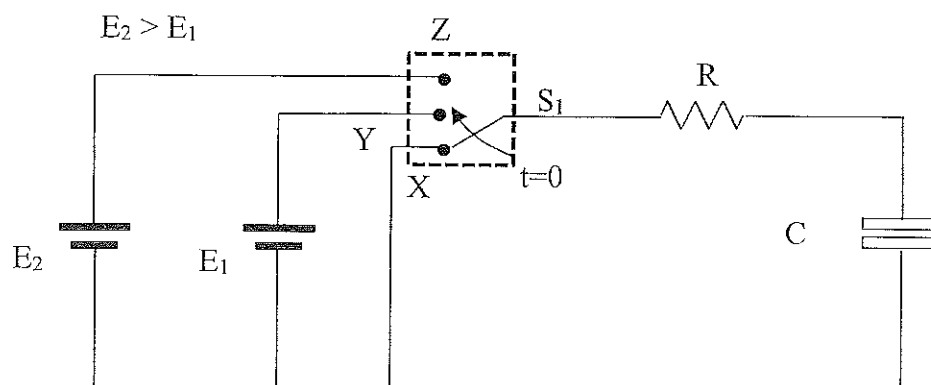


Figure 02
Page 2 of 5

- At $t = 0$ the switch is moved from position X to Y. Apply Kirchhoff's voltage law and write the voltage equation in differential form. [02 Marks]
- Derive an expression for the instantaneous current $i(t)$ by solving the differential equation obtained in 'i' [06 Marks]
- Calculate the voltage across the capacitor at $t = 100$ ms. Use $R = 10 \text{ k}\Omega$, $C = 10 \text{ }\mu\text{F}$ and $E_1 = 10 \text{ V}$. [02 Marks]
- While the circuit is in operation at $t = 5$ s the switch S_1 is suddenly moved from position Y to Z without any interruption. Using the results obtained above, deduce an expression to determine the voltage across the capacitor from $t = 5$ s onwards. State any assumptions you made. Select initial state as $t = 0$. [05 Marks]
- Using the two expressions obtained in (ii) and (iv), sketch the voltage variation of the capacitor against time of this new condition. (starting from 5s) [05 Marks]

Q3. Consider the RLC circuit shown in Figure 03. At $t = 0$ the switch S_1 is closed.

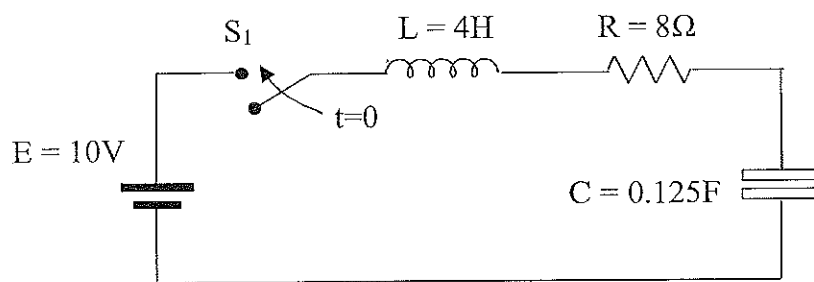


Figure 03

- Write a differential equation relating voltages across each element using Kirchhoff's voltage law. Assume the capacitor is initially fully discharged. [02 Marks]
- Solving the differential equation you have written in 'i', obtain an expression to the current through the circuit for $t > 0$. (consider the initial voltages across and currents through each element) [12 Marks]
- Plot the variation of current against time of the circuit. (start from $t = 0$) [04 Marks]
- State the type of the response of this circuit. [02 Marks]

Q4. Consider the circuit given in Figure 04. The switch S_1 is closed at $t = 0$ s.

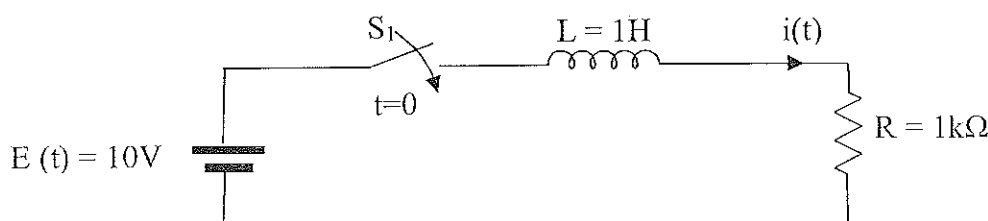


Figure 04

- Write the differential equation to find the current through the circuit after closing the switch. [02 Marks]
- Convert the differential equation in to s – domain using Laplace Transform and obtain an expression to the impedance function $Z(s)$ which is also in s – domain. [02 Marks]
- Derive the solution for current through the circuit in s – domain $I(s)$. [02 Marks]
- Using inverse Laplace transform, derive the solution for current through the circuit in time domain $I(t)$. [08 Marks]
- Using the expression derived in step iii above, obtain the natural response of the circuit in both time and s – domain. [06 Marks]

Hint – Replace the voltage source with a voltage impulse.

Q5.

- Determine whether the following functions are positive real. [02 Marks]

Hint- Use the partial fraction expansions where necessary.

$$(a). F(s) = \frac{S^2 + 1}{S^3 + 4S} \quad (b). F(s) = \frac{(S + 2)(S + 4)}{(S + 1)(S + 3)}$$

- Synthesize the following RC impedance function using Foster I and II, Cauer I and II forms. [16 Marks]

$$Z(s) = \frac{2S^2 + 8S + 6}{S^2 + 2S}$$

- Synthesize the following RLC driving point impedance function. [02 Marks]

$$Z(s) = \frac{S^2 + 2S + 2}{S^2 + S + 1}$$

Q6.

Pole zero maps of four different impedance functions $Z(s)$ are shown in Figure 6. Note that the locations of poles and zeros are not drawn to scale.

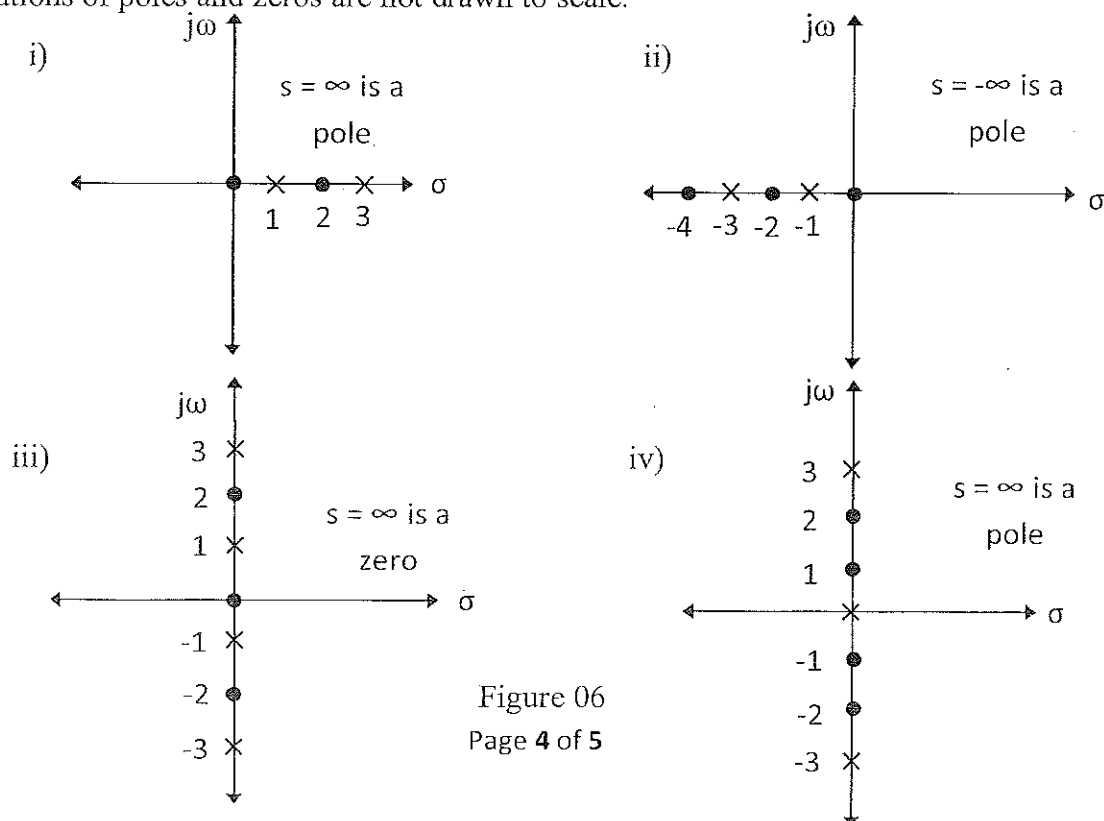


Figure 06
Page 4 of 5

- i. Giving reasons state which of the above systems are realizable in the form of RC, RL or LC. [04 Marks]
- ii. Formulate the driving point impedance function for the realizable systems that you have figured out. [04 Marks]
- iii. Realize each network using:
 - a. Foster 1st form.
 - b. Cauer 2nd form. [12 Marks]

Q7.

- i. Write the terminal characteristic equations of a general two port network in matrix form using,
 - a. Open circuit impedance (Z) parameters.
 - b. ABCD transmission parameters. [02 Marks]
- ii. A simplified equivalent circuit diagram of a transmission line is given in Figure 07.

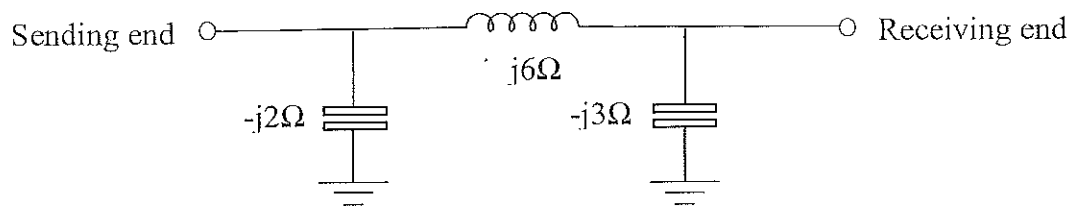


Figure 07

- a. Considering the circuit as a two port network; find the open circuit impedance parameters. [04 Marks]
- b. Convert the impedance parameters in to ABCD parameters. [02 Marks]
- c. Derive an expression to the characteristic impedance (Z_0) of the network and obtain the value of it. [04 Marks]
- d. A load is connected to the receiving end and a generator is connected to the sending end of the above transmission line. The impedance of the load and internal impedance of the generator are equal to the characteristic impedance (Z_0). Determine the generator output terminal voltage (magnitude and phase) to maintain the Voltage (V_{RMS}) across the load at 150V. [08 Marks]

END

