



The Open University of Sri Lanka  
 B.Sc. Degree Programme- Level 05  
 Final Examination 2021/2022  
 PHU5303 - Data Acquisition and Signal Processing  
 Duration: Two (2) Hours


Date: 28.10.2022

Time: 2.00 p.m. – 4.00 p.m.

ANSWER ANY FOUR (04) QUESTIONS ONLY.

1. (a)
  - i. Briefly discuss the basic processing stages of a computer-aided data acquisition system
  - ii. With the aid of circuit diagrams explain how to use the following temperature sensors in data acquisition systems.
    - A. Thermistor
    - B. PN junction thermometer
- (b)
  - i. Draw a diagram of a photomultiplier tube
    - A. Mark and name all the parts of the photomultiplier tube
    - B. Write down the function of each part mentioned in the photomultiplier tube
  - ii. Briefly discuss the usage of the Cerenkov detector

Figure 01

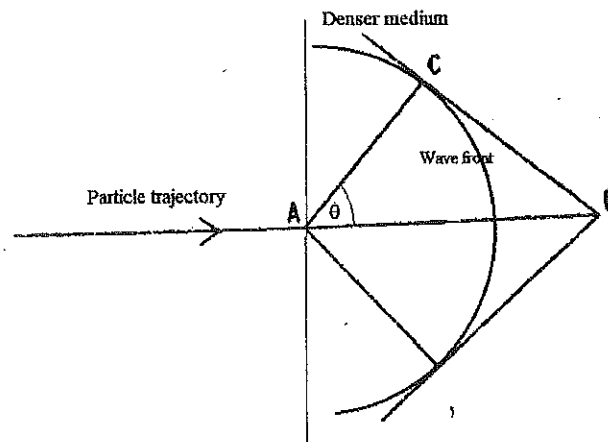

- iii. Figure 01 shows an electron travelling through a medium of refractive index of  $n$  with a velocity  $v$ . Derive an expression for  $\cos\theta$ .
  - iv. Assume that an electron move through the water with the momentum of  $1 \text{ GeV}/c$ . The momentum ( $p$ ) of a relativistic particle can be expressed as follows  $p = \frac{m\beta}{\sqrt{1-\beta^2}}$
- Where  $m$  is the rest mass of the electron of  $0.5 \text{ MeV}$ ,  $\beta$  is the ratio of the velocities of the moving electron and the emitted radiation. Calculate  $\beta$  ( Velocity of light  $c= 2.997 \times 10^8 \text{ ms}^{-1}$  )
- v. Find the velocity of the electron.
  - vi. If the refractive index of water is 1.33 show that the Cerenkov radiation is emitted by the electron.

2. (a)

- i. Draw a circuit diagram of an Op-amp follower/ Unity gain circuit.
- ii. Briefly discuss how to use the Op-amp follower/ Unity gain circuit in a data acquisition system
- iii. Using a comparator, design a circuit to convert a sine wave into a square wave with 10 V peak to peak output.

(b)

- i. Using the proper values for resistors, design a non-inverting amplifier with a voltage gain of 11.
- ii. Using a non-inverting amplifier, construct a multi-range voltmeter for the following ranges 0 - 0.1 V, 0 - 0.25 V and 0 - 0.5 V
- iii. Briefly discuss the advantages of using the above multi-range voltmeter over an analogue voltmeter.

3. (a)


- i. Explain briefly why noise plays a major role in a data acquisition system
- ii. Describe briefly the following types of noise.
  - A. Johnson Noise
  - B. Shot Noise
  - C. Environmental Noise

(b)

- i. Draw low pass RC and RL filters circuits
- ii. Write down the voltage transfer ratio for both types of filters mentioned in part (i). Define the symbols used in your answer.
- iii. A detector produces a range of frequencies from 4 kHz to 6 kHz. In addition, it picks up a noise with a 15 kHz frequency.
  - A. Find the cutoff frequency for a suitable low pass filter for removing the noise.
  - B. Calculate the resistance (R) and capacitance (C) to design a RC filter for that purpose.

4.

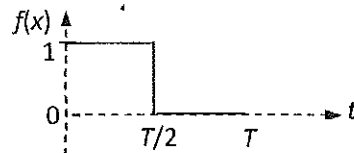
- i. Why is spectrum analysis useful in signal processing stages of a data acquisition system?
- ii. Explain the theory behind the spectrum analysis by writing down the relevant equations.
- iii. Fourier analyze the following square waveform of period  $T=1/f_0$  to find its spectrum.



- iv. Hence draw the power spectrum of the above signal.
- v. If the signals of the above spectrum needs to be digitized, what would be the maximum sampling interval that avoids aliasing?

5.

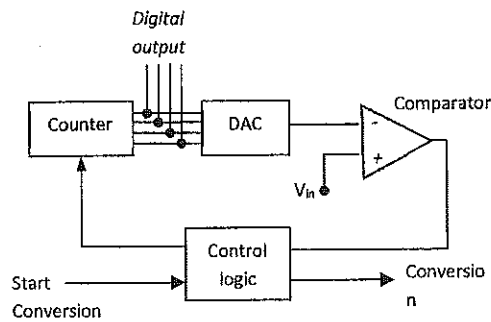- i. Define the terms (i) Range (ii) Resolution (iii) Quantization error and (iv) sampling error in relation to analogue to digital conversion of signals.
- ii. Write down two methods to convert a digital signal to an analogue signal. Discuss the advantages and disadvantages of these two methods.
- iii. Briefly explain how an analogue signal is converted to a digital signal with the counter ADC given in the following block diagram.



- iv. What are the differences of tracking ADC and successive approximation register (SAR) ADC when compared with the counter ADC?
- v. A 4 bit SAR ADC has an internal DAC with 0-8 V range. Write down the sequence the SAR would go through to convert a 2 V analogue input to a digital output.

6.

- i. The EPROM labeled 2716 has two kilobytes of memory. If the data bus of this chip is 8 bit, calculate the width of the address line.
- ii. Illustrate with the help of a diagram, how to construct a 32 kilobit ( $4096 \times 8$ ) memory using 2716 chips.
- iii. Discuss the tasks of (i) programme counter, (ii) A and B accumulators and (iii) flag registers of a typical microprocessor.
- iv. Explain how these registers help in the sequence of general operation of a microprocessor when run a programme.
- v. Write a simple assembly language programme to subtract 2 from 3 and draw a diagram to illustrate how this programme is stored in a memory starting from address  $10_{16}$ .

