



ANSWER ANY FIVE QUESTIONS.

Date 17.12.2016

Time: 9:30-12:30 hrs.

Q1.

(a) Using proper diagrams compare the ideal and practical diode characteristics.

(4 Marks)

(b) Consider the circuit diagram in Figure-Q1.

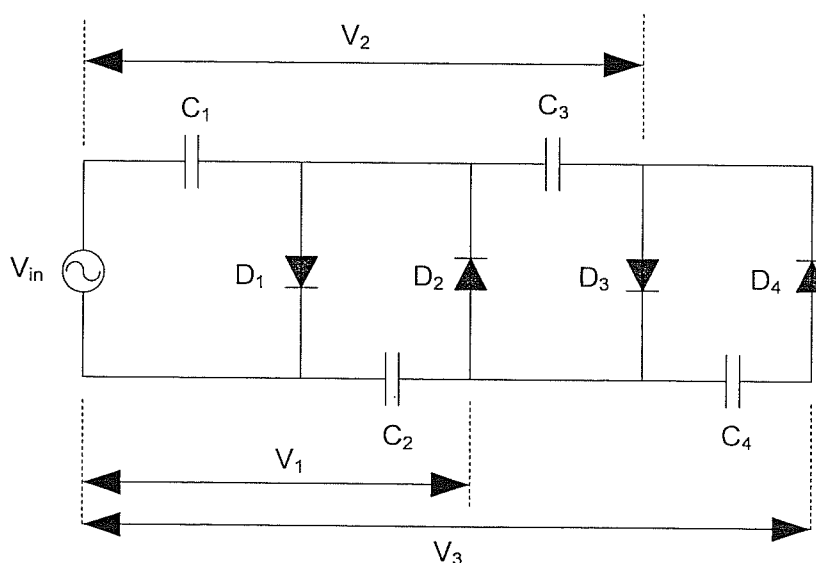


Figure-Q1

- Assuming ideal diode and capacitor behavior, explain the operation of the above circuit. (4 Marks)
- Hence draw the waveforms of V_1 , V_2 and V_3 for an input signal of $v_{in} = 10 \sin 20\pi t$. (6 Marks)
- Draw the waveforms of V_1 , V_2 and V_3 under non-ideal (practical) Si diode characteristics. (6 Marks)

- Q2. Let the transistor in the amplifier circuit in Figure-Q2 has the following parameters with the usual notation. $r_{be} = 1k\Omega$, $r_{bc} = 4M\Omega$, $r_{ce} = 80k\Omega$, $C_c = 3pF$, $C_e = 100pF$ and $g_m = 50mAV^{-1}$. Assume the effect of all the other unmentioned parameters to be negligible.

- (a) Draw the high frequency equivalent circuit for this amplifier circuit. (6Marks)
 (b) Using Miller's theorem, simplify the equivalent circuit model. (6Marks)
 (c) Hence, find the voltage gain of the same amplifier. (8Marks)

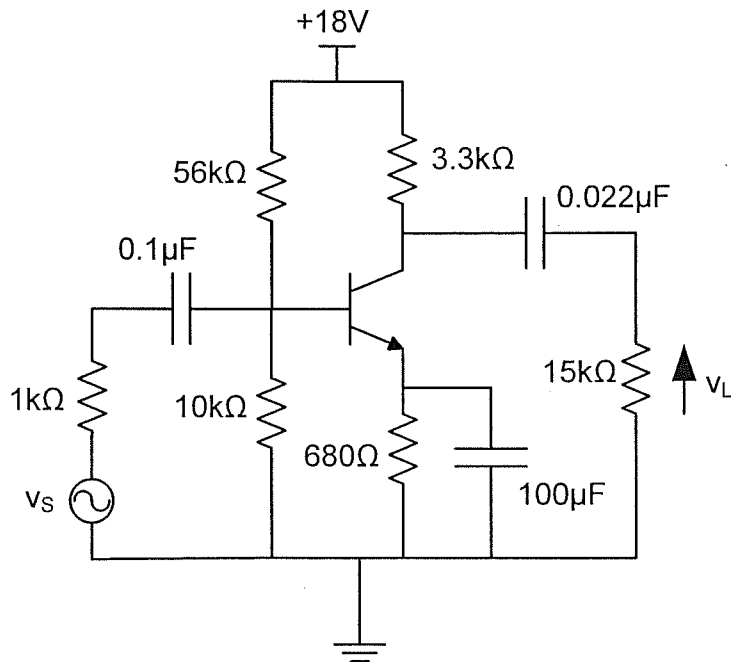


Figure-Q2

Q3.

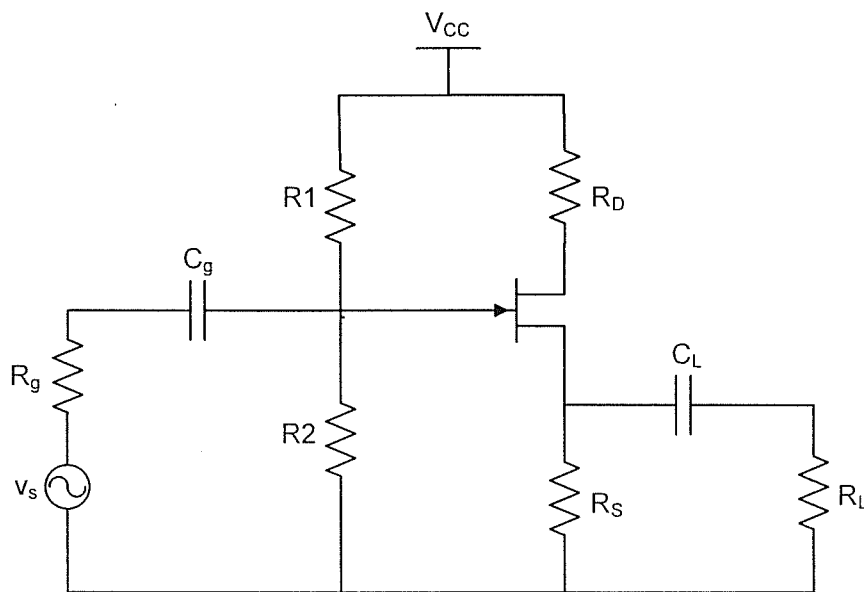


Figure -Q3

Consider the arrangement in the above Figure-Q3 circuit diagram.

- i. Using the symbols under the usual notation, draw the high frequency equivalent circuit diagram. **(6Marks)**
- ii. Find expressions for the voltage gain, input impedance and the output impedance. **(9Marks)**
- iii. Hence derive an expression for the low frequency voltage gain of the above amplifier. **(5Marks)**

Q4.

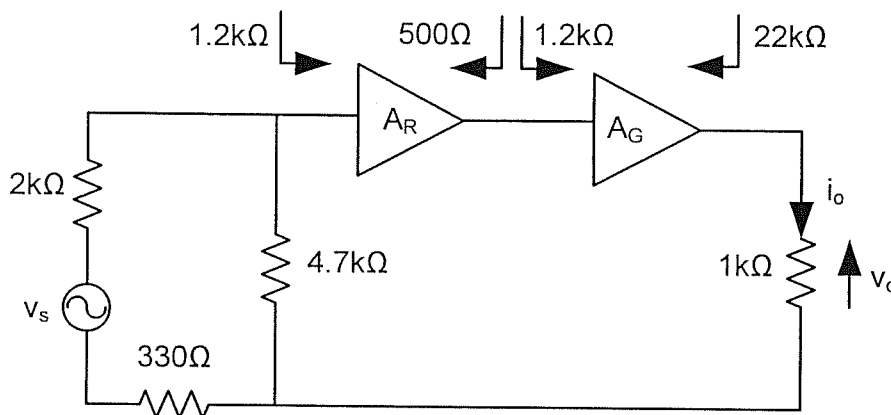


Figure-Q4

The circuit shown in the above Figure-Q4 has a transresistance amplifier and a transconductance amplifier with $A_R = -100 \text{ VA}^{-1}$ and $A_G = 50 \text{ AV}^{-1}$ respectively. The input and output impedances of the two amplifier stages are as shown.

- (a) Draw the open loop ac equivalent circuit. **(6Marks)**
- (b) Find the open loop gain and the feedback factor. **(8Marks)**
- (c) Hence find the closed loop current gain, input impedance and the output impedance. **(6Marks)**

Q5.

- (a) List three commonly used filter transfer functions and their characteristics. (4Marks)
- (b)

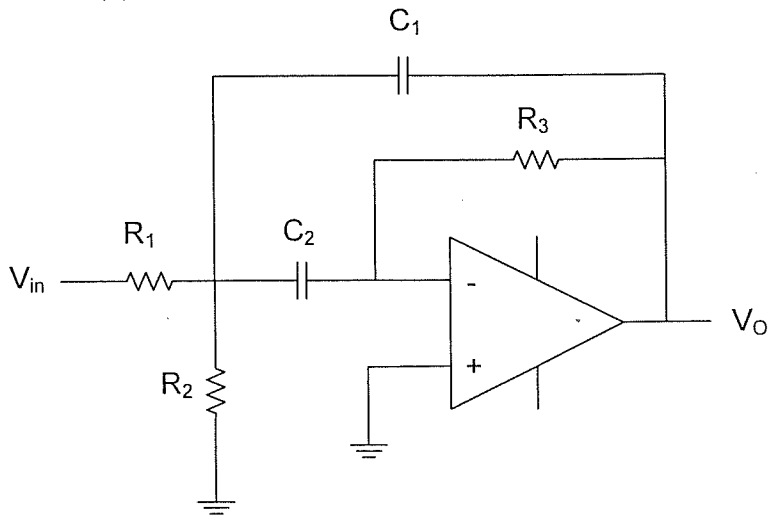


Figure Q5(a)

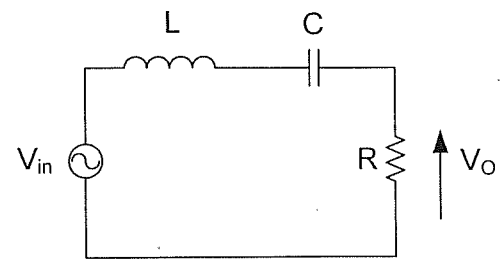


Figure Q5(b)

- i. Derive the transfer function for the circuit in Figure Q5(a). (8Marks)
- ii. Show that the filter effects are the same for both circuits. (4Marks)
- iii. Find the expressions for the bandwidths of the two filter circuits. (4Marks)

Q6.

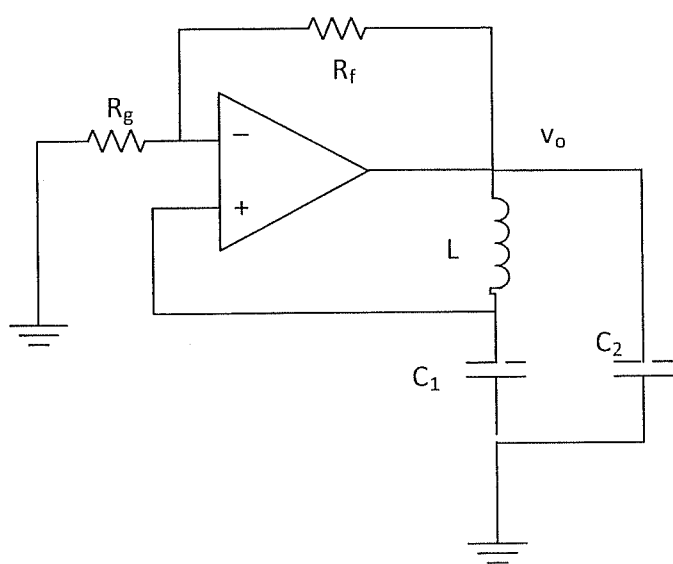


Figure Q6

- (a) Starting from the first principles, derive the Barkhausen criteria for oscillations to occur. (4 Marks)

- (b) Stating all your assumptions, derive an expression for the feedback factor for the circuit in Figure Q6. **(8 Marks)**
- (c) Derive an expression for the forward gain. **(4 Marks)**
- (d) Hence find the frequency of oscillation. **(4 Marks)**

Q7.

- (a) A weight measuring system should measure $500 - 2500\text{kg}$ with a resolution of at least 10kg . Sensitivity of the transducer employed is 5mVkg^{-1} . The output of the transducer is fed to an ADC. Calculate the minimum number of bits required at the ADC and the minimum possible resolution at the ADC input. **(6Marks)**
- (b) A basic level microprocessor control unit is to be designed according to the following specifications.
- Operations: Addition, logical AND, logical OR, bitwise inversion.
 - Operations to be performed by ALU on 4 bit data stored in A and B registers accordingly.
 - Results of the ALU operation to be stored in the 4 bit register C.
 - Current instruction (in binary for) is loaded to the instruction register (IR).
 - Depending on the current instruction (in binary form) required functional circuit inside the ALU is activated together with the registers.

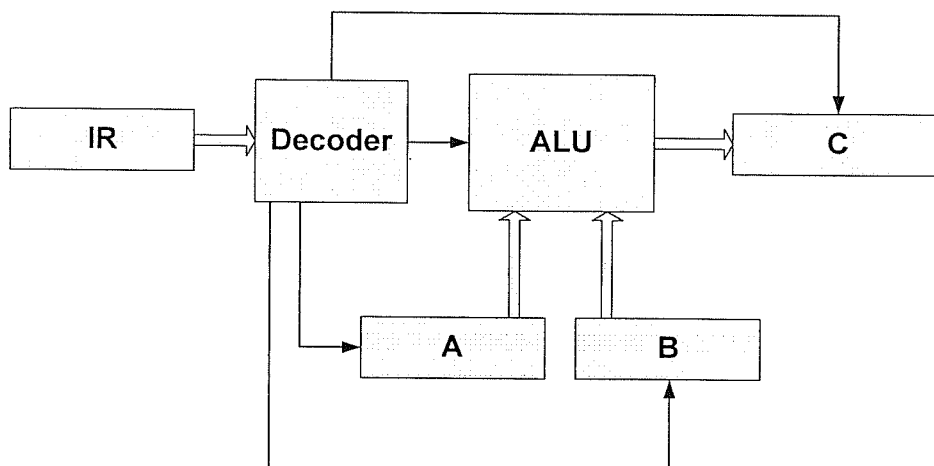


Figure Q7

- i. Select a suitable binary instruction set. **(2Marks)**
- ii. Design the combinational circuit in the decoder to activate the different circuit elements.
 - a. Draw the truth table. **(4Marks)**
 - b. Produce the simplified Boolean expressions. **(4Marks)**
 - c. Implement using an appropriate PLA. **(4Marks)**

Q8.

- (a) Design a synchronous sequential circuit to detect a 101 in a long series of bits.
- i. State the state table. **(2Marks)**
 - ii. Draw the state transition diagram. **(3Marks)**
 - iii. Produce the Boolean expressions. **(3Marks)**
 - iv. Draw the circuit with suitable logic gates. **(1Marks)**
- (b) Design a counter circuit which counts 1 to 7 in odd numbers only.
- i. How many flip flops are required to design this counter? **(1Marks)**
 - ii. Draw the state diagram for the counter. **(2Marks)**
 - iii. Draw the truth table and the state transition table. **(3Marks)**
 - iv. Simplify the functions using Karnaugh maps. **(3Marks)**
 - v. Design the circuit with required logic gates. **(2Marks)**