



Date: 16.05.2025

Time: 9.30 a.m. – 11.30 a.m.

**ANSWER ANY FOUR (04) QUESTIONS ONLY.**

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 \text{N}^{-1} \text{m}^{-2} \quad \mu_0 = 4\pi \times 10^{-7} \text{ WbA}^{-1} \text{m}^{-1} \quad g = 10 \text{ N kg}^{-1}$$

1.

- i. State the Coulomb's law used in electrostatics.
- ii. Two charges of  $+5 \mu\text{C}$  and  $+20 \mu\text{C}$  are placed at a distance of 24 cm apart. A third charge Q is placed at the middle point of the line joining them. What would be the magnitude and the nature of the charge Q so that the net force on  $+5 \mu\text{C}$  is zero?
- iii. Calculate the Electric field intensity and the direction on the charge Q
- iv. Write down the relationship between the Electric field intensity and the electrostatic potential
- v. Find the Electrostatic potential 5 cm from the charge Q perpendicular to the line joining the  $+5 \mu\text{C}$  and  $+20 \mu\text{C}$  charges.

2.

- i. Using the Biot-Savart law, explain qualitatively how the magnetic field at a point P near a wire carrying a current depends on the distance r from the wire. What happens to the magnetic field if the current is doubled?
- ii. A conductor carrying a current is placed in a magnetic field perpendicular to the current. Using Fleming's left-hand rule, explain how to predict the direction of the force on the conductor. Give one practical example where this rule applies.
- iii. Calculate the magnitude of the magnetic field at a point 5 cm away from a long straight conducting wire carrying a current of 10 A.
- iv. Another long straight conducting wire carrying 5 A is placed to the right side, parallel to the above-mentioned wire at a distance of 5 cm. Calculate the force per unit length and the direction of the force acting on the wire.
- v. State Faraday's law of electromagnetic induction. Explain conceptually why the induced electromotive force (EMF) increases when the rate of change of magnetic flux increases.
- vi. A circular coil with 50 turns and radius 10 cm is placed in a uniform magnetic field perpendicular to its plane. If the magnetic field changes uniformly from 0.2 T to 0 T in 0.1 s, calculate the magnitude of the induced EMF in the coil.

3.

- i. Write down an expression for the resistance of a wire in terms of length and the cross-sectional area of the wire. Describe the symbols in your written expression.
- ii. A resistor is made by connecting two wires of the same material in series. The radii of the two wires are 1 mm and 3 mm, while their lengths are 3 cm and 5 cm respectively. a battery of 16 V with negligible internal resistance is connected serially across the resistor. Find the ratio of the resistance of the two wires.
- iii. Calculate the potential difference across the short wire
- iv. Show that the ratio of the power dissipation of the two wires is the same as the ratio of the resistance of the two wires.
- v. Hence show the shorter wire, delivers more power than the other.

4.

- i. State the Gauss theorem.
- ii. Using the Gauss theorem, derive an expression for the electric field strength for an infinite conducting sheet of charge density  $\sigma$ .
- iii. Show that the capacitance ( $C$ ) of a parallel plate capacitor is  $C = \frac{A\epsilon_0}{d}$  where  $A$ ,  $\epsilon_0$  and  $d$  are the area of the plates, permittivity of the air and the separation of the plates respectively.
- iv. For the above-mentioned capacitor dielectric medium of  $k$  is inserted into half of the area of the plate as shown in figure 01. Find the new capacitance ( $C_1$ ) of the capacitor.

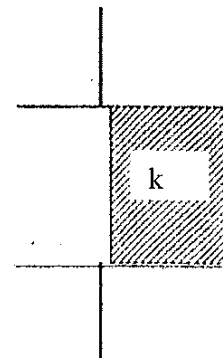


figure 01

- v. In the given circuit shown in the figure 02 each of the capacitors  $C_1, C_2, C_3$  and  $C_4$  is equal to  $1 \mu\text{F}$ . Find the effective capacitance across the battery.

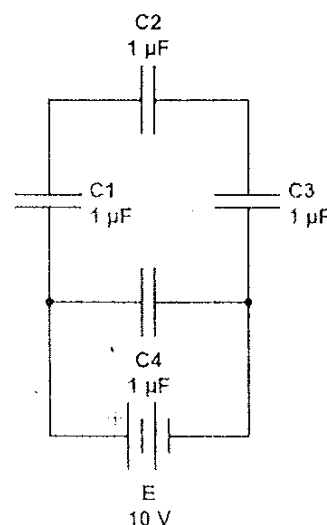


figure 02

5.

Consider the circuit shown in Figure 03, where a battery with an electromotive force (emf)  $E$  is connected in series to a resistor  $R$  and a capacitor  $C$ , through a switch.

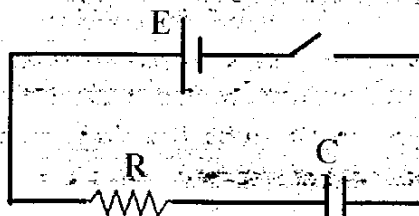


Figure 03

The charge  $q$  stored in the capacitor at time  $t$  is given by the following equation

$$q = EC \left( 1 - e^{-t/CR} \right)$$

Determine the maximum (total) charge  $q$  that can be stored on the capacitor after a long time.

Derive an expression for the current  $I(t)$  flowing in the circuit at time  $t$ , using the above expression for  $q$ .

Sketch a graph showing how the current  $I$  changes with time  $t$ .

From the graph, determine the maximum current  $I_{\text{max}}$  in the circuit. What is the value of this maximum current?

Show that the time taken ( $t_{1/2}$ ) for the current to drop to half of its initial value is given by

$$t_{1/2} = RC \ln 2$$

vi. In the above circuit  $E$ ,  $R$  and  $C$  values are 5 V, 2 M $\Omega$  and 4  $\mu$ F respectively. Calculate the Time Constant of the circuit.

6.

i. Write down the expressions for:


- Capacitive reactance  $X_C$
- Inductive reactance  $X_L$

Also, clearly define the symbols used in each expression.

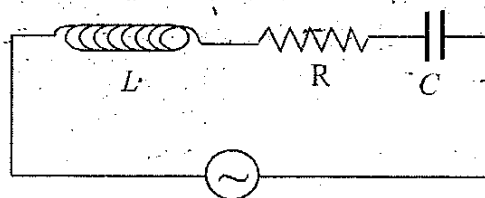ii. Draw the phasor diagrams for the following components, showing the relationship between voltage and current for:

- A resistor
- A pure capacitor
- A pure inductor

Consider the L C R series circuit with values of 0.2 H, 50  $\mu$ F and 100  $\Omega$  respectively, shown in Figure 04, where the current in the circuit is given by  $i = i_0 \sin \omega t$



$$i = i_0 \sin \omega t$$

Figure 04

- Draw the phasor diagram for this circuit when  $X_L > X_C$ .
- Derive an expression for the total impedance  $Z$  of the circuit, using either the phasor diagram or another suitable method.
- Determine an expression for the phase angle ( $\phi$ ) between the supply voltage and the current.
- Show that the resonance frequency  $f$  of the circuit is given by  $f = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$
- Calculate the resonance frequency ( $f$ ) of the circuit given in figure 4.

\*\*\*\*\*