



Date: 26.03.2024

Time: 1.30 p.m. – 3.30 p.m.

ANSWER ANY FOUR (04) QUESTIONS ONLY.

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 \text{N}^{-1} \text{m}^{-2}$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ WbA}^{-1} \text{m}^{-1} \quad g = 10 \text{ N kg}^{-1}$$

01. (a)

- i. State the Coulomb's law for the forces between two charges.
- ii. Figure 01 shows the positive charge of A with $4 \times 10^{-8} \text{ C}$ and the negative charge of B with $25 \times 10^{-8} \text{ C}$. In line with another P positive charge of $1 \times 10^{-8} \text{ C}$ distances between the charges are shown in Figure 01. Calculate the force on the charge P.

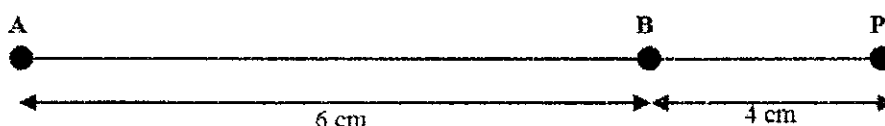


Figure 01

- iii. Now Charge P has been removed, find the neutral point.
- iv. Draw the diagram of electric field lines for A and B charges.

(b)

- i. State the Gauss' theorem.
- ii. Using Gauss's law, determine the electric field intensity at a distance r away from an infinite line of charge with a linear charge density λ .
- iii. Determine the linear charge density (λ) of a wire with a length of 2 m and given $10 \mu\text{C}$.
- iv. Find the electric field intensity 20 cm away from the wire.

02. (a)

- i. Write down an expression for the charge (Q) stored in a capacitor (C) connected to potential V.
- ii. Draw the variation for the charge (Q) and potential (V). Hence derive an expression for the energy stored in the capacitor.
- iii. The total energy stored in the capacitors is 10 J when three (03) identical capacitors are connected in series to a voltage. What is the total energy stored in the capacitors when the same capacitors are connected in parallel to the same potential?

(b)

Briefly describe the followings,

- i. Electronic polarizability
- ii. Ionic polarizability
- iii. Dipolar polarizability

Figure 02 shows that the parallel plate capacitor is inserted with a dielectric medium.

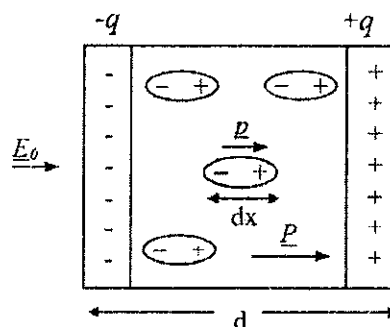


Figure 02

- iv. Show that the dipole moment per unit volume (P) is given by surface charge density σ_p .
- v. When a dielectric slab of thickness 2 cm and area 20 cm² is placed in an electric field, a 50 μC charge is induced on the surface. Calculate the dipole moment of the induced charge and magnitude of the polarization vector.

03. (a)

- i. State Faraday's law of electromagnetic induction. Hence derive an expression for induced e.m.f of a moving conductor in a magnetic field. Describe the symbols in your derived expression.
- ii. Figure 03 shows an inductor and resistor of 10 Ω are connected in series. Magnetic flux (ψ) varies with time t in the inductor according to the following expression.

$$\psi = 5t + 2$$

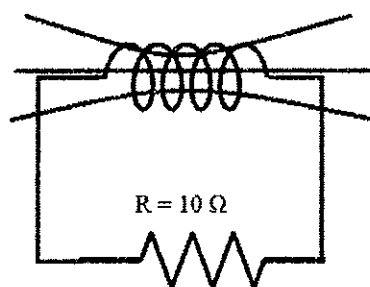


Figure 03


- iii. Determine the induced e.m.f. across the inductor.
- iv. Determine the current passing through the 10 Ω resistor.

(b) Briefly explain the basic design of the following with a diagram.

- i. Suspended moving coil Galvanometer (Ballistic Galvanometer)
- ii. AC Generator

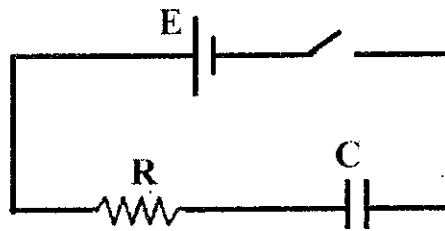04.

The circuit diagram 01 shows a battery with e.m.f. of E connected in series to a resistor R and a capacitor C through a switch.



circuit diagram 01


The charge (q) stored in the capacitor after time t is given by the following expression.

$$q = EC \left(1 - e^{-t/CR} \right)$$

- i. Determine the total charge (q_0) stored in the capacitor.
- ii. Derive an expression for the current after time t passing in the circuit using the above expression.
- iii. Sketch the variation of the current with the time.
- iv. Explain how you would obtain the maximum current passing in the circuit. What would be the maximum current?
- v. Show that the time taken ($t_{1/2}$) to decrease the current to half of its initial current is $t_{1/2} = RC \ln 2$
- vi. In the previous circuit E , R and C values are 5 V, 2 M Ω and 4 μ F respectively. Calculate the Time Constant of the circuit.
- vii. Calculate the time taken to charge the capacitor to half of its maximum charge.

05. (a)

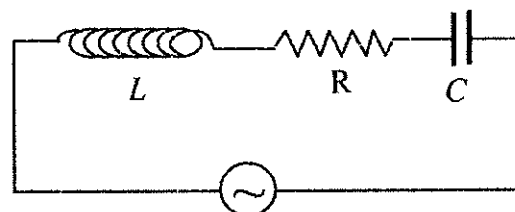- i. Write down the expressions for capacitive reactance (X_C) and Inductive reactance (X_L). Name the symbols used in the expressions.
- ii. Draw the phasor diagrams for the resistor, pure capacitor and pure inductor separately.
- iii. L R C series circuit is shown in the following figure 04. current $i = i_0 \sin \omega t$ is passing through the circuit.



$$i = i_0 \sin \omega t$$

Figure 04

- iv. Draw the phasor diagram for the above circuit for $X_L > X_C$
- v. Derive an expression for the total impedance of the circuit using the phasor diagram or any other method.
- vi. Determine the phase angle (ϕ).
- vii. Show that the resonance frequency of the circuit is given by $f = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$.

06. (a)

- i. State the four experiments that can be done using the potentiometer.
- ii. State the advantage of conducting experiments using the potentiometer.
- iii. A potentiometer wire of length 100 cm has a resistance of $10\ \Omega$ connected with a 2 V driver cell of negligible resistance. Briefly explain how you balance 10 mV in 40 cm length.

(b)

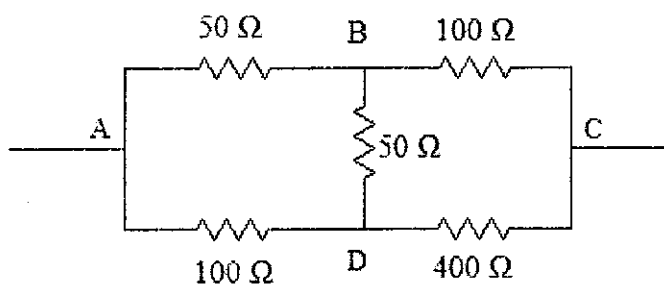


Figure 05

- i. Five (05) Resistors are connected in the circuit given in Figure 05. A 10 V Battery is connected across A and C. A voltmeter with an internal resistance of $400\ \Omega$ is connected across a $400\ \Omega$ Resistor. What is the reading of the voltmeter?
- When the above voltmeter is connected to the circuit,
- ii. Calculate the current in each resistor.
 - iii. Determine the equivalent resistance of the circuit.
