

The Open University of Sri Lanka

Faculty of Engineering Technology



Study Programme	: Bachelor of Technology (Engineering)
Name of the Examination	: Final Examination
Course Code and Title	: MEX5270 Power electronics and motor drives
Academic Year	: 2012/2013
Date	: 10 th August 2013
Time	: 9.30am – 12.30pm
Duration	: 3 hours

General instructions

1. Read all instructions carefully before answering the questions.
2. This question paper consists of 8 questions. All questions carry equal marks.
3. Answer any 5 questions only.

Q1.

- a. Discuss *Conduction loss* and *Switching loss* of real power semiconductor switches using appropriate diagrams.
- b. Briefly describe *four quadrant dc drives* and their functionalities.
- c. Discuss the principle of regenerative braking of dc – dc converter fed dc motor drives.
- d. A full bridge inverter produces a 200V square wave at 50Hz across a series R-L load where $R=10\ \Omega$ and $L=50\text{mH}$. The relevant waveforms are shown in Figure Q1. Find the following
 - i. An expression of load current in positive half cycle and negative half cycle
 - ii. Peak value of the load current

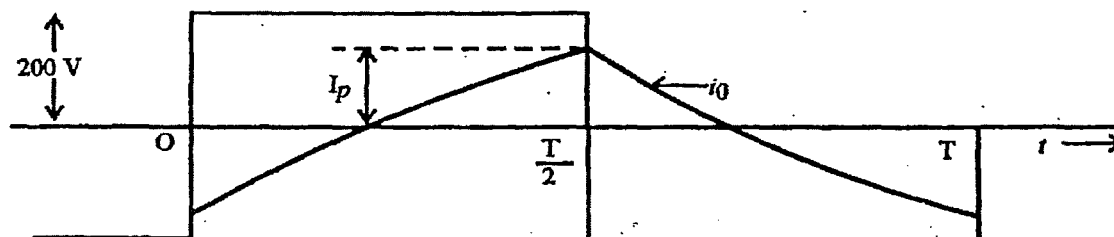


Figure Q1

Q2. A transistor with a snubber circuit experiences a linear fall in current from 50A to 0A in $1.5\mu\text{s}$ at turn-off. At turn-on the transistor experiences a linear fall in voltage from its off state value of 200V to 0V in $1.2\mu\text{s}$.

Determine the following if the voltage rise time is delayed to $0.5\mu\text{s}$, $1.0\mu\text{s}$ and $1.5\mu\text{s}$.

- Value of the capacitor
- Transistor switching loss during turn-off
- Capacitor stored energy
- Total loss

Observing the results you obtained, suggest a suitable value for the snubber resistance, if $t_{\text{on}(\text{min})} = 10\mu\text{s}$. Give reasons for your answer.

Q3.

- a) The turn ON and the turn OFF switching transition times for the power semiconductor switch S in Figure Q3(a) are respectively $t_{\text{sw}(\text{on})}$ and $t_{\text{sw}(\text{off})}$. Assume linear variation of current and voltage during the switching transitions. The ON state voltage drop across the switch is V_D .

Show that the average switching power loss across the switch is

$$P_{\text{sw}} = \left(\frac{VI}{6} + \frac{V_D I}{3} \right) (t_{\text{sw}(\text{on})} + t_{\text{sw}(\text{off})}) f_s$$

Where V is the off state voltage across the switch, I is the ON state current through the switch and f_s is the switching frequency.

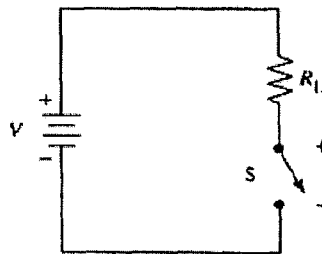


Figure Q3(a)

- b) Consider the single phase controlled half wave bridge rectifier shown in Figure Q3(b). The firing delay angle is 45° . Draw the waveforms of the half wave bridge rectifier for the following clearly labeling the graphs.

- Supply voltage (v_s)
- Output voltage (v_o)
- Output current (i)
- Voltage across the SCR (v_{SCR})

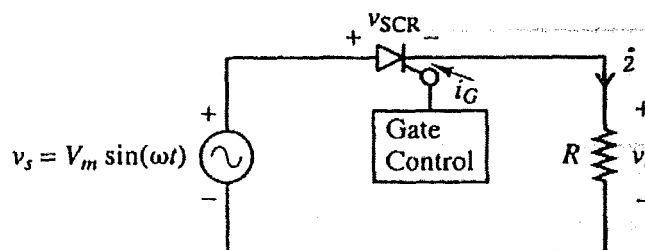


Figure Q3(b)

Q4.

- Compare and contrast controlled and uncontrolled rectification.
- The single phase full bridge rectifier shown below has an AC source with $V_m=100V$ at 60Hz and a series R-L load with $R_L=10\Omega$ and $L=10mH$.

Determine

- the average current in the load
- the power absorbed by the load
- the average and rms current in the diode.

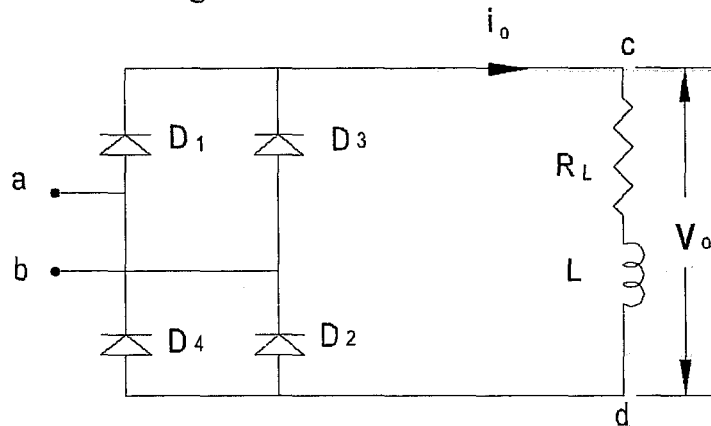


Figure Q4

Q5. The single phase AC voltage controller of Figure Q5(a) has a $120V_{rms}$ 60Hz source and a load resistance of 15Ω . The delay angle α is 90° .

- Draw the wave forms of v_s , i_o , v_o and v_{sw} (the voltage across the SCRs)

Note:- Use three graphs. v_s and i_o on one graph and others on separate graphs.

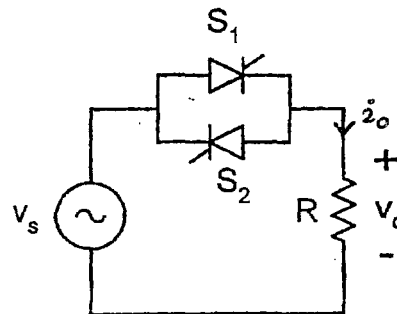


Figure Q5(a)

- Determine the following

- the rms load voltage
- the power absorbed by the load
- the power factor
- the rms and average currents in the SCRs

NOTE:- Use the graph given in Figure Q5(b) as applicable

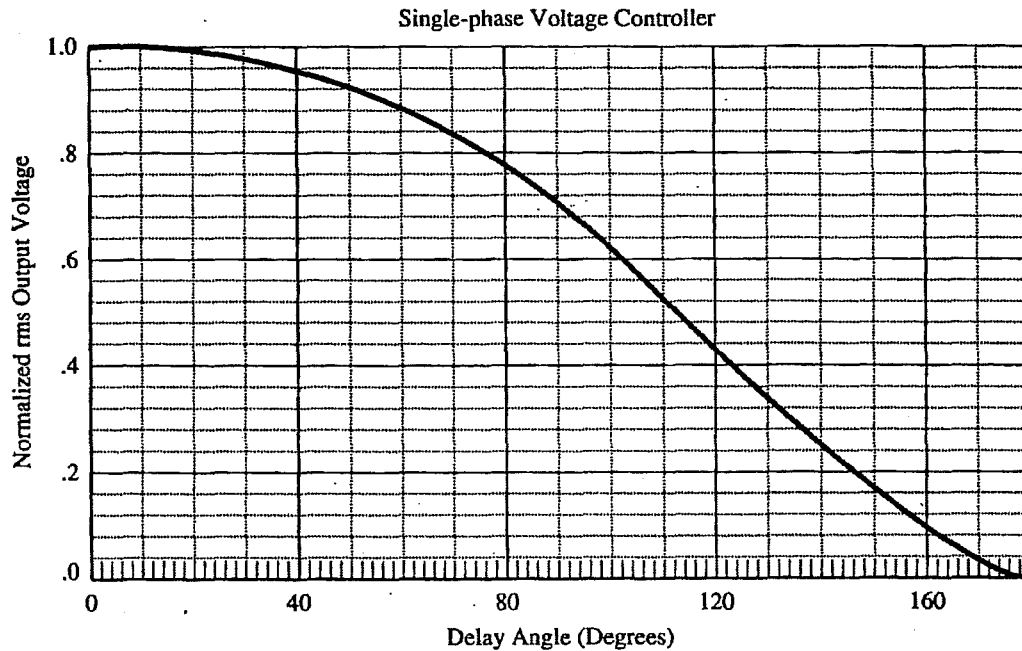


Figure Q5(b) The Normalized rms load voltage versus delay angle for a single phase ac voltage controller with a resistive load

- Q6.** A buck converter has an input voltage, $V_d=15V$. The required average output voltage $V_o = 5V$ and the peak to peak output ripple voltage is $10mV$. The switching frequency is $20KHz$. The peak to peak ripple current of the inductor is limited to $1A$. Determine
- the duty cycle D
 - the filter inductor L
 - the filter capacitor C

- Q7.** The buck boost converter as shown in Figure Q7 has $V_d= 24V$, $V_o=36V$ and a load resistance of 10Ω . The switching frequency of the converter is $60kHz$.
- Determine the inductance value such that the minimum inductor current is 40% of its average value.
 - Determine the capacitance required to limit the output voltage ripple to 0.5%.

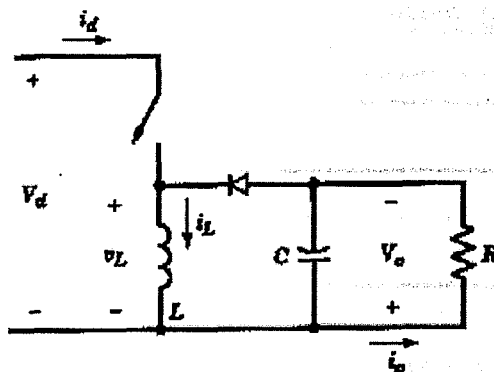


Figure Q7

- Q8.** A full bridge inverter is used to produce a 60Hz voltage across a series R-L load using bipolar PWM. The dc input to the bridge is 100V, the amplitude modulation ratio m_a is 0.8, and the frequency modulation ratio m_f is 21. The load has a resistance $R = 10\Omega$ and inductance $L = 20\text{mH}$.

Determine the following

- The amplitude of the 60Hz component of the output voltage and load current
- The power absorbed by the load resistance

NOTE:- Use the values given in Table Q8 as applicable

	$M_a = 1$	0.9	0.8	0.7	0.6	0.5	0.4	0.3	0.2	0.1
$n = 1$	1.00	0.90	0.80	0.70	0.60	0.50	0.40	0.30	0.20	0.10
$n = m_f$	0.60	0.71	0.82	0.92	1.01	1.08	1.15	1.20	1.24	1.27
$n = m_f \pm 1$	0.32	0.27	0.22	0.17	0.13	0.09	0.06	0.03	0.02	0.00

Table Q8 Normalized Fourier coefficients $\frac{V_n}{V_{dc}}$ for bipolar PWM

END