

Time: 1330 – 1630 hrs.

Date: 2006-03-25

Answer any *FIVE* questions

1.

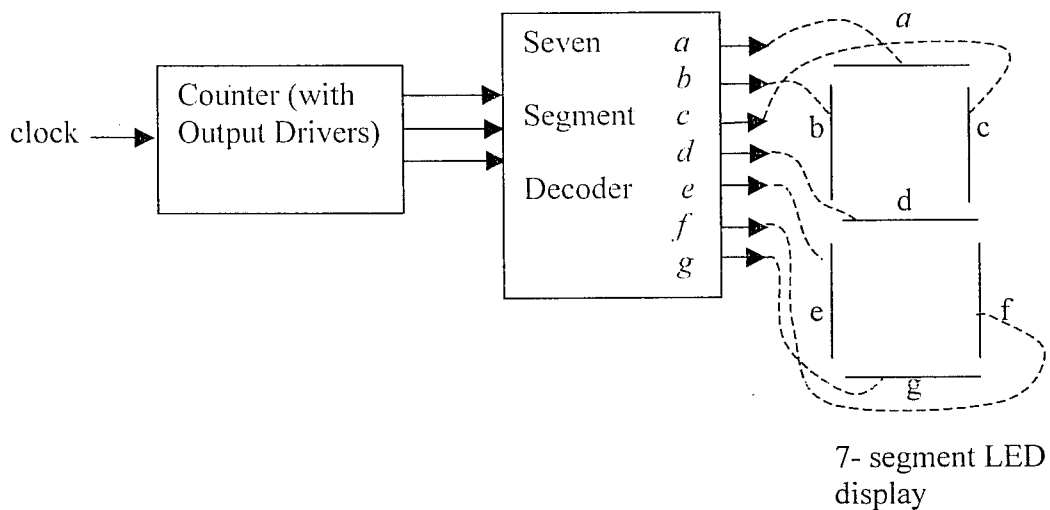


Fig.1

Fig.1 shows a circuit consisting of a binary counter, a decoder and a 7-segment LED display. The counter output is fed to a *binary to seven-segment decoder* circuit which decodes the binary number into corresponding 7-segments. The outputs *a, b, c, d, e, f* and *g* of the 7-segment decoder are connected to the corresponding segments of the 7-segment display.

- What is the maximum possible count of the counter?
- Design a *binary to seven segment decoder* circuit.

2.

Simplify the following functions using Quine McClusky method.

(a) $f(x) = \sum m(0, 1, 2, 3, 4, 5, 6, 7)$

(b) $f(x) = \sum m(6, 7, 12, 13, 14, 15)$

(c) $f(x) = \sum m(0, 5, 10, 15)$

3.

(a) What is understood by Consensus of two terms minterms t_1 and t_2 ?

(b) Simplify the following functions using *Iterative Consensus method*.

(i) $f(x) = \sum m(0, 2, 8, 10)$

(ii) $f(x) = \sum m(0, 1, 4, 5)$

(iii) $f(x) = \sum m(2, 8, 13)$

(c) Compare the advantages and disadvantages of using Karnaugh map over Quine Mc Clusky method.

4.

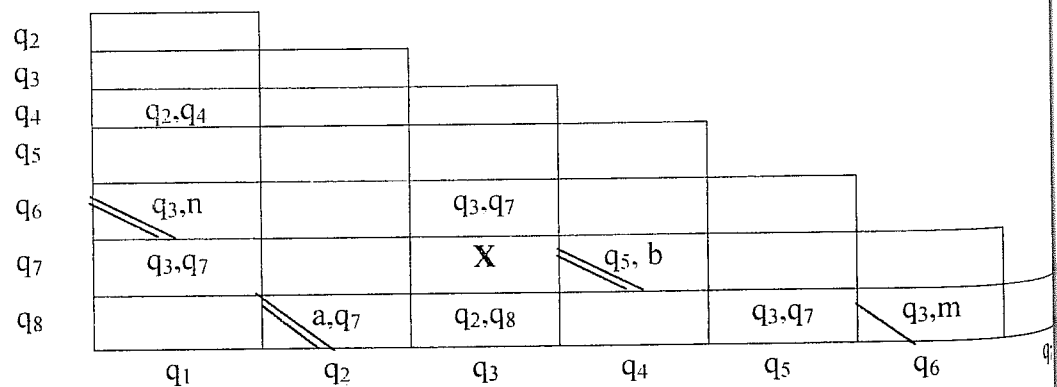


Fig 4

An Implication table is shown in Fig.4.

- (a) Find the values of a, b, m and n
- (b) Determine maximal compatibles.

5.

- (a) Describe the construction of a 2-input Threshold gate circuit which uses only passive components. Give the circuit diagram of it.
- (b) Implement using minimum number of Threshold logic gates:
 - (i) $f(x) = \sum m (4, 5, 7, 13)$
 - (ii) $f(x) = \sum m (2, 6, 14, 15)$
 - (iii) $f(x) = \sum m (6, 7, 13, 14, 15)$

6.

- (a) What are the factors that affect the highest operating frequency of a logic gate?
- (b) What value should the *row multiplicity / column multiplicity* of a Partition map of $f(x)$ take so that the Partition map can be converted into a reduced Partition map?
- (c) Check whether the following functions are totally symmetric:
 - (i) $f(x) = \sum m (0, 1, 2, 4, 8, 15)$
 - (ii) $f(x) = \sum m (1, 3, 4, 6, 8, 15)$

7.

- (a) What is understood by 2-distinguishable state?

(b)

Present state ($y_1 y_2$)	Next State (Y_1, Y_2) for Input (x)	
	$x = 0$	$x = 1$
$q_1 = 00$	00	11
$q_2 = 01$	11	00
$q_3 = 11$	10	11
$q_4 = 10$	11	00

Fig.7

Fig.7 shows a *state transition table* for a certain state machine.

Design the state machine using RS flip-flops.

8.

A continuous binary serial bit stream is fed to a *data logger*. The data logger searches for *four* consecutive '1's in the bit stream. If it detects *four* consecutive '1's then the device gives out an alarm.

- (i) Draw a state diagram for the above process. How many states are there in the state machine?
- (ii) How do you assign binary numbers to different states? What criterion should be adopted when assigning numbers to adjacent states?
- (iii) Draw a *state transition table* for the state machine.