



The Open University of Sri Lanka
Department of Electrical and Computer Engineering
Final Examination -2011
ECX4230.- Fault Diagnosis in Electronic Circuits

Date:17.03.2012

Time: 1400 -1700 hrs

Answer any five questions.

- 1) A two stage amplifier is shown in figure 1. Test points are marked as 1,2,3,4 and 5 in the circuit.

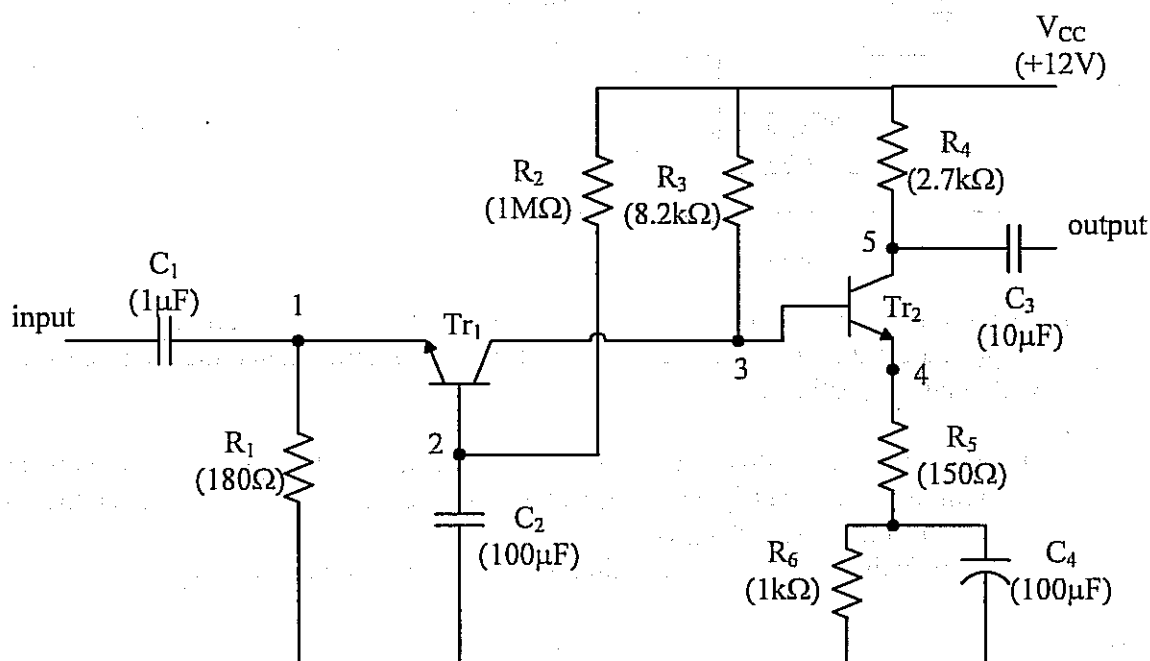


Figure 1

- a) Current gain of Tr_1 and Tr_2 transistors are 100 and 75 respectively, calculate the test point voltages at no signal. Do not assume for maximum output swing.
- b) Calculate the amplitude of the signal at the output, if the voltage of the signal at test point 3 is 0.23V peak to peak. (Assume the capacitors offers negligible reactance at the signal frequency)
- c) Identify the faulty component/s with fault type giving reasons.

Case	T.P 1	T.P 2	T.P 3	T.P 4	T.P 5	output
A	0.2	0.8	2.82	0	12.00	No output
B	0.2	0.8	2.7	2.19	11.46	Positive clipped
C	0.2	0.8	1.036	0.436	0.630	No output

- 2) Figure 2 shows a circuit employing two thyristors with a trigger module. The trigger module triggers the two thyristors sequentially.

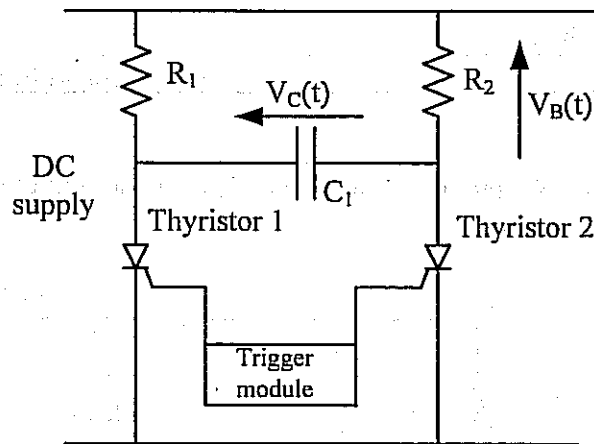


Figure 2

- Explain the operation of this circuit and give one possible application.
 - Suggest a circuit which can be used as the trigger module, sketch the complete circuit with your suggestions.
 - If two identical bulbs B_1 and B_2 are used to replace R_1 and R_2 respectively, and if both thyristors are triggered sequentially at same trigger voltages, sketch the voltage waveforms $V_C(t)$ and $V_B(t)$.
 - Identify the fault/s with reasoning, if the B_1 bulb is on and B_2 is off.
- 3)
- An amplifier of open loop A_0 is supplied with positive feedback. If the feedback ratio is β , find an expression for the overall gain.
 - What will happen when $\beta A_0 = 1$?
 - The circuit shown in figure 3 is a blocking oscillator. Test points are marked as 1,2,3 and 4 in the circuit.

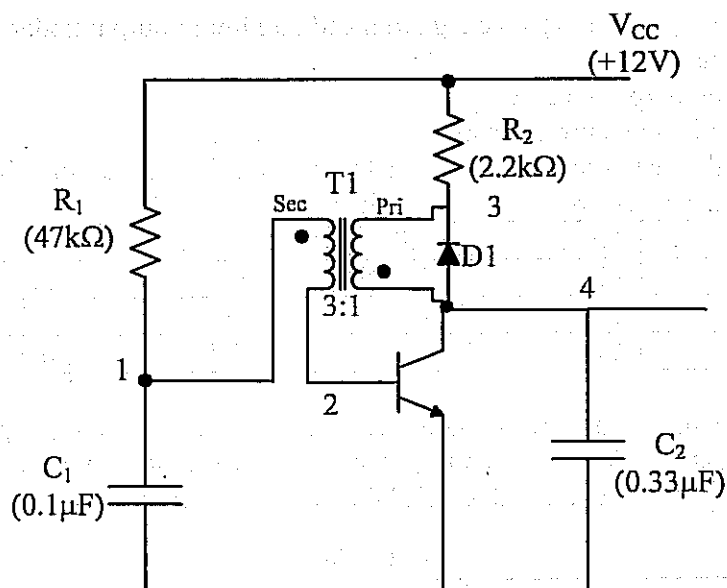


Figure 3

- Explain the operation and, sketch the waveforms at the output.
- What is the function of D_1 ?
- State the faulty component/s and the fault type with reasons for the following.

Fault	T.P 1	T.P 2	T.P 3	T.P 4	Symptom
A	0	0	12	12	Oscillator fails
B	0.7	0.7	0.1	0.1	Oscillator fails
C	9.7	0	12	12	Oscillator fails

- A DC regulator circuit is shown in figure 4. The Tr_2 has a high current gain and the Tr_1 has following specifications. Test points are marked as 1,2,3,4 and 5 in the circuit.
Current gain – 25, Minimum voltage across collector and emitter – 1.5V, Maximum power dissipation – 3W.

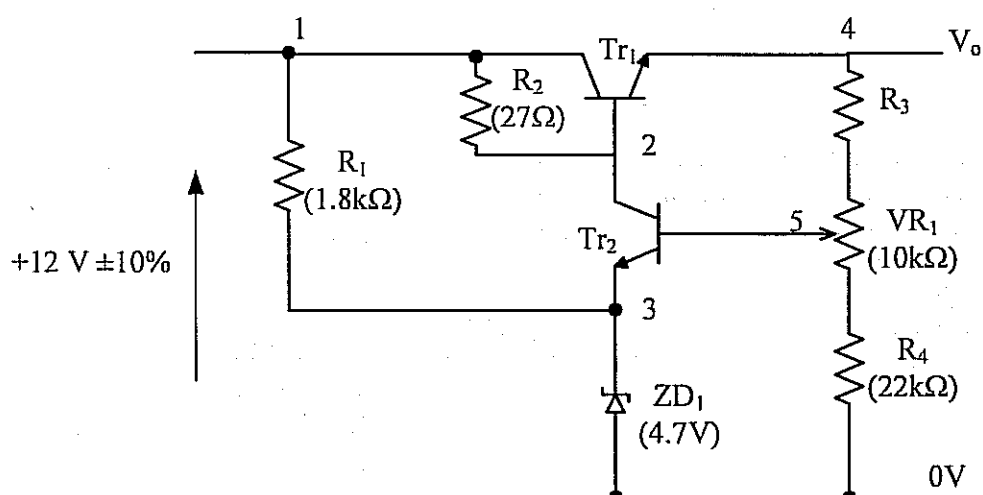


Figure 4

- Find a suitable value for R_3 resistor to give a guaranteed maximum output under the specified input conditions.
- Calculate the range of the output voltage.
- What is the maximum safe load current ensuring safe operation?
- Following table shows the test point voltage under faulty condition. Determine the faulty component/s giving reasons. Assume V_{R_1} is set to its maximum.

Case	T.P 1	T.P 2	T.P 3	T.P 4	T.P 5
A	12	11	4.7	0	5.3
B	12	0	4.7	0	5.3
C	12	6.8	0	5.4	0.6

- 5) A transistor amplifier is shown in figure 5. The Drain current of the transistor Tr_1 is given by $I_D = 0.2(V_{GS} - V_P)$, where I_D is in mA, V_{GS} in Volts and $V_P = -4V$. Current gain of the Tr_2 transistor is very high. Test points are marked as 1,2,3,4 and 5 in the circuit.

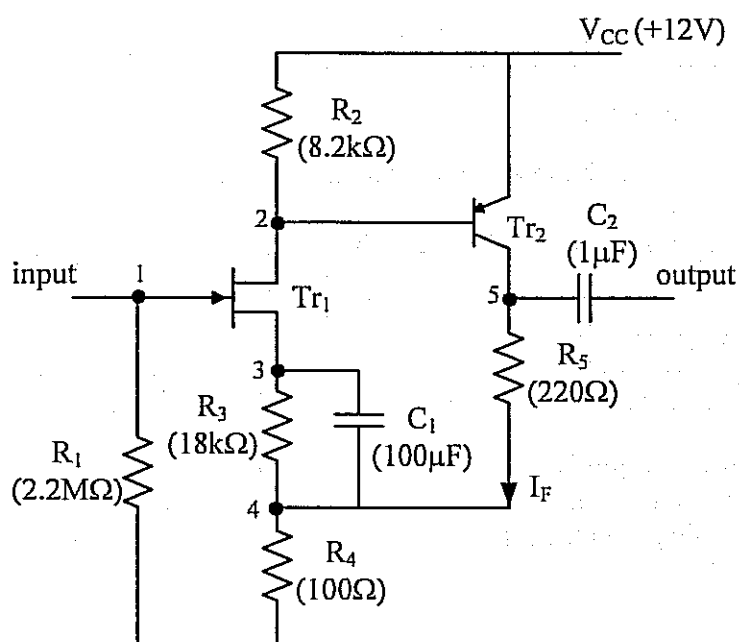


Figure 5

- Calculate the current I_F and then find the voltages at Test points when no signal is applied. Do not assume maximum swing at the output.
- What is the phase relationship between input and the output?
- Calculate the test point voltages.
- State the faulty component/s and the fault type with reasons for the following

Fault	T.P 1	T.P 2	T.P 3	T.P 4	T.P 5	Symptom
A	0	11.9	3.3	2	0	No output
B	0	11.4	3	0.6	7.4	Very low gain
C	0	11.4	0	0	0.1	No output

- 6) Consider the circuit shown in figure 6. A narrow width pulse train of 250 Hz frequency and +2V height is applied to the input. Test points are marked as 1,2,3 and 4 in the circuit.

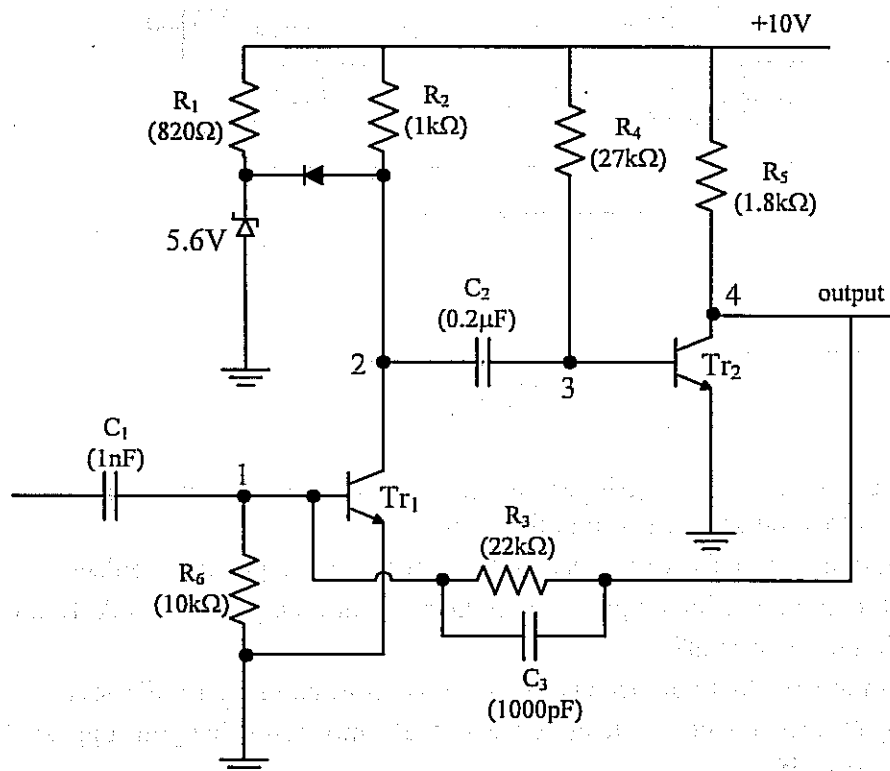


Figure 6

- Draw the waveforms at each test point to a common time scale with the input
- Calculate the parameters of the output waveform.
- Calculate the voltages at test points when no signal is applied.
- The output is not available under the following fault conditions. Find the faulty component/s and the fault type giving reasons for the following

Fault	T.P 1	T.P 2	T.P 3	T.P 4
A	0.2	6.2	0.6	0.2
B	0.2	0.6	0.6	0.2
C	0.6	0.2	0.6	10

7) Consider the logic circuit shown in Figure-Q7.

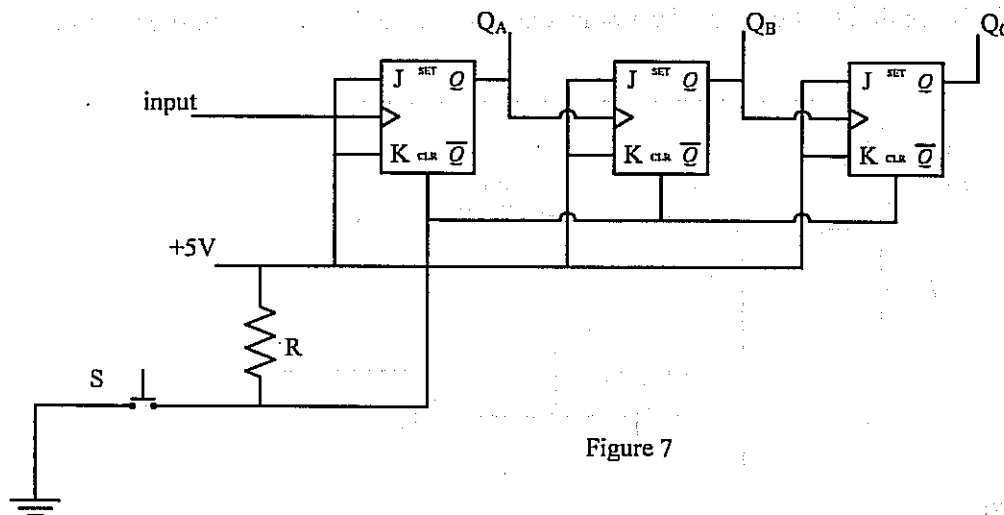


Figure 7

The JK flip-flops are +ve edge trigger (triggers on the +ve edge of the clock) type.

After pressing S, clock pulses are given to the input.

- Draw the timing diagram to show Q_A , Q_B , and Q_C for the first eight clock pulses.
- Hence tabulate the number of clock pulses with the relevant binary values of A, B, and C.
- Write the function of the circuit?
- What are the components that you need to display this information in a SSD (Seven Segment Display)? Draw the complete circuit with the components that you suggested
- Explain the operation, if
 - R is open,
 - Second JK flip flop is faulty

8)

- What are the main sections of a tuner in a TV receiver? Explain the function of each section.
 - In a defective TV receiver only the sound signal is received. Explain what sections are likely to be faulty and how you are going to identify the faulty section.
- Compare the R.F and A.F amplifiers in radio receiver.
 - Draw the block diagram of a superheterodyne receiver.
 - A defective radio receiver gives a distorted audio. If an oscilloscope is given to you explain how you find the faulty section.