



Date:30.08.2014

Time: 0930 -1230 hrs

Answer any five questions.

1. A two stage transistor amplifier circuit is shown in figure1. Circuit consists of two Si transistors. Tr1 has high current gain. The current gain of Tr2 is 40.

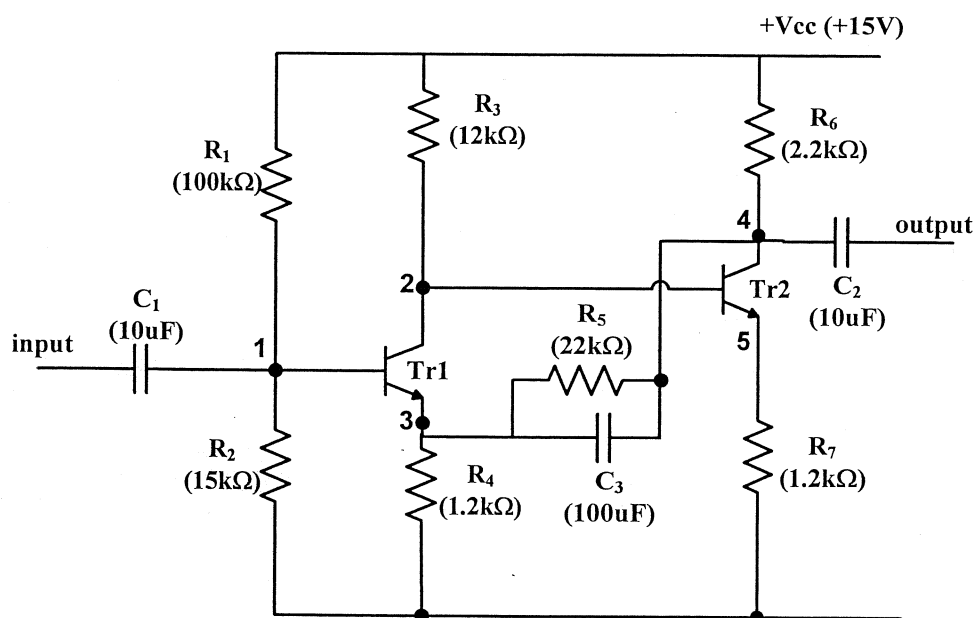


Figure 1

- Calculate the current  $I_x$ ,  $I_y$  and the test point voltages. [10 marks]
- Estimate the open loop gain of this amplifier, if the output from the test point 4 is 930mV with the input signal of 6.2mV. [2 marks]
- Determine the faulty component and the fault for the following cases giving reasons.

Case	1	2	3	4	5	
A	3.31	2.96	2.71	10.2	2.3	Positive half clips
B	1.96	6.66	1.31	14.8	6.6	No output
C	1.96	9.13	1.41	8.63	8.53	No out put
D	1.96	11.1	1.3	10.7	10.5	the output signal clips

[8 marks]

2. The circuit in figure 2 represents a Wien bridge oscillator. All transistors in the circuit are high gain type.  $R_T$  is a thermistor.

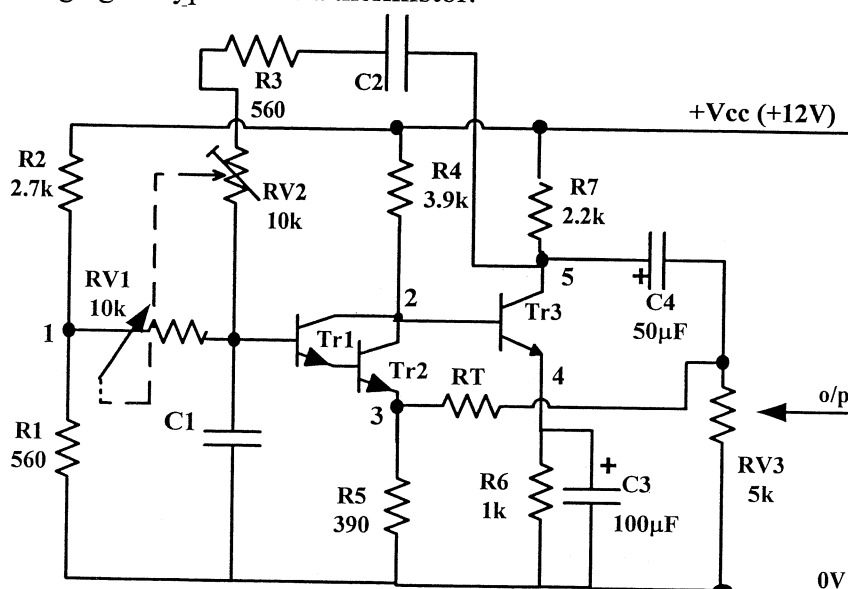


Figure 2

- What are the main sections needed for a circuit to oscillate? [2 marks]
- Write the components or paths in figure 2 for the section mention in 2.a. [2 marks]
- State the function of  $R_T$ . [1 mark]
- Compute the capacitance value for the capacitor  $C_1$  and  $C_2$  if the circuit generates 15 kHz signal as a maximum operating frequency. (Consider  $C_1 = C_2$ ). [2 marks]
- Estimate the minimum operating frequency using the calculated capacitance value in 2.d. [2 marks]
- Calculate the test point voltages for the circuit shown in figure2. [5 marks]
- Find the fault and the faulty component/s for the following faulty cases.

Case	1	2	3	4	5	
A	2.061	3.381	0.861	12	0	No output
B	2.061	3.381	0.861	5.800	2.781	Output signal high and clipped
C	0	5.470	0	4.970	4.870	No output
D	2.061	3.381	0.861	5.800	2.781	There is a waveform at T.P.2, No output

[6 marks]

3. A Schmitt trigger circuit is shown in figure 3.1. Transistors have high gains and saturated collector emitter voltage is 0.

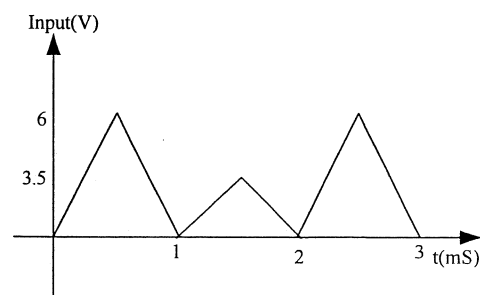
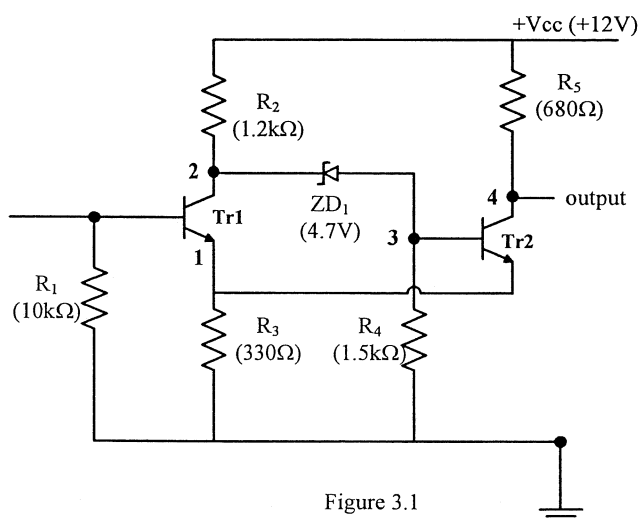


Figure 3.2


- Calculate the threshold voltages. [2 marks]
- Find the possible values for the output. Derive the test point voltages for each output value. [6 marks]
- Draw the output waveform for the input signal shown in figure 3.2. [4 marks]
- Under fault conditions, two dc voltages are given to the input and the resulting test point voltages are listed below. State the faulty component/s giving fault type with reason. [8 marks]

Case	input	1	2	3	4
A	6	5.4	8.2	4.1	12
B	6	5.4	5.6	0.9	0
C	0	0	12	0	12
D	0	0	8.2	4.1	12

4.

- What are the main sections of a tuner in a TV receiver? Explain the function of each section. [6 marks]
  - In a defective TV receiver only the sound is received. Explain what sections are likely to be faulty and how you are going to identify the faulty section. [4 marks]
- Compare the R.F and A.F amplifiers in a radio receiver. [2 marks]
  - Draw the block diagram of a superheterodyne receiver. [3 marks]
  - A defective radio receiver gives a distorted audio. Explain process of the detection of the faulty section if you are given an oscilloscope. [5 marks]


5. A Switch mode power supply circuit is shown in figure 5.

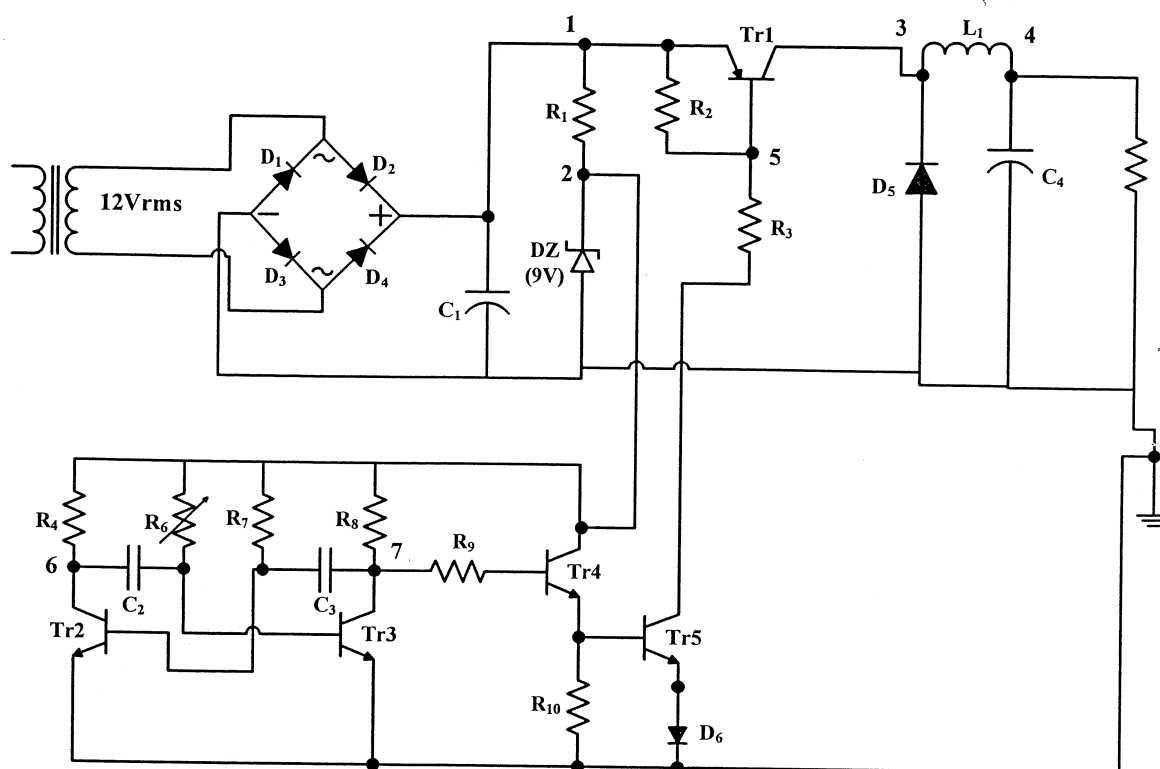

**Figure 5**


- Indicate the current path via the load for the two cases when V5 is high and low. [4 marks]
- What is the function of L1 and D5? [3 marks]
- State the effect on the output voltage when R6 is
  - increases
  - decreased. [4 marks]
- State the difference between D1 and D5. [2 marks]
- Draw the waveforms at test points 5, 6 and 7 on a common time scale with clear indication of voltage levels. [4 marks]
- Consider following fault cases and determine the fault, faulty components giving the reasons. [3 marks]

Case	1	2	3	4	5	6	7
A	15.5	9	10.5	10	16.2	0	0
B	16.3	9	11	10.5	16.2	0	9

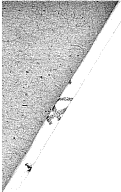

-

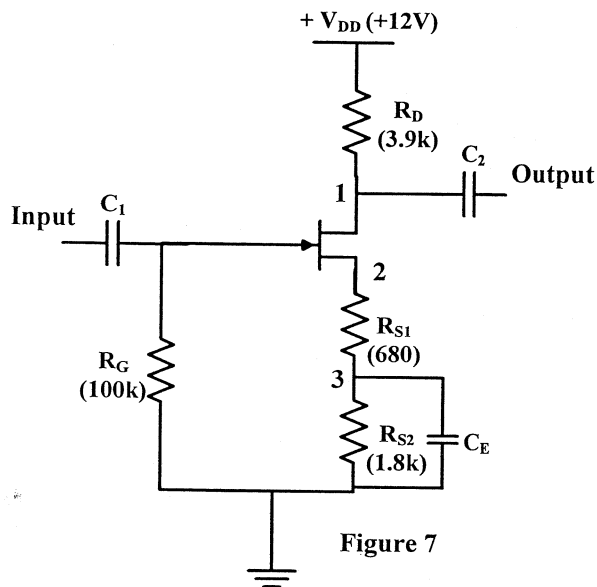
7. The circuit shown in figure 7 is an FET operated amplifier. The drain current of the JFET is given by  $I_D = 0.3 (V_{GS} - V_P)^2$  with  $V_P = -5V$ .



- Find the drain current, transconductance of the FET and the test point voltages at no signal. [7marks]
- Find an expression for the voltage gain and calculate its value. [5 marks]
- Find the maximum input voltage applicable for a distortion free output. [2 marks]
- Find the faulty component/s giving fault type with reasons for the following cases. [6 marks]

Case	1	2	3	
A	7.29	2.99	2.17	Output is 1.18V when the input is 1V.
B	3.50	3.00	2.17	-ve half of the output is clipped
C	9.66	3.58	3.17	+ve peak of the output is clipped for maximum input signal

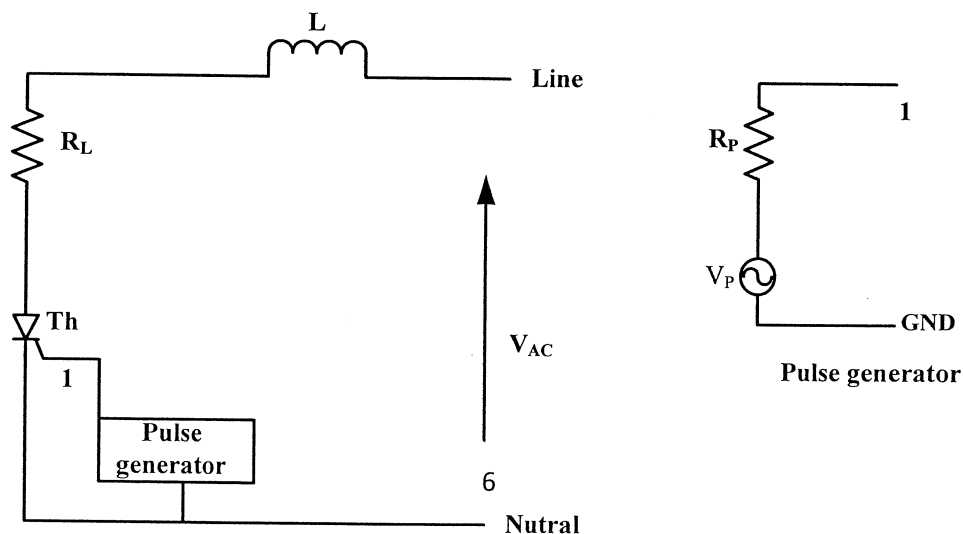8. Power control circuit is shown in figure 8. The pulse generator has pulse voltage  $V_P$  with a internal resistance of  $R_P$ .



The power device specifications are given below.

Repetitive peak off state voltage : 350V

On state current RMS : 20A

On state voltage : 2V

Peak gate voltage : 2V

Peak gate current : 2A

Minimum gate voltage : 2V

Minimum gate current : 30mA

Holding current : 50mA

- a. Select a suitable voltage for  $V_p$  and calculate the  $R_p$  value. [4 marks]
- b. Calculate the maximum and minimum usable values of the load  $R_L$ . [4 marks]
- c. If the pulse generator generates a signal with a 1ms pulse width, draw the voltage variation signal via the load with reference to the line voltage of the signal. [4 marks]
- d. Locate the fault, if the load is getting the maximum power which cannot be changed by controlling the pulse repetition rate of the pulse generator. [4 marks]
- e. Comment on the operation of the circuit, when the supply voltage is increased by 10%. [4 marks]