



**ECX3230 – Electronics**  
**Final Examination**

**Closed Book Test**

Date: 23<sup>rd</sup> April 2008

Time: 09.30-12.30

Answer any five questions.

1. Figure-Q1A shows a single stage transistor amplifier which makes use of a simple biasing arrangement. Figure-Q1B shows the output characteristics of the above transistor.
  - (a) Explain the functions of  $R_B$ ,  $R_C$  and  $R_L$ .
  - (b) Calculate the base current  $I_B$ .
  - (c) Draw the dc load line on figure-Q1B. (Use the given answer sheet)
  - (d) Locate the operating point of the transistor on figure-Q1B and find  $V_{CE}$  and  $I_C$  at the operating point.
  - (e) Now a sinusoidal signal is applied to the input of the amplifier and the signal amplitude is gradually increased. What is the maximum possible value of the undistorted output voltage?

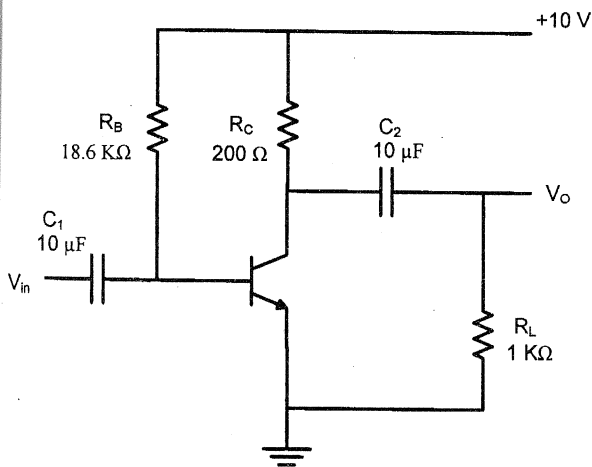


Figure - Q1A

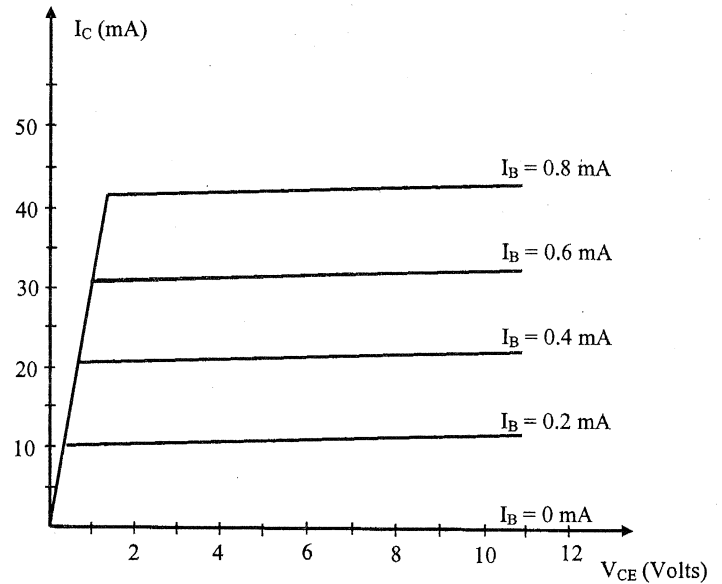


Figure-Q1B

2.
  - (a) Write down the advantages of field effect transistors (FETs) over bipolar junction transistors (BJTs).
  - (b) Consider the circuit shown in figure-Q2.

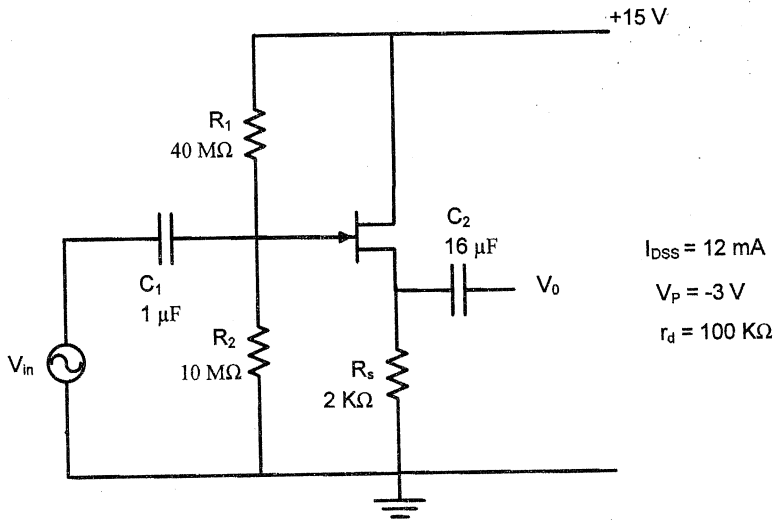


Figure - Q2

- i. What is the amplifier configuration used in this circuit?
- ii. Find the current  $I_D$  when no input signal is applied.
- iii. Find the  $g_m$  of the device under the operating conditions given in part (b).
- iv. Draw the AC equivalent circuit for the amplifier and derive expressions for the voltage gain and input impedance for mid band frequencies.
- v. Calculate voltage gain and input impedance. Assume that the reactance of the capacitors is negligible.

3.

- (a) Indicate the transistor configurations that exhibit the following properties.
  - i. Highest input resistance
  - ii. Highest voltage amplification
  - iii. Lowest output resistance
  - iv. Highest current amplification
- (b) A transistor amplifier is shown in figure-Q3A.

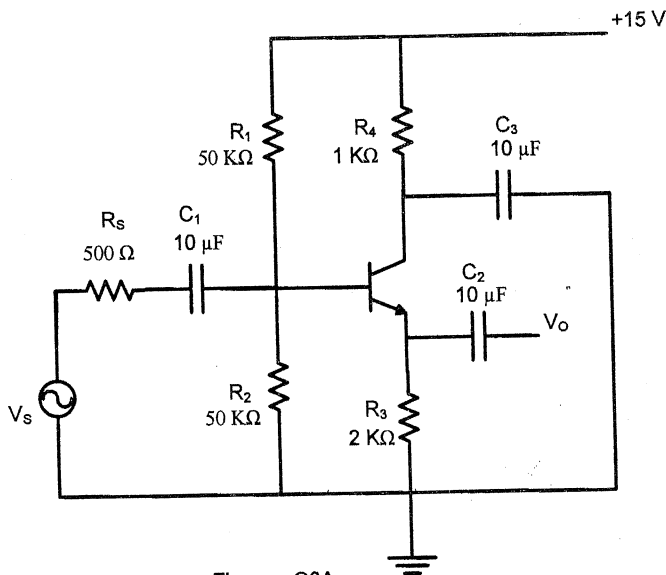


Figure - Q3A

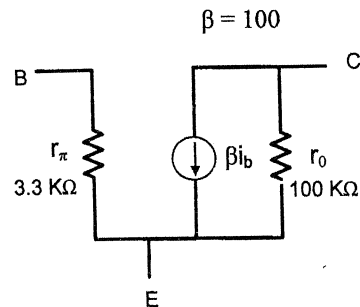


Figure - Q3B

5. A simple dc power supply circuit is shown in figure-Q5.

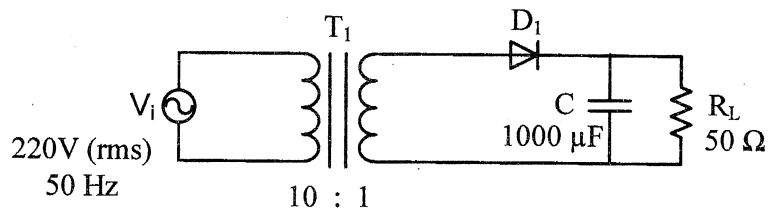


Figure-Q5

- (a) Identify the type of this rectifier circuit.  
 (b) Sketch the voltage across  $R_L$  as a function of time showing its relationship to the secondary voltage from the transformer.  
 (c) Calculate the peak secondary voltage from the transformer  $T_1$ .  
 (d) Assuming 10% ripple voltage across the load calculate the peak to peak amplitude of the ripple voltage.  
 (e) Explain how the circuit could be modified to produce a 5% ripple voltage.
- 6.
- (a) Figure-Q6A shows a D latch circuit. Write the truth table indicating E, D, Q and  $\bar{Q}$  for the circuit.  
 (b) Show how this D latch can be used to form a gated SR latch and give its truth table.  
 (c) The waveforms of figure-Q6B are applied to the D and E inputs of figure-Q6A. Draw the timing diagrams of the waveforms Q and  $\bar{Q}$  with D and E inputs. Assume Q = 0 initially.

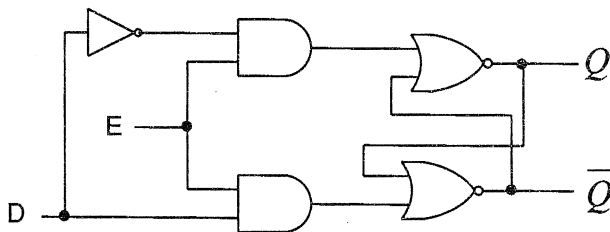


Figure - Q6A

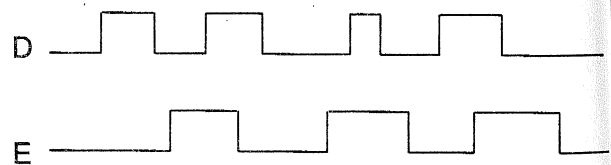


Figure-Q6B

- 7.
- (a) Obtain the logic function Z of the circuit shown in figure-Q7 in the sum of products form and then derive the truth table for the circuit.  
 (b) Find the minimized solution of the following function in sum of products form using the karnaugh's map.  

$$F = \sum 0, 1, 2, 3, 4, 5, 8, 10, 11, 14$$
  
 (c) Design a logic circuit with inputs P, Q, R so that output S is HIGH whenever P is 0 or whenever  $Q = R = 1$ .  
 (d) Implement the design of part (c) using only NAND gates.

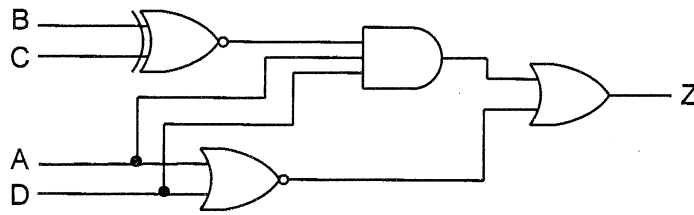


Figure - Q7



8. A multivibrator circuit is shown in figure-Q8.

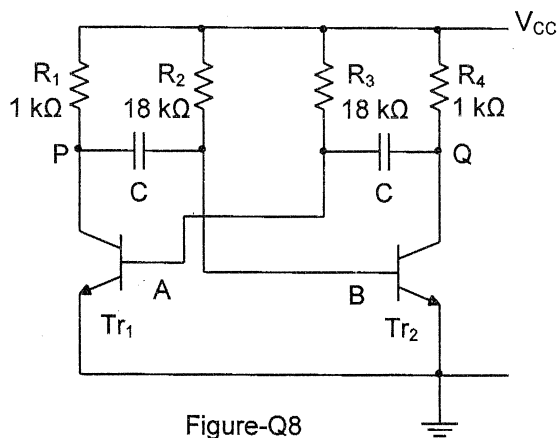


Figure-Q8

- What is the type of this multivibrator?
- Draw the waveforms at points A, B, P and Q in a common time scale. Assume that at time  $t = 0$ ,  $Tr_1$  is switched on.
- Derive an expression to find the frequency of the waveform at point Q.
- The multivibrator shown in figure-Q8 is designed to give a symmetrical output waveform having a periodic time of 2 ms. Calculate the value of C.

## Answer Sheet for Question 1

Attach this answer sheet to your answer script if you answer for question 1.

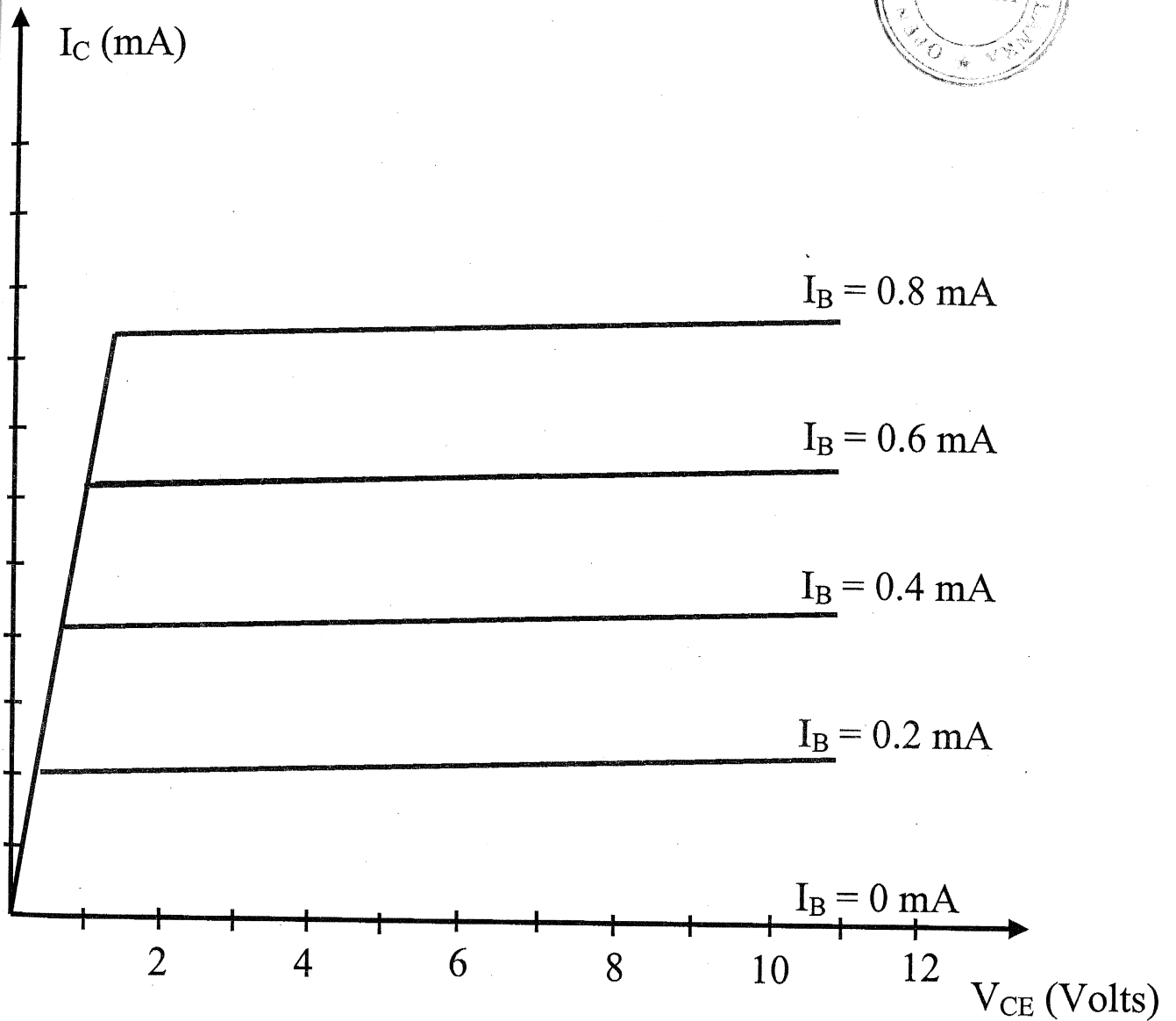


Figure-Q1B