



ECX3231 - Electrical Circuits & Measurements
 Final Examination 2007/2008

Duration: 3 hours

Date: 06.05.2007

Time: 9.30-12.30

This question paper consist of two sections over four pages. The paper contains ten questions and each question carry equal marks. Answer **six** questions selecting **at least two** questions from **section B**.

Section - A

Q1. An AC circuit having two sources of same frequency is shown in the figure Q1.

- Find the Thevenin's equivalent circuit across the terminals AA' of the circuit.
- There is a value of the capacitance C that causes maximum power P_{max} that flows across the terminals AA'. Determine the capacitance C and power P_{max} using the Thevenin's equivalent circuit. Assume that only value of the C can be varying for this purpose, but the real part of the load impedance cannot change.

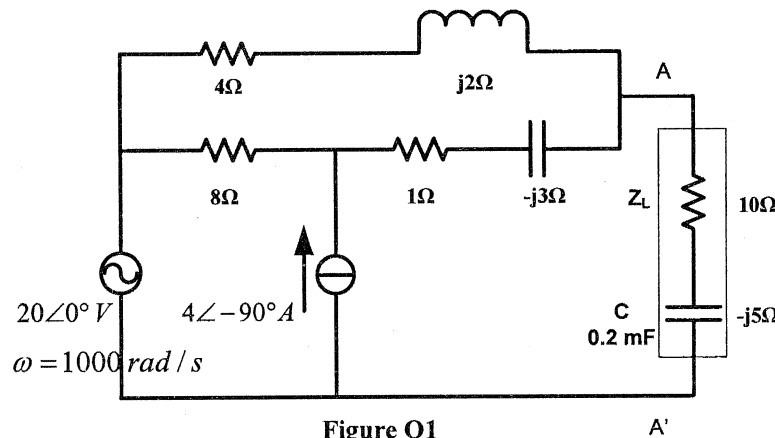


Figure Q1

Q2. The switch S shown in the figure Q2 has been closed for long time. Hence, the inductor is act as a short circuit, because this condition is like a dc stage. Switch is opened at $t=0$, so, current will decay through the resistors as in a simple first in order RL circuit, but in this case not via a single resistor instead of the equivalent resistance.

- Determine the steady state current through the inductor before the transition of the switch
- Write an expression to the inductor current $i_L(t)$ for $t \geq 0$
- Find the current through the inductor $10 \mu s$ after the switching.

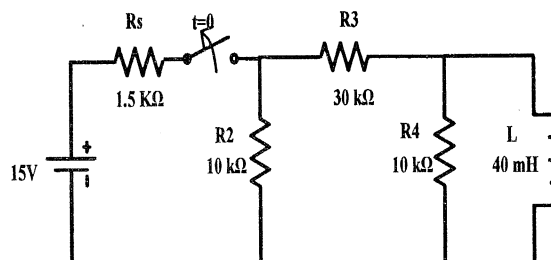


Figure Q2

Q3. Consider an equivalent circuit of a practical amplifier shown in the figure Q3/4.

- (a) Write the current balance equations (KCL) to the Node 1 and Node 2 in terms of the nodal voltages and the input current I_1 of the amplifier.
- (b) Obtain the matrix form of the nodal equations by eliminating I_1 from the results of Q3 (a)¹.
- (c) Determine the nodal voltages V_1 and V_2 of the given circuit using the derived formulation in Q3 (b).

1. **Hint:** Get another independent expression for I_1 and eliminate it from above equations.

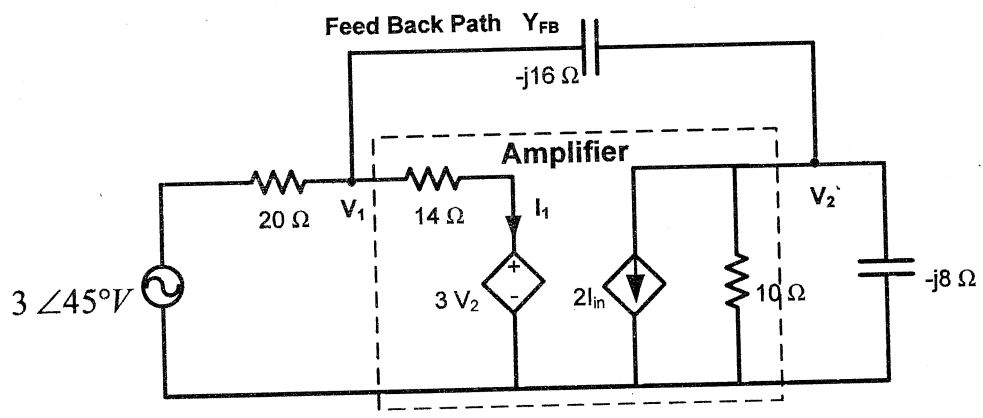


Figure Q3/4

Q4. Formulate the circuit given in the figure Q3/4 using two port network modeling by following the steps given below.

- (a) Obtain Y parameters of the amplifier¹
- (b) Determine the Y parameters of the parallel resultant of the amplifier and the feed back².
- (c) Use Y parameter model of the resultant circuit to obtain two expressions for V_1 and V_2 .

1. **Hint:** You can determine the h parameters first and then obtain Y using $Y = \begin{vmatrix} 1/h_{11} & -h_{12}/h_{11} \\ h_{21}/h_{11} & |h|/h_{11} \end{vmatrix}$

2. **NB:** All elements of the Y parameters model of a single series resistor R is 1/R.

Q5. A passive constant K filter has to be designed to suppress the frequencies below 6 kHz.

- (a) Derive expressions for the open circuit input impedance and the short circuit input impedances of the T type high pass filter circuit.
- (b) Determine the pass band of the T type high pass filter using a reactance sketch.
- (c) Calculate the values of the components L and C that fix the cut off frequency f_c to the 3 kHz and the design resistance R_o or the value of $\sqrt{L/C}$ to the 600Ω.

Q6. A driving point impedance function $Z(s)$ of a realizable LC network is given below.

$$Z(s) = 3 \frac{(s^2 + 1)(s^2 + 16)}{s(s^2 + 9)}$$

- Sketch the pole zero diagram to indicate the poles and zeros of the driving point impedance function $Z(s)$.
- Plot the variation of the reactance $X(s)$ versus the angular frequency ω .
- Realize the driving point impedance function.



Section – B

Q7

- Determine the number of turns N required to set the full scale deflection current to 5 mA of Permanent Magnet Moving Coil (PMMC) instrument if the magnetic flux density at the air gap is $5 \times 10^{-3} \text{ Wb/m}^2$, and the area of the bobbin is $2 \times 10^{-2} \times 1.5 \times 10^{-2} \text{ m}^2$. If the torque required for the full scale deflection is $0.3 \times 10^{-5} \text{ Nm}$.
- Resistance per unit length of the wind the coil is 125 m Ω /m. Determine the shunt resistor required to extend the measuring range to 50 mA.
- The full scale deflection voltage of the above instrument is set to 1 V using a limiting resistor R_1 , and another resistor R_2 used to extend the measuring range to 20 V. Determine the values of R_1 and R_2 .

Q8. An AC Bridge circuit is shown in the figure Q8.

- Given that the Z_2 and Z_3 contain pure resistors. Show that a practical inductor having self inductance as well as effective series resistance can be measured with help of another parallel capacitor and a variable resistor Z_4 or Z_1 .
- Briefly explain why this bridge is not suitable to measure low quality inductors if two resistors varies to obtain the balance condition. The quality factor of an inductor at a given frequency is the ratio of inductive reactance to self resistance or $\frac{\omega L_s}{R_s}$.

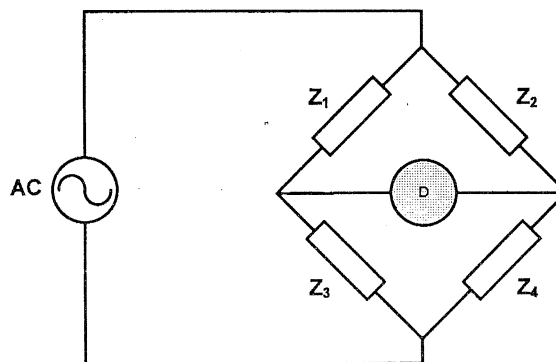


Figure Q8

1. **Hint:** For the given components show that balance can be obtain hence given parameters can be measured

Q9. It is required to design a simple digital voltage measuring instrument that indicates the voltage through displaying devices. The voltage range to be measured is between 0 V to 200 V and at least it should indicate measured values in steps of 100 mV.

- (a) Draw a functional block diagram of such a digital voltmeter.
- (b) Select an appropriate Analogue to Digital Converter (ADC) for the above application which used to measure the random voltage samples. Briefly explain the operation of the selected ADC by using a sketch and with proper justification of your selection.
- (c) Determine the number bits required to achieve the required resolution of the measuring device.

Q10. Write brief short notes on three of following topics.

- (a) Advantages and disadvantages of using analogue multi meters for electrical measurements.
- (b) Application of Digital Storage Oscilloscope
- (c) Operational principles of Spectrum Analyzer
- (d) Role of electronic circuit simulators in circuit analysis

The Op
Diplom
ECX 32
Final E
Durati
Date: /
This p
marks

1.

2.