



**ECX3231 - Electrical Circuits & Measurements**  
 Final Examination 2005

Duration: 3 hours

Date: 08.05.2006

Time: 9.30-12.30

Answer *five* questions.

All questions carry equal marks

Q1

- Use super position theorem to find the open circuit voltage across the impedance  $Z$  of the circuit shown in Figure Q1.
- Find the Thevenin's equivalent circuit required to determine the current through the impedance  $Z$ .
- Determine the maximum achievable power across the impedance  $Z$ .

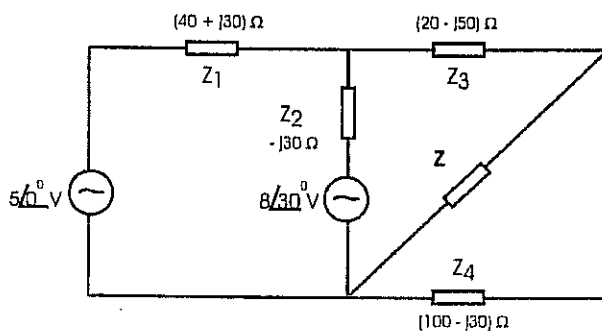


Figure Q1

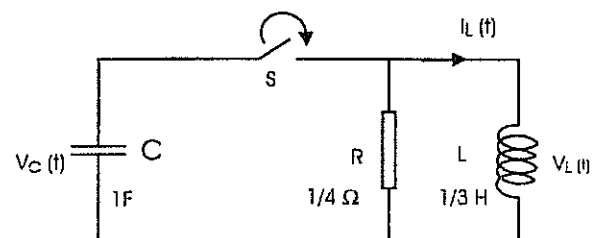


Figure Q2

- Q2 The switch  $S$  of the circuit shown in Figure Q2 is closed at  $t = 0$  and initial circuit conditions of the circuit are  $V_C(-0) = 10 \text{ V}$  and  $I_L(-0) = 0 \text{ A}$
- Determine the general form of the voltage across the inductor  $V_L(t)$
  - Obtain an expression to evaluate the instantaneous voltage across the inductor  $V_L(t)$ .
  - Show that the initially stored energy in the capacitor is completely dissipating through the resistor as  $t$  tends to infinity.
  - Sketch the variation of voltage across the inductor without actually solving the circuit if inductance of the inductor is 100mH.

Q3 For the circuit shown in Figure Q3

- Write the tie set matrix.
- Write the branch impedance matrix and branch emf vector
- Determine the mesh impedance matrix.
- Determine the mesh emf vector.

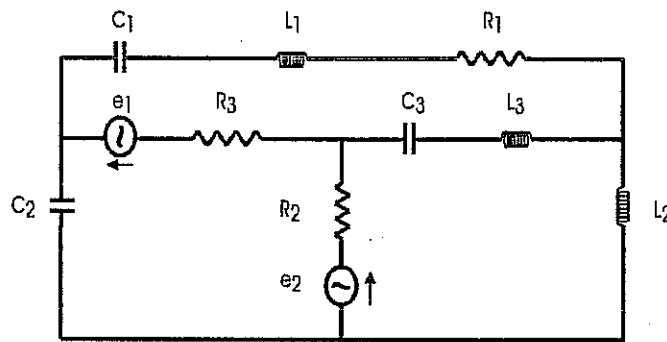


Figure Q3

Q4

- List the observations that required to determine the Y parameters of a symmetrical T network.
- Determine the ABCD parameters for the T network shown in Figure Q4.(a) in terms of  $Z_1$  and  $Z_2$ .
- Obtain Y parameters of the above T network by using determined ABCD parameters.
- Hence or otherwise, determine the Y parameters of the twin T network shown in Figure Q4.(b)

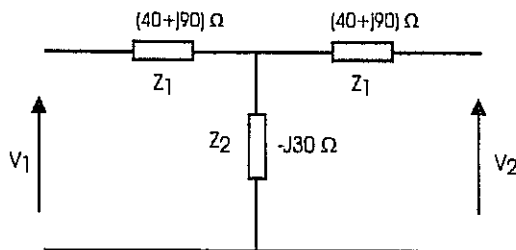


Figure Q4.(a)

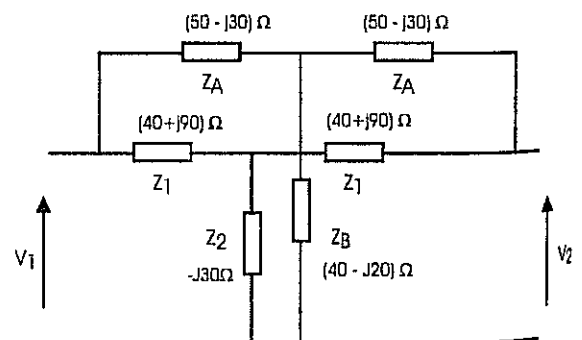


Figure Q4.(b)

Q5

- (a) For the bridge circuit shown in Figure Q5, determine the self-inductance  $L_1$  and resistance  $R_1$  in terms of bridge components at the balance condition. You may follow below instructions to obtain the balance equations.

- 1) Equate potential differences between **bc** to **ce**
  - 2) Potential difference between nodes **ab** is equals to nodes **ade**
  - 3) Voltage drop across  $R_4$  is same as potential difference between **dec**
- (b) Select two components that causes easy convergence to the balance condition
- (c) Draw the phasor diagram indicating the voltages across each element at balance condition.

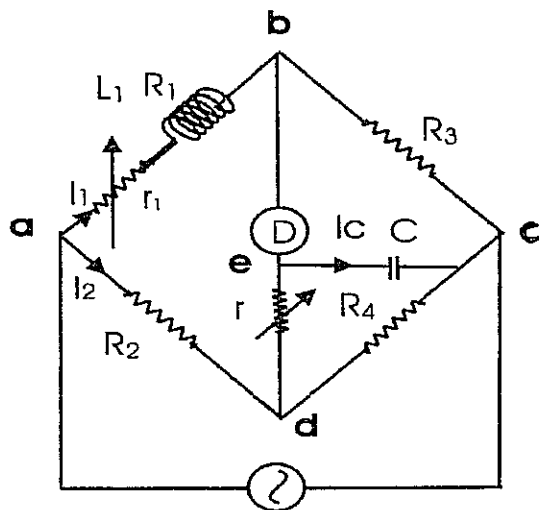


Figure Q5

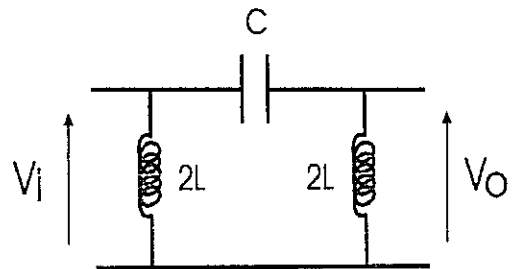


Figure Q6

Q6

- (a) Determine the open circuit impedance  $Z(s)_{oc}$  and short circuit impedance  $Z(s)_{sc}$  for the LC filter circuit shown in Figure Q6.
- (b) Determine the type and pass band of the given filter by using reactance sketches.
- (c) If inductance  $L$  is 4.77 mH and capacitance  $C$  is 0.01326  $\mu$ F, find followings;
  - (i) Characteristics impedance and phase constant at 25 KHz
  - (ii) Attenuation at 5 KHz

Q7

- List three features of a realizable driving point impedance function using L and C elements.
- Partial factored form of a driving point impedance function contains a pole at origin, a pole at infinity, and a complex conjugate pair of poles. Show the configuration of the LC network corresponds to the above driving point impedance function.
- Realize first Foster form of the RL impedance function  $Z_1(s)$  given below
- Determine the first Cauer form of the driving point impedance function  $Z_2(s)$  given below.

$$Z_1(s) = \frac{(2s^2 + 6s + 1)}{(2s + 2)}$$

$$Z_2(s) = \frac{(12s^4 + 10s^2 + 1)}{(4s^3 + 2s)}$$

Q8

- Explain how the capabilities of measuring DC voltages, AC voltages, resistances, and extensions of DC ammeter range are integrated to a basic Permanent Magnet Moving Coil instrument to use it as a multi meter.
- A DC voltmeter having sensitivity of  $20 \text{ k}\Omega/\text{V}$  is used to measure voltage across the resistor R of Figure Q8. Determine the meter reading, if the voltmeter selector switch is positioned at 10 V.
- A symmetrical square wave voltage having amplitude A (V) is applied to an average value responding ac voltmeter having a scale calibrated in terms of rms value of a sine wave. By assuming the meter rectifies any negative voltages before taking average value, calculate
  - The form factor of the square wave voltage
  - The error in meter indication

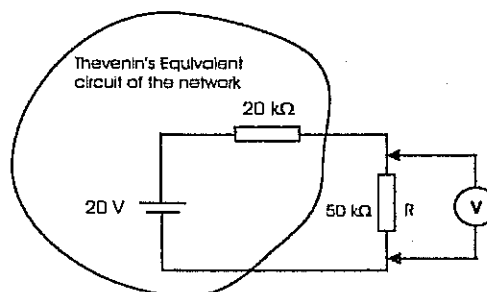


Figure Q8