

The Open University of Sri Lanka
 Department of Electrical and Computer Engineering
 Diploma in Technology/Bachelor of Technology - Level 03



ECD1204 – Circuit Theory
 Final Examination 2005

Duration: 3 hours

Date: 18.04.2006

Time: 0930 – 1230 hrs.

Answer *five* questions.
 All questions carry equal marks

Q1

- Obtain the Thevenin's equivalent circuit required to determine the current through impedance Z of figure Q1 using source conversion
- Draw the Norton's equivalent circuit using the answer for Q1 (a)
- Find the short circuit current through the resistor R if R_A is infinity

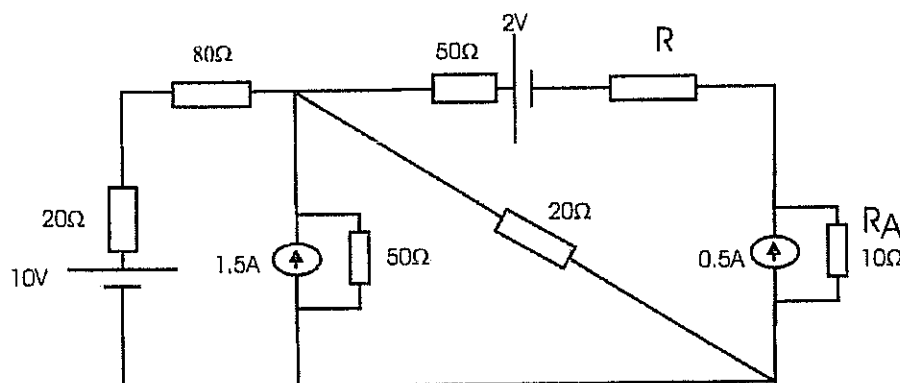


Figure Q1

- Q2 A balance star connected load having impedance of $(10 + j3) \Omega$ on each phase is connected to a balance supply of 415V line voltage using connecting wires having impedance of $(3 + j1) \Omega$.
- Find the line current
 - Find the phase voltage at load
 - Find the power delivered to each load
 - Sketch the phasor diagram for the line and phase voltages at the load

Q3

- Use superposition theorem to obtain the Thevenin's equivalent circuit that required to determine the current through the load impedance Z_L of the network shown in figure Q3.
- Estimate the maximum possible power that can be delivered to the load and impedance Z_L at which this maximum amount of power is appearing.
- Is it possible to obtain the same amount of maximum power to Z_L at another frequency?

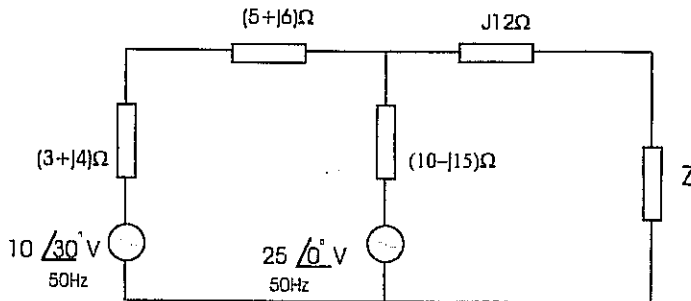


Figure Q3

Q4 An electrical circuit is shown in figure Q4

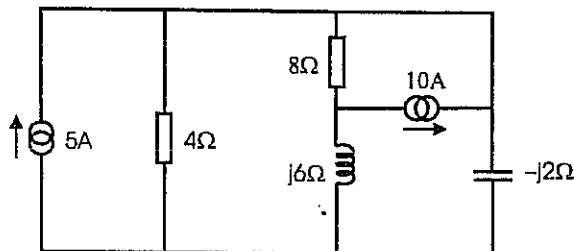


Figure Q4

For the circuit shown in figure Q4

- Find number of nodes and branches
- Draw the oriented graph for the circuit
- Find the cut-set matrix and nodal admittance matrix

Q5 A circuit contains series connected 5Ω resistor, $10\mu\text{F}$ capacitor, and a 90mH inductor. If the following voltage is supplied to the circuit:

$$v(t) = 60 + 100 \sin(100\pi t) + 30 \sin(300\pi t - 90^\circ) + 80 \sin(500\pi t + 30^\circ)$$

Find

- Instantaneous value of current through the circuit
- Active and reactive power delivered from the source

Q6

- (a) Obtain Y parameters for the two networks shown on figure Q6 (a) and (b).

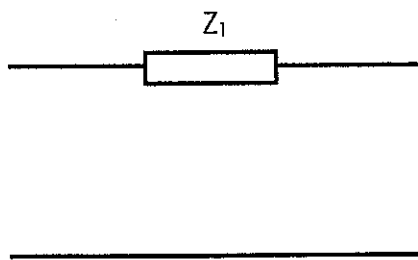


Figure Q6 (a)

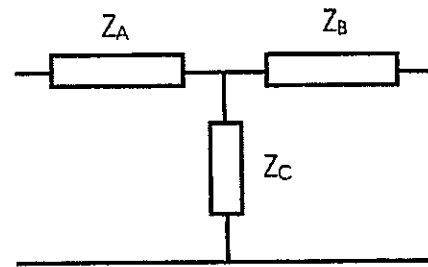


Figure Q6 (b)

- (b) Hence or otherwise estimate the I_1/I_2 ratio for the network shown in figure Q6 (c).

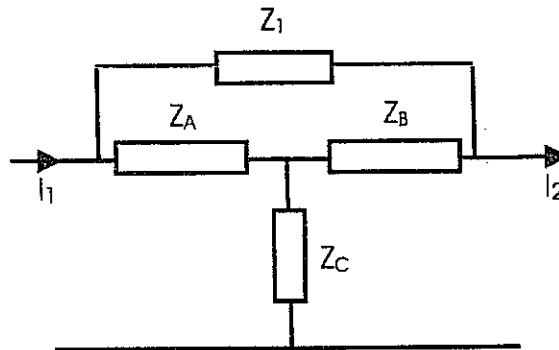


Figure Q6 (c)

Q7

- (a) Determine the open circuit voltage transfer ratio for the filter shown in figure_Q7.
- (b) If above circuit is used as a second order LC Low Pass Filter, determine the type of reactive component that should be used for Z_1 and Z_2 using upper and lower limits of the open circuit voltage transfer function.
- (c) Determine the pass band of the LPF filter by assigning $L/2$ and C for appropriate components

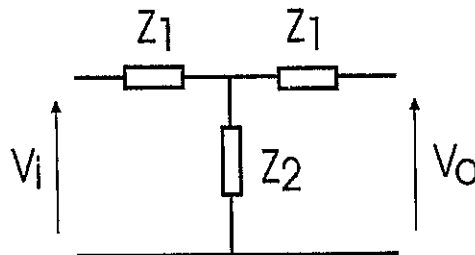


Figure Q7

- (d) Draw the circuit diagram of π -type LC band pass filter

Q8

- (a) Derive an expression for the driving point impedance $Z(s)$ of the network shown in Figure Q8. Hence identify the poles and zeros of the driving point impedance $Z(s)$.

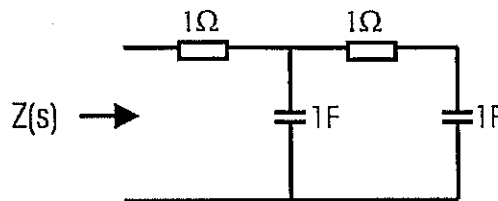


Figure Q8

- (b) Realize **First Foster** form of the following impedance function. Hence determine the frequencies at which driving point impedance is infinite.

$$Z(S) = \frac{S^4 + 14S^2 + 32S + 40}{2S^3 + 8S}$$

- (c) Realize **Second Cauer** form of the impedance function given below.

$$Z(S) = \frac{2S^2 + 6S + 1}{2S + 2}$$