

THE OPEN UNIVERSITY OF SRI LANKA
 B.Sc. DEGREE PROGRAMME: LEVEL 04
 DEPARTMENT OF MATHEMATICS AND COMPUTER SCIENCE
 FINAL EXAMINATION – 2011/2012
 CSU2178: DIGITAL COMPUTER FUNDAMENTALS
 DURATION: TWO HOURS (2 HOURS)



Date: 06th December 2012

Time: 9.30am - 11.30am

Answer **FOUR** Questions **ONLY**.

Q1.

- a) Briefly describe the following.
 - i. Two's complement
 - ii. Seven segment display
 - iii. The von-Neumann computer model
 - iv. Unicode character set
- b) Convert the following Decimal numbers into **Binary**, **Octal**, and **Hexadecimal**.
 - i. 178_{10}
 - ii. 32_{10}
- c) Use **two's complement addition** to perform the following calculations.
 - i. $89_{10} + 28_{10}$
 - ii. $89_{10} - 28_{10}$
 - iii. $-89_{10} + 28_{10}$
 - iv. $-89_{10} - 28_{10}$
- d) Convert the following **hexadecimal** numbers into **binary**.
 - i. $5FB2_H$
 - ii. $F089_H$
- e) Draw the truth table of a **full adder circuit** and implement it using basic logic gates.

Q2.

- a) Describe **AND**, **OR**, **NOT** operations with use of **truth tables**.
- b) Implement the following gates using **two-input NAND** gates.
 - i. NOT
 - ii. OR
 - iii. NOR
 - iv. XOR
- c) Briefly explain the following.
 - i. Multiplexer
 - ii. Counter
 - iii. Register
 - iv. 8 to 3 encoder.
- d)
 - i. Draw the block diagram and truth table for a **4 to 1 Multiplexer**.
 - ii. Implement the 4 to 1 multiplexer using basic logic gates.
 - iii. Implement the **16 to 1 Multiplexer** using **4 to 1 Multiplexers** only.

Q3.

a) Prove the following using **Boolean algebra**.

i. $(\overline{A} + B)(A + B + D)\overline{D} = B\overline{D}$

ii. $ABC + A\overline{B}C + AB\overline{C} = A(B+C)$

iii. $A(B + \overline{C}) + B(C + \overline{A}) + C(A + \overline{B}) = A + B + C$

iv. $(A + B)(A + \overline{B})(\overline{A} + C) = AC$

v. $(A + B + C)(A + \overline{B} + C)(A + B + \overline{C})(A + \overline{B} + \overline{C}) = A$

b) Find the minimal logic expression for the following truth table using the **K-MAP** method.


Design a circuit to implement this truth table using **3-input NAND** gates only.

A	B	C	D	F (output)
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

c) A three bit binary number is represented as $A_2A_1A_0$, where A_2 , A_1 , A_0 represent the individual bit. A_0 = **LSB** (Least Significant Bit) and A_2 = **MSB** (Most Significant Bit)
Design a logic circuit that will produce a high output (1) when the input **binary value** is **greater than 010** and low output (0) when the input value is **less than 100**.

- a) Write short notes for each of the following.
- Direct memory access.
 - Data path.
 - Disk files system.
 - System bus model.
- b) "PORTs can be used to communicate with the computer." Do you agree with this statement? Justify your answer.
- c) What is the difference between CMOS and TTL IC types?
- d) What is fetch-execute cycle? Briefly explain.
- e) What are the advantages and disadvantages of the Assembly Language?

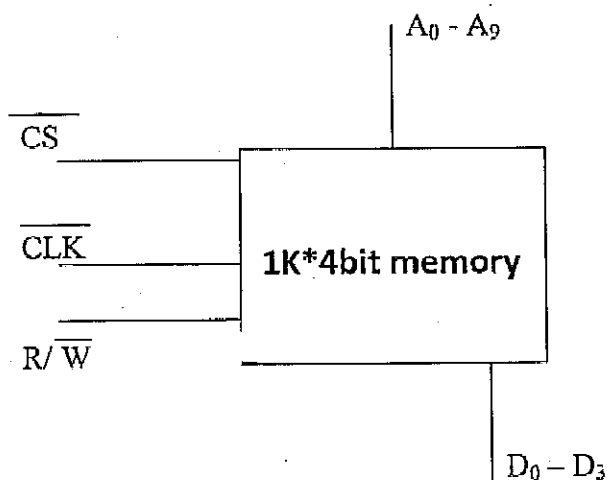- a) Explain the need for a Memory Hierarchy in a computer system.
- b) Briefly explain how Cache Memory could be used to improve the performance of a computer system.
- c) Describe the advantages of SRAM and DRAM.
- d) What is meant by the Word Length of a processor?
- e) Assume that you are given FOUR 1K*4bit memory chips and other necessary digital components (see Figure Q5.e). Using these:



(Figure Q5.e)

- Construct 1K*16 bits memory.
- Construct 4K*4 bits memory.
- Construct 2K*8 bits memory.

Q6.

- a) Describe **Combinational circuits** and **Sequential circuits**. Use a block diagram if necessary.
- b) What is the importance of a **Clock** in **Sequential Circuits**?
- c) Explain the function of a **JK flip-flop**, **T flip flop** and **D flip flop** using truth tables and block diagrams.
- d) Construct a 4 bit shift register using **D flip-flop** as the basic building block. (draw the block diagram)
- e) Explain the function of the 4-bit shift register constructed in above (Q6 – f)

*****All Right Reserved*****