

THE OPEN UNIVERSITY OF SRI LANKA
DEPARTMENT OF MATHEMATICS AND COMPUTER SCIENCE
B. SC. DEGREE PROGRAMME 2013/2014



FINAL EXAMINATION

CSU2178 : DIGITAL COMPUTER FUNDAMENTALS

DURATION: TWO HOURS (2 HOURS)

Date: 02.12.2014

Time: 9.30 am – 11.30 am

Answer **FOUR** Questions **ONLY**.

Q1.

a. Convert the following Decimal numbers into Binary, Octal and Hexadecimal.

i. 111_{10}

ii. 97_{10}

b. Convert the following Binary numbers into Octal and Hexadecimal.

i. 110010101_2

ii. 1010.11_2

c. Convert the following Decimal numbers into BCD format.

i. 35_{10}

ii. 937_{10}

d. Draw a truth table for a full adder.

Q2.

a. Prove the following rules with regards to Boolean Algebra.

i. Associative Law

ii. Distributive Law

b. Prove DeMorgan's Theorem.

c. Let X be defined by $X = A'BC + ABC' + A'B'C' + ABC + A'B'C$

i. Minimize the expression for X using Boolean rules. State the rules.

ii. Draw the logic circuit for X.

- d. Minimize the following truth table using K-map method.

Input				Output
A	B	C	D	Q
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Q3.

- State two differences between sequential logic and combinational logic?
- Draw the Block diagrams to represent combinational logic and sequential logic.
Describe the function of both logics.
- Briefly describe the term Circuit Hazard using an example circuit.
- Draw the truth table for the output of a S-R Flip-Flop.
- Draw the Circuit diagram and Timing diagram for a clocked S-R Flip-Flop.

Q4.

- a. Implement the following gates using two-input NAND gates.
 - i. NOT
 - ii. OR
 - iii. XOR
- b. Briefly explain the following digital circuits.
 - i. Multiplexer.
 - ii. Counter.
 - iii. Register.
- c. Draw the block diagram and truth table for a 4 to 1 multiplexer.
- d. Implement a 4 to 1 multiplexer using basic logic gates.

Q5.

- a. Briefly describe the following terms
 - i. Von Neumann architecture.
 - ii. System bus model.
- b. Briefly explain the fetch-execute cycle and explain how CPU works for a given data set.
- c. Write an advantage and a disadvantage of the Assembly language. Write an Assembly language program to add two values in the main memory and display the result.

Q6.

- a. Using examples, briefly explain the existence of a memory hierarchy in a computer system.
- b.
 - i. Design a RAM that stores Four-bit words.(Imagine RAM as a collection of registers)
 - ii. Draw the simplified version of four-word by the four-bit RAM designed above.
- c. State two advantages of a cache memory over main memory.

***** All Right Reserved *****