

The Open University of Sri Lanka  
 B.Sc. Degree Programme, Level – 04  
 Final Examination – 2017/2018  
 PHU4301 – Electronics  
 Duration: 2 hours




Date: 24<sup>th</sup> April 2019

Time: 1.30 p.m. to 3.30 p.m.


Answer all the questions in part A and any 3 questions from part B  
 Non-programmable calculators are allowed. All questions carry equal marks.

### Part A

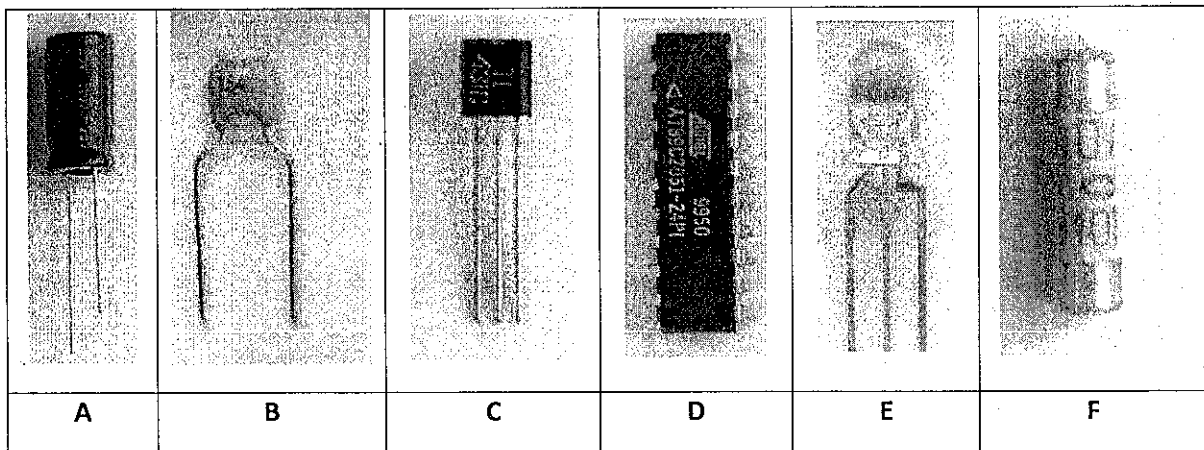- 1) a) Identify the component shown in the figure.



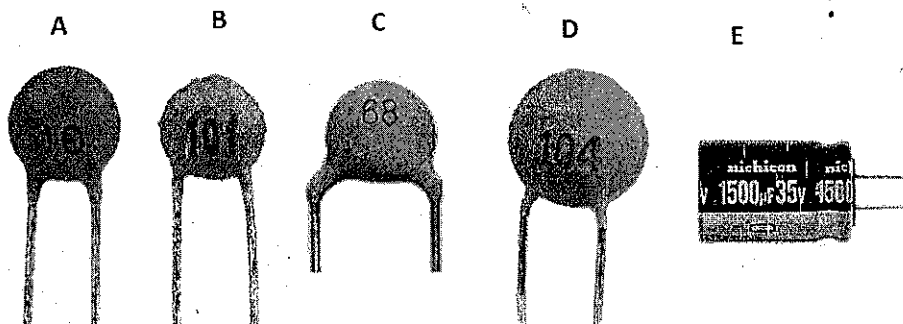- b) Write down the capacitance of each of the following capacitor.



- c) Prototype boards (plug boards / Solderless breadboards) are used to quickly build a circuit. Following is a diagram of a standard prototype board. Copy the following table to the answer script and fill it indicating whether the given points are internally connected to each other or not.



- 2)
- According to Bohr's model of atom, electrons have definite energy levels. But in an energy band diagram for a solid they are represented as a band, which has a range of energy, and not as a single line with specific energy. Explain the reason for this.
  - A cylindrical copper wire of 3 mm diameter with conductivity of  $5.8 \times 10^7 \Omega^{-1} \text{m}^{-1}$  and electron mobility of  $0.0032 \text{ m}^2 \text{V}^{-1} \text{s}^{-1}$  is subjected to an electric field of  $20 \text{ mV m}^{-1}$ . Calculate the following.
    - Charge density of free electrons
    - Current density
    - Current flowing in the wire
    - Electron drift velocity

3)

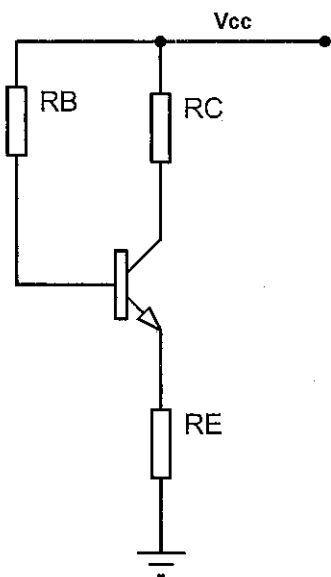


Figure 1

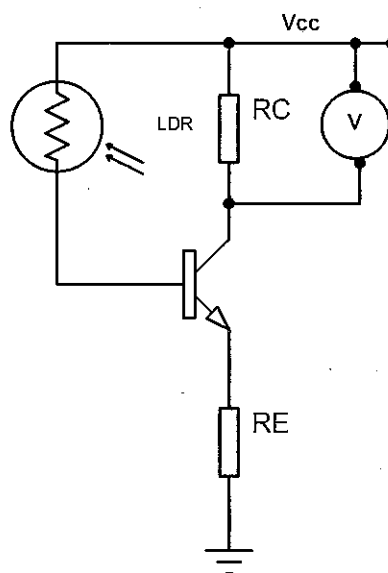


Figure 2

- Consider the circuit in Figure 1. All notations have their standard meanings.
  - Obtain an expression for  $V_E$  using only the terms  $R_E$  and  $I_E$
  - Obtain an expression for  $I_B$  using only the terms  $V_{CC}$ ,  $V_{BE}$ ,  $V_E$  and  $R_B$
  - Write an expression for  $I_B$ , that contains only the terms  $V_{CC}$ ,  $V_{BE}$ ,  $R_B$ ,  $\beta$  &  $R_E$ .
  - According to Ebers-Moll model,  $I_C = \beta I_B$ . Show that  $I_C = \frac{\beta(V_{CC} - V_{BE})}{R_B + (1 + \beta)R_E}$
  - If  $\beta \gg 1$  and  $\beta R_E \gg R_B$  show  $I_C$  is independent from the  $\beta$
- b) A student change the above circuit as follows. He replaces the  $R_B$  resistor with an LDR and connects a Voltmeter to measure  $V_{RC}$ . Resistance of the LDR changes from  $100 \Omega$  to  $1 \text{ k}\Omega$  depending on the ambient light. He wants to show 5 V and 1 V in the voltmeter depending on the light and dark condition. Assuming  $\beta = 100$ ,  $V_{CC} = 6 \text{ V}$ ,  $V_{BE} = 0.6 \text{ V}$ , calculate suitable values for  $R_C$  and  $R_E$ .


4)

a)


- i) Write down the characteristic truth table of a R-S Flip flop
- ii) Design an active low S-R latch using NAND gates

b) Consider the following circuit to find B and R if,

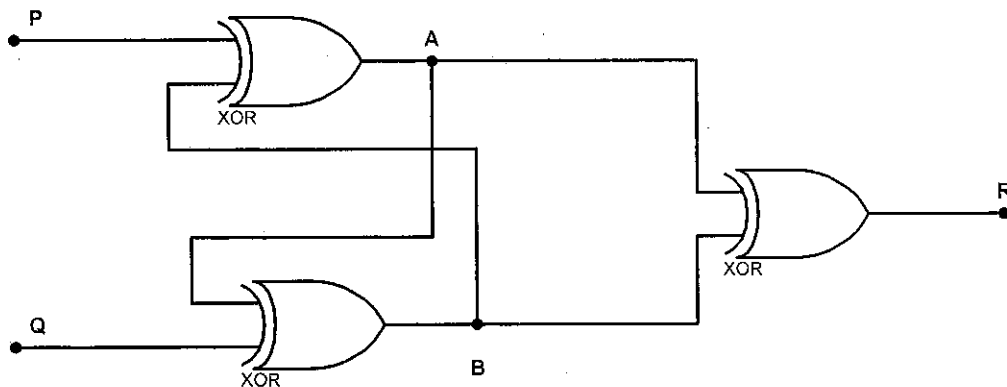- i)  $P = Q = A = 0$
- ii)  $P = Q = 0 ; A = 1$
- iii)  $P = Q = A = 1$
- iv)  $P = 1$  and  $Q = 0$




5) Assume all components are ideal

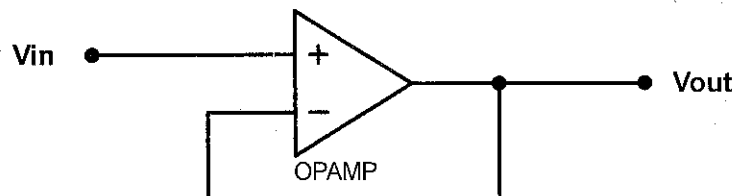
a) Consider the following circuit to obtain an expression for the  $V_{out}$  as a function of  $V_{in}$ 

b) Consider the following circuit.

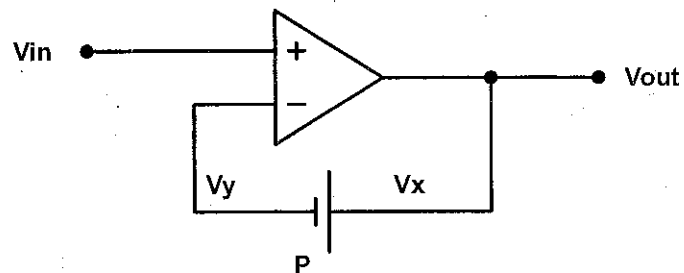- i) If the cell has a voltage of P, Obtain a relationship between  $V_x$  and  $V_y$ .
- ii) Obtain an expression for  $V_{out}$  as a function of  $V_{in}$



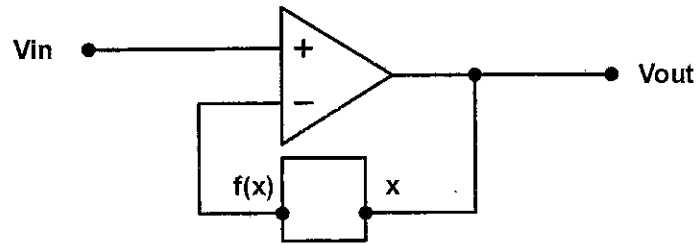c) Consider the following circuit. A hidden circuit is represented by the square. It will output  $f(x)$  voltage when input voltage is  $x$ . If  $f(x) = x^2$  Obtain an expression for  $V_{out}$  as a function of  $V_{in}$



6)

In the following circuit,  $D_1$  is a silicon diode with 0.6V potential barrier and  $D_2$  is a Germanium diode with 0.3 V Potential barrier. ( $V_1 = 1.5 V$ ;  $R_1 = 15 \Omega$ ;  $R_2 = 100 \Omega$ )


a) Calculate the current through

- i)  $D_1$  Diode
- ii)  $D_2$  Diode
- iii)  $R_1$  Resistor

b)  $R_2$  resistor was changed to  $10 \Omega$  Calculate the current through

- i)  $D_1$  Diode
- ii)  $D_2$  Diode
- iii)  $R_1$  Resistor

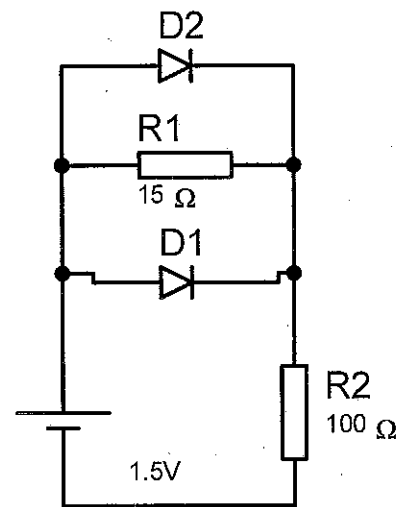c) Draw and label the internal structure of a JFET transistor



-END -