



Date: 17.08.2013

Time: 0930-1230

*This paper consists of two parts: **part A** and **part B**.*

***Part A** contains five questions and **part B** contains three questions.*

*Answer any **three (3)** questions from **part A** and any **two (2)** questions from **part B**.*

**PART – A**

**Q1**

- a) Discuss merits and demerits of an auto-transformer when compare with two winding transformer. (4 marks)
- b) A 2500 V/250 V, 25 kVA transformer has a core loss of 150W and full load copper loss of 300W. If the transformer delivers full load at 0.8 power factor lagging calculate the efficiency. (6 marks)
- c) The above transformer is now connected as an autotransformer to give 2500V/2750V.
  - i. Determine the rating of auto-transformer
  - ii. Calculate efficiency at rated load with 0.8 power factor lag
  - iii. Compare the rating and efficiency with two winding transformer and give your comment.

(10 marks)

**Q2**

- a) Briefly explain the types of distribution systems available (6 marks)
- b) What are the most important factors in a good AC distribution system? (6 marks)
- c) A three-phase, delta connected, 50 Hz, 415V AC motor, develops power of 30 kW.  
The efficiency of motor is 87% and a power factor equals to 0.8. Calculate:
  - I. line current
  - II. phase current


(8 marks)

**Q3**

- a) Use power triangle to explain terms “active”, “reactive” and “apparent” power. What are the unit of measurement of above quantities (4 marks)
- b) What are the causes of poor power factor? Explain the disadvantages of having poor power factor (5 marks)
- c) Explain the use of static capacitors in improving power factor. (4 marks)
- d) A three-phase 5kW induction motor has a power factor of 0.7 at full load. Determine the kVAr rating of the capacitor that is to be connected in parallel with the motor to improve the power factor up-to 0.9. (7 marks)

Q4

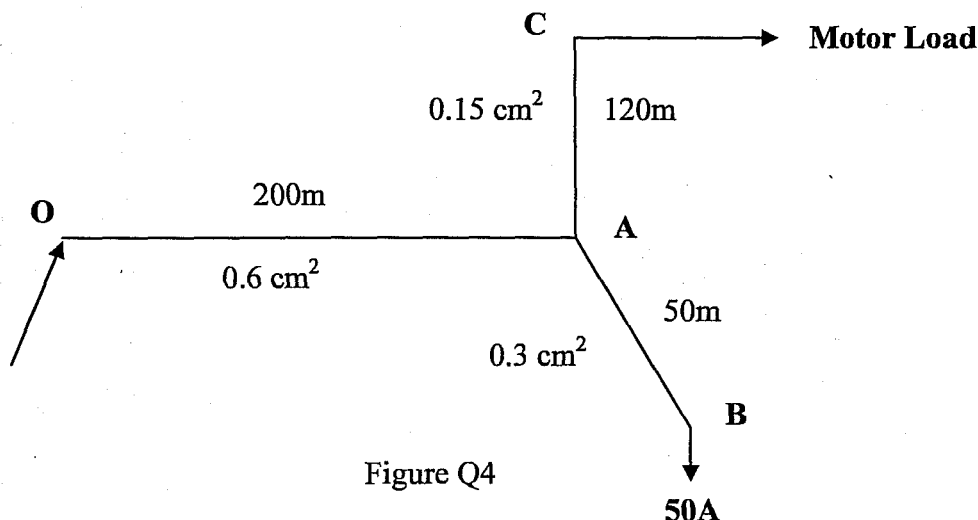- a) Briefly explain the types of DC distribution system? (5 marks)
- b) What are the merits and demerits of DC distribution system in comparison with AC distribution system? (5 marks)
- c) XYZ industrial factory has DC distribution system with copper cable as shown in figure Q4. The load B consumes current of 50A. At point C a motor is connected which is running at full load. The motor voltage is 230V and the voltage at point B is 235V. Determine the motor load current and the supply end voltage. Assume copper cable resistivity as  $1.73 \mu\Omega \cdot \text{cm}$  (10 marks)



Q5

- a) State the classification of industrial drivers. (3 marks)
- b) State the important factors affecting the selection of industrial drivers. (4 marks)
- c) What are the advantages of industrial drivers? (3 marks)
- d) What are the different types of DC motors? Explain their applications. (5 marks)
- e) Draw the mechanical characteristic of all types of DC motors in the same diagram (3 marks).
- f) Explain the advantages of electrical braking methods over mechanical braking. (2 marks)

### PART – B

- Q6. (a) Draw the  $I - V$  characteristic curves for a (4Marks)
- Practical diode
  - Ideal diode
- (b) Consider the following circuit.

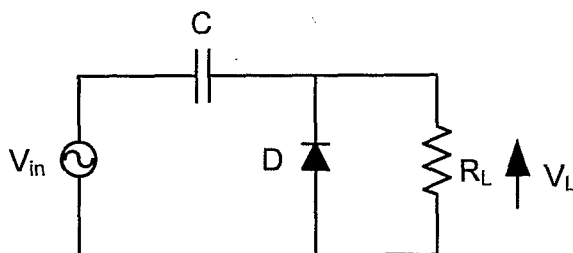


Fig-Q6 (b)

Assume the diode to be a silicon diode and the capacitor behaves ideally. If a sinusoidal signal  $V_{in} = (2 \sin 20\pi t) \text{ Volts}$  is supplied at the input, draw the waveform of  $V_L$ . (You have to clearly show all the important values in your plot.) (8Marks)

- (c) The transistor in the circuit in Fig-Q6 (c) is having a common emitter current gain of 100. Find  $I_B$ ,  $I_C$  and  $V_{CE}$ . (8Marks)

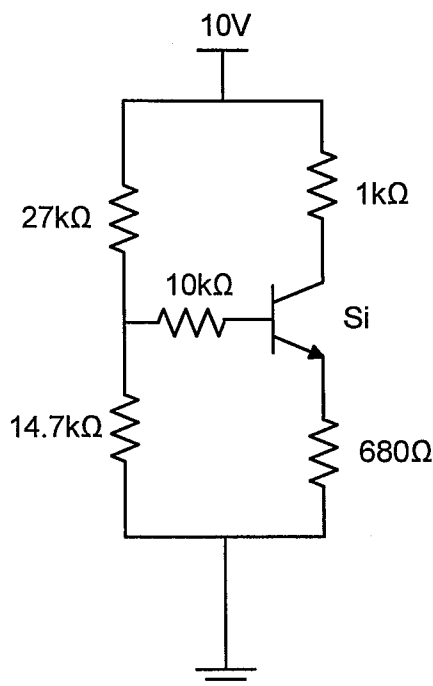


Fig-Q6 (c)

- Q7. (a) Write down three assumptions that you would make for an idea operational amplifier. (3Marks)

(b)

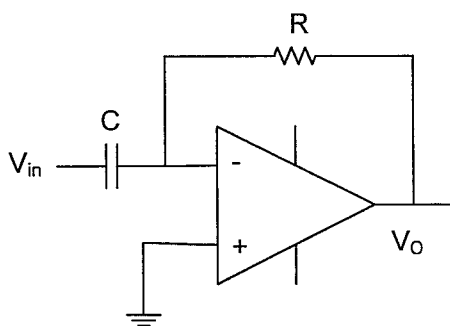


Fig-Q7 (b) i

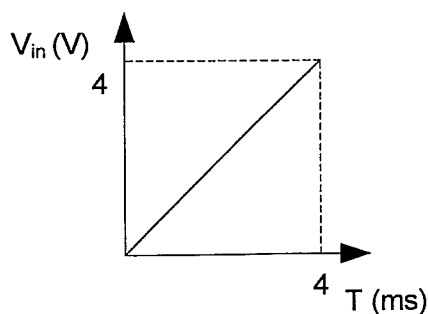


Fig-Q7 (b) iii

- Derive the input-output relationship for the above circuit. (6Marks)
- What is the main function of the above circuit? State one practical application of this circuit. (4Marks)
- If a ramp signal shown in fig 7 (b)iii is applied as the input, draw the output waveform. ( $R = 330\Omega$  and  $C = 100\mu F$ ) (4Marks)

- (c) Briefly discuss the applications of FETs stressing why BJTs are not suited for these applications. (3Marks)

**Q8.**

- (a) Differentiate combinational and sequential logic circuits. (3Marks)
- (b) You are assigned to design a combinational logic circuit to input a four bit binary number and to output logic "1" only if the input number is a prime number (can be exactly divided only by 1 or by itself).
- i. Draw the truth table. (4Marks)
  - ii. Draw the Karnough map. (3Marks)
  - iii. Provide the simplified Boolean expression. (3Marks)
  - iv. Show the circuit in terms of common logic gates. (3Marks)
- (c) What is the advantage of implementing logic circuits in terms of NOR or NAND gates only? Convert the above circuit in (b) iv. to NOR logic. (4Marks)