



Date: 12.08.2014

Time: 1330 – 1630 hrs

Answer any five questions

1.

- Draw the Characteristic curve of a Germanium (Ge) diode. [4 marks]
- Differentiate between Tunnel diode, Zener diode and Varactor diode. [3 marks]
- A diode application and the capacitance characteristic curve of that diode are shown in figure 1.1 and figure 1.2 respectively.

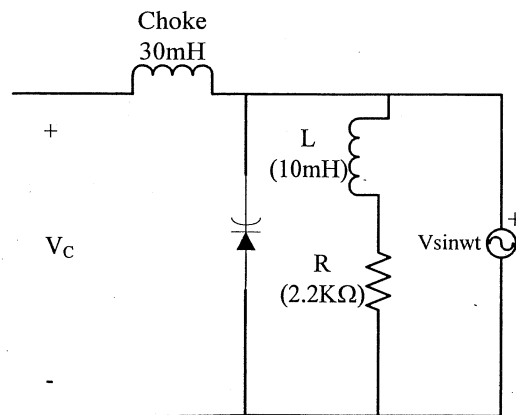


Figure 1.1

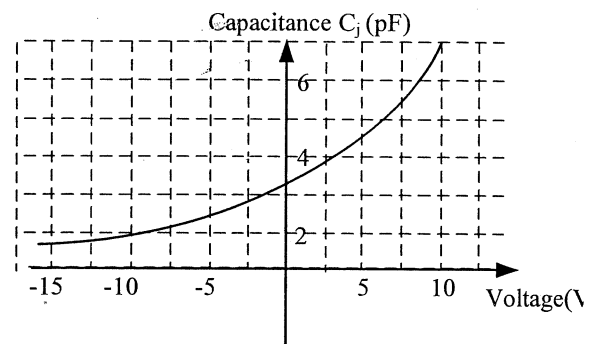


Figure 1.2

- Identify the special purpose diode used in figure 1.1. [1 marks]
  - Write the purpose of choke and the function of the diode. [2 marks]
  - What is the capacitance value, if the biased voltage is 10V? [2 marks]
- d. A thyristor circuit is shown in figure 1.3. Thyristor specifications are as follows.
- Gate voltage 3V
  - Gate current 10mA
  - Forward voltage of the thyristor 1V

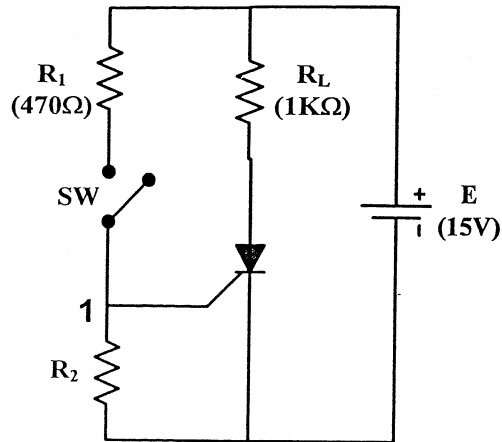


Figure 1.3

- i. Explain the operation of the circuit when the switch (SW) is closed.

[3 marks]

Calculate,

- ii. the  $R_2$  resistor.

[3 marks]

- iii. the power consumption of  $R_L$ .

[2 marks]

2. A student is working with a single phase line. He needs to make a stabilized power supply.

- a. Name the basic methods of rectification.

[2 marks]

- b. Differentiate between capacitor filter, inductor filter and inductor-capacitor filter.

(note: ripple factor is also needed to be considered)

[6 marks]

- c. A regulator circuit is given in figure 2. Circuit consists with a Si transistor and a 7V Zener diode. Current gain of the transistor is 40. Maximum dissipation of the Zener and the minimum current via the Zener is 0.125W and 0.1mA.

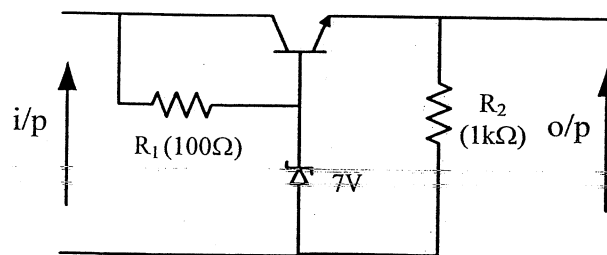


Figure 2

- i. Explain the effect to the output voltage, if the input voltage varied to 10V – 15V.

[4 marks]

- ii. Write the purpose of  $R_1$  resistor.

[2 marks]

- iii. Calculate the output current range for this circuit.

[4 marks]

- iv. Suggest a modification to change the output voltage to 5V.

[2 marks]

3. An emitter follower circuit is shown in figure 3. A silicon transistor with a current gain of 100. (Note: equations and steps need to be included)

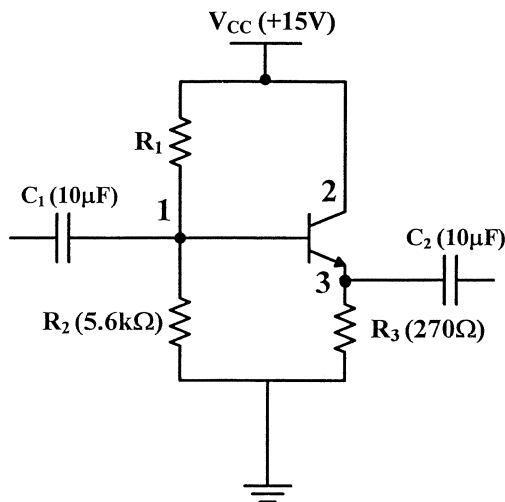


Figure 3

- Write the configuration of the circuit shown in figure 3. [2 marks]
- Calculate the  $R_1$  value, if the base voltage is 3V. [3 marks]
- Find the voltages of test point 2 and 3 in the circuit. [2 marks]
- Calculate the base current and the emitter current of the transistor. [4marks]
- Draw the DC load line for the circuit. [4 marks]
- Comment on the stability of the amplifier in figure 3. [5 marks]

4.

- Write the output of the logic circuit shown in figure 4. [2 marks]

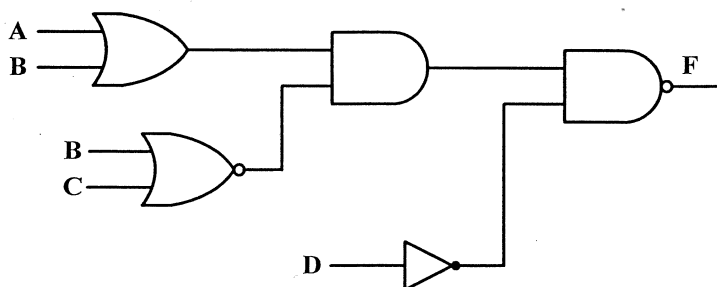


Figure 4

- Simplify the Boolean function of the logic circuit shown in figure 4. [2 marks]
- With a Karnaugh map simplify the function  $f(A,B,C,D) = \{2,3,5,7,10,11,13,15\}$  [5 marks]
- Draw the circuit diagram using only NAND gates for the function obtained in 4. c. [5 marks]
- Convert the followings,
  - 2510 to binary
  - 15010 to hexadecimal
  - 20 to 1's complement
  - 45 to 2's complement

[6 marks]

5.

- a. What is the main difference between combinational logic and sequential logic?  
[2 marks]
- b. Eight complimentary flip flops are connected in series to the form an electronic counter. Calculate the maximum number that the counter memorize.[3 marks]
- c. A 5 kHz square pulse train clock signal is fed to the input X. Draw the outputs of the JK flip flops related to input signal (X) shown in figure 5. (Note : use a graph sheet)  
[6 marks]
- d. Tabulate the truth table for the design and suggest a method to reset the circuit after all the LED bulbs light together.  
[9marks]

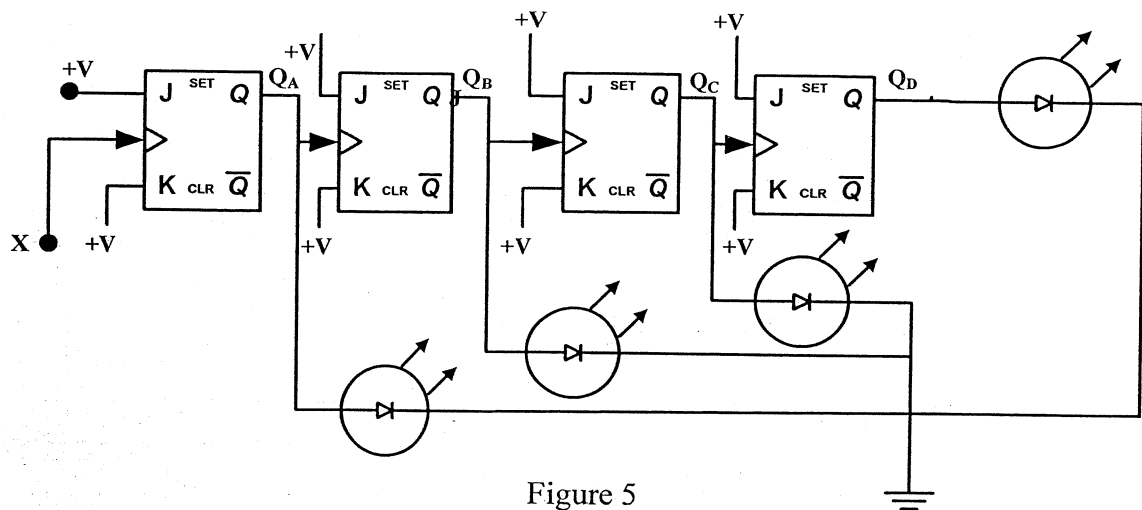


Figure 5

6. A Single stage transistor amplifier circuit is shown in figure 6.

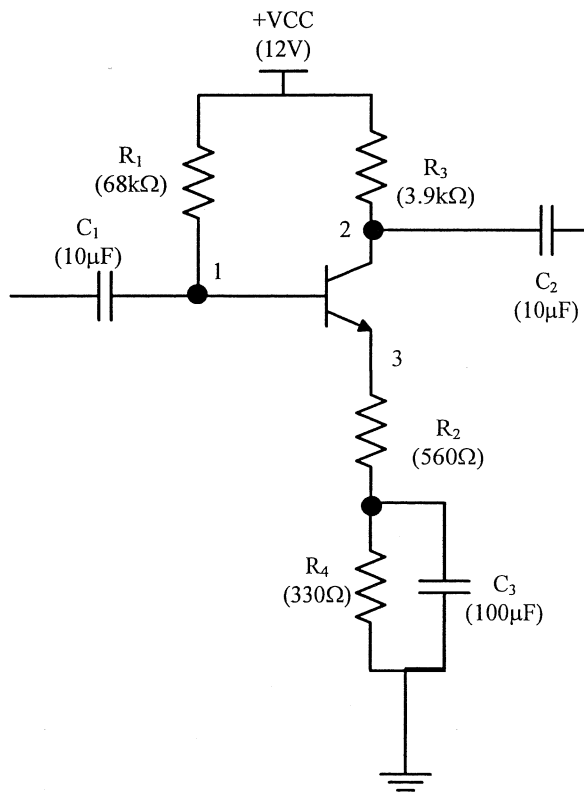


Figure 6

- Draw the h parameter model for the transistor considering the following parameters.  $h_{ie} = 2.2k\Omega$ ,  $h_{fe} = 50$  and neglect the effect of  $h_{re}$  and  $h_{oe}$ . [3 marks]
- Using the above drawn transistor model, draw an AC equivalent circuit for the amplifier circuit shown in figure 6. [5 marks]
- Derive an expression for
  - Input impedance
  - Current gain
  - Voltage gain
  - Output impedance
  - Power gain
 [12 marks]

7.

- Compare and contrast the bipolar and unipolar transistors. [5 marks]
- State the operating regions of JFET and give applications for each region. [4 marks]
- A JFET amplifier is shown in figure 7. The drain current of the JFET can be obtained using the  $I_{DSS}[5 + V_{GS}]^2$  equation.  $I_{DSS} = 10mA$ .

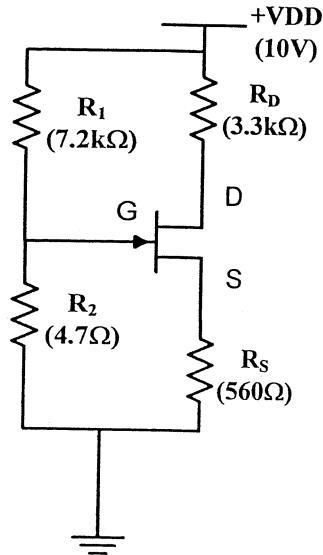


Figure 7

Calculate the,

- i. Voltage at the Gate terminal [2 mark]
- ii. Gate-Source voltage [6 marks]
- iii. Drain current. [3 marks]

8.

a. An operational amplifier circuit is given in figure 8.1.

- i. Derive the transfer function of the amplifier. [5 marks]
- ii. Calculate the output voltage, if the  $V_{in}$  is a 2V sinusoidal signal. [2 marks]
- iii. Draw the output waveform with reference to the input. [2 marks]
- iv. Write the function of the circuit in figure 8.1. [1 marks]

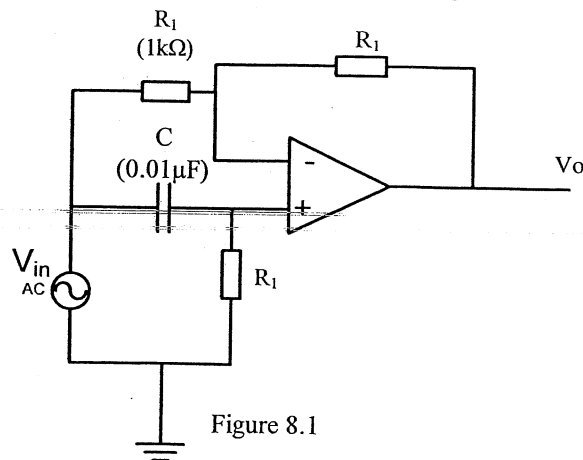


Figure 8.1

b. An uni junction transistor circuit is given in Figure 8.2.

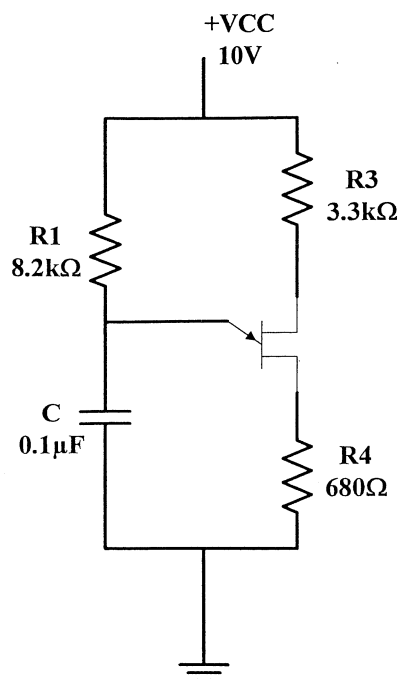


Figure 8.2

- i) Calculate the frequency oscillation. [4 marks]
- ii) Draw the output signal of the oscillator (Note: mark all the necessary voltages and the time period of the signal.) [6 marks]