

The Open University of Sri Lanka
 Department of Electrical and Computer Engineering
 Bachelor of Technology (Engineering) – Level 3
 ECX 3231 – Electrical Circuits and Measurements
 Academic Year 2014/2015
 Final Examination



Date: 26 - 08 - 2015

Closed Book
 Time: 13:30 – 16:30

This question paper consists of eight questions on five pages. Answer **any five** questions. All questions carry equal marks.

Q1. Consider the circuit given in figure 1. The switch S_1 is closed at $t = 0$ s (Before closing the switch the circuit is at neutral state)

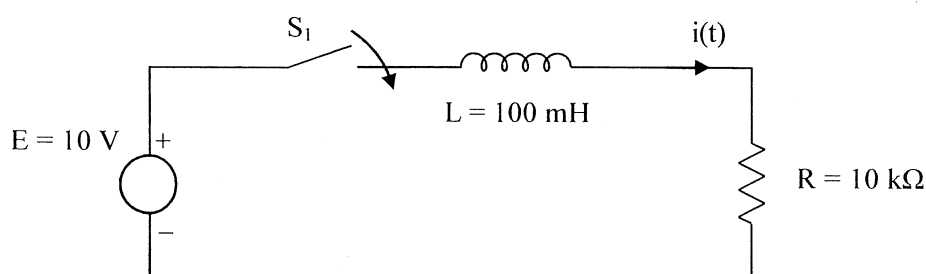


Figure 1

- i. Write the differential equation to find the current through the circuit after closing the switch. (2 marks)
- ii. Convert the differential equation written in (i) in to s – domain using Laplace Transform and obtain an expression for the impedance function $Z(s)$ which is also in s – domain. (5 marks)
- iii. Find the solution for current through the circuit in s – domain $I(s)$. (4 marks)
- iv. Using inverse Laplace transform, derive the expression for current through the circuit in time domain $i(t)$. (5 marks)
- v. Using the expression derived in step (iii) above, obtain the natural response of the circuit in time domain. (4 marks)

Q2. Consider the RLC circuit shown in figure 2. At $t = 0$ the switch S_1 is closed. (Before closing the switch the circuit is at neutral state)

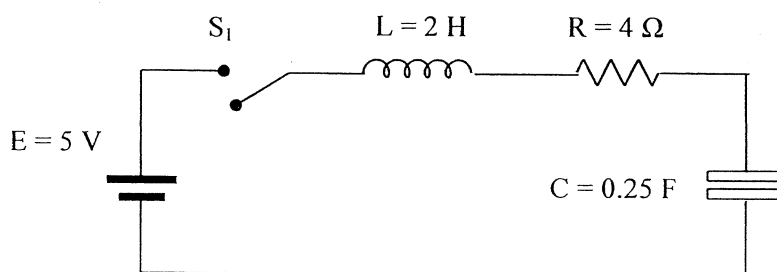


Figure 2

- Write a differential equation relating voltages across each element using Kirchhoff's voltage law. Assume that the capacitor is initially fully discharged. (5 marks)
- Solve the differential equation found in (i) and obtain an expression for the current through the circuit for $t > 0$. (consider the initial voltages across and currents through each element) (12 marks)
- State the type of the response of this circuit. (3 marks)

Q3. A simplified equivalent circuit diagram of a transmission line is shown in figure 3.

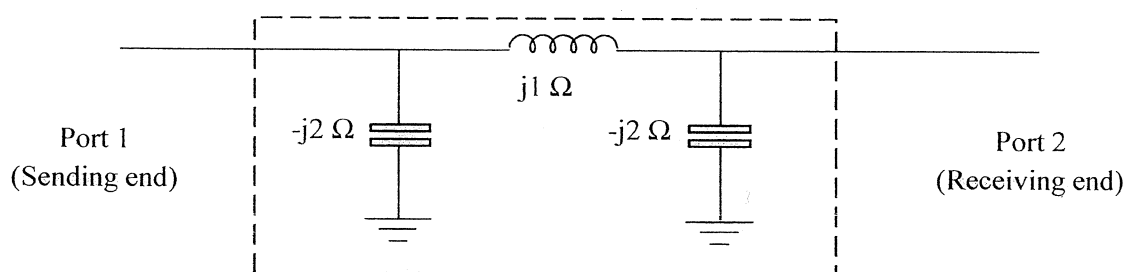


Figure 3

- Considering that the circuit as a two port network, find the ABCD parameters of the network. (8 marks)
- Using the parameters found in (i), write the terminal characteristic equation in matrix form. (4 marks)
- Now an AC generator with internal impedance of $2/\sqrt{3} \Omega$ is connected to the sending end while a load of $2/\sqrt{3} \Omega$ is connected to the receiving end. If the voltage at the load is to be maintained at $100 V_{RMS}$, determine the magnitude and phase angle of sending end voltage (which is port 1). (8 marks)

Q4. Pole zero maps of three different impedance functions $Z(s)$ are shown in figure 4.
(Locations of poles and zeros are not to scale)

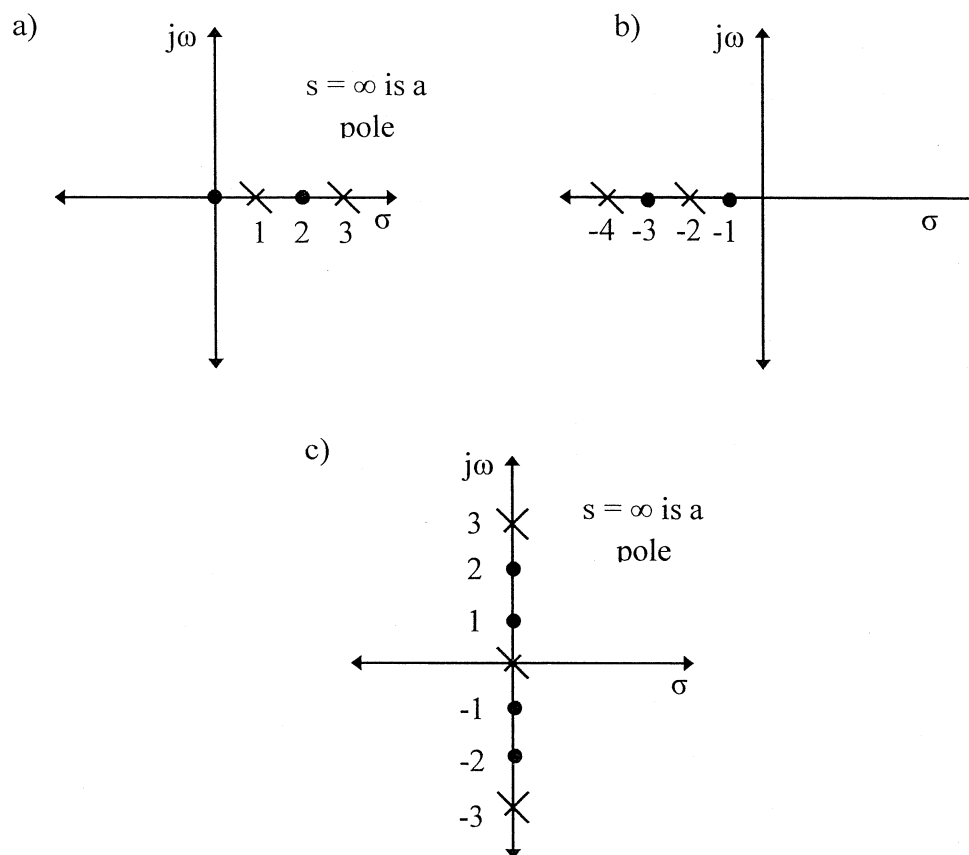


Figure 4

- i. State which of the above system/s are realizable in the form of RC, RL or LC. Give reasons for each. (2 marks)
- ii. Formulate the driving point impedance function for the realizable system/s that you have figured out. (4 marks)
- iii. Realize each network that you have figured out in part ii. using:
 - a. Foster 1st form
 - b. Cauer 1st form(14 marks)

Q5. Select **any four** topics from the following list and write a short note for each. Limit each of your short notes to a maximum of 100 words. (4 × 5 = 20 marks)

- i. Use of guard terminal in insulation testers. (You are required to draw a sketch)
- ii. Loss of charge method for high resistance measurement.
- iii. Importance of measurement of contact resistance.
- iv. Principle of operation of single ramp type analog to digital converter.
- v. Use of X-Y mode of the oscilloscope to plot the V-I characteristics of a rectifier diode. (You are required to draw a sketch of the connection diagram)
- vi. Selection of variable components of an AC bridge circuit to obtain the balance condition effectively.

Q6.

- i. Briefly describe a method used to measure magnetic flux density. (4 marks)
- ii. Define the term "Dielectric loss". Briefly explain how it affects the operation of an electrical circuit. (4 marks)
- iii. Explain the method of measuring capacitance and loss factor of an insulating material using Schering Bridge. (12 marks)

You may include,

- (a). Circuit diagram
- (b). Balance equations
- (c). Assumptions made

Q7.

- i. List down two real world examples where the measurement of insulation is important and write what are the benefits of measuring insulation for each example. (4 marks)
- ii. A certain coil of PVC insulated single core cable which is having a length of 100 m has been given for quality testing. You are required to measure the insulation of the full length of wire.
 - (a). Draw a sketch of the experimental setup to measure the insulation of the wire. (Physical view). (5 marks)
 - (b). Draw the simplified circuit diagram of the experimental setup. (4 marks)
 - (c). List down two assumptions made during the experiment. (4 marks)
 - (d). Write the equation to calculate the insulation. (Use standard notation) (3 marks)

Q8.

- i. Define following terms regarding a digital voltmeter.
 - (a). Accuracy
 - (b). Resolution (4 marks)
- ii. Briefly explain how the internal impedance of a voltmeter can change the readings from the actual values. You may use appropriate circuit diagram. (4 marks)
- iii. The output voltage of a power supply circuit has been observed using an oscilloscope. The observed waveform pattern is given in figure 5. (12 marks)

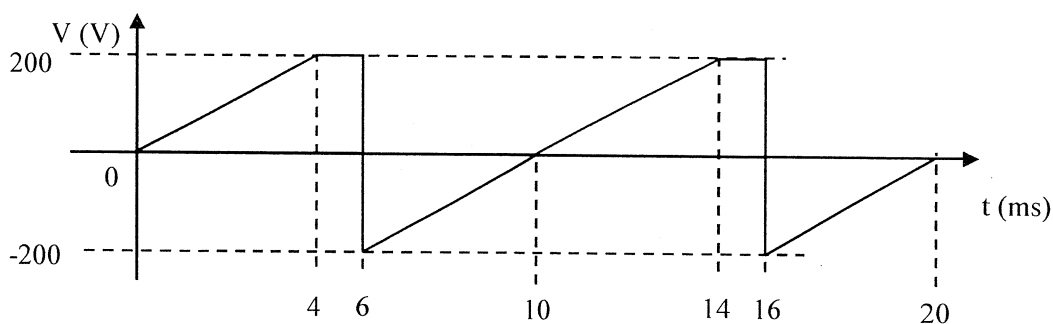


Figure 5

Calculate the voltmeter RMS reading if the output has been measured using an Average responding voltmeter. You may assume the internal impedance of the voltmeter as infinite.