

The Open University of Sri Lanka
 Department of Electrical and Computer Engineering
 ECX4150 –Electronics II
 Final Examination – 2014/2015



Date: 2015-08-07

Time: 0930-1230

This paper has two sections. Answer five questions selecting at least one question from Section B.

Adhere to the usual notations.

Section A

Q1.

 


Figure –Q1

Let,

$$h_{ib} = 15\Omega \quad R_1 = 1k\Omega \quad V_{CC} = 10V \quad -V_{DD} = -15V$$

$$R_2 = 50\Omega \quad h_{fb} = -0.992 \quad R_3 = 9.1k\Omega \quad R_L = 22k\Omega$$

- Draw the h-parameter equivalent circuit of the circuit arrangement in the above Figure-Q1. (8Marks)
- Find r_{in} and r_o . (6Marks)
- Calculate $\frac{v_L}{v_s}$. (6Marks)

Q2.

- Tabulate two similarities and two differences in Thyristor and a Triac. (4Marks)
- The power delivered to a load is controlled by a Thyristor. Figure-Q2 shows a Thyristor circuit.

 


Figure –Q2

- Explain the operation of the circuit shown in figure-Q2. (3Marks)
- Sketch the waveform across the load with reference to the input signal.
(3Marks)
- Calculate the power delivered to the load? (4Marks)
- Comment on the delivered power to the load, if the Thyristor is replaced with a Triac.
(6Marks)

Q3.

- Show the output waveforms and conduction angles of different classes of power amplifiers. (6Marks)
- Class B power amplifiers provide a better efficiency than Class A. Discuss a main disadvantage of Class B over Class A. Further discuss a method to overcome the above disadvantage. (5Marks)
- A Class B push-pull power amplifier delivers $16W$ to a 8Ω load. It uses a $\pm 20V$ DC power supply. Determine,
 - Peak current drawn from each supply. (2Marks)
 - Total power supplied to the circuit. (2Marks)
 - Power efficiency. (2Marks)
 - Maximum power dissipation capability for each transistor. (3Marks)

Q4.

- a. List the advantages of field effect transistors over bipolar junction transistors. (4Marks)
- b. Consider the circuit shown in figure-Q4. I_{DSS} and pinch off voltage of the JFET is 12mA and -3V respectively.

 


Figure-Q4

- What is the amplifier configuration used in this circuit? (2Marks)
- Find the gate source voltage, when no input signal is applied. (6Marks)
- Hence find the Drain current of the channel. (4Marks)
- Draw the ac equivalent circuit for the figure-Q4 and derive the voltage gain of the circuit. (4Marks)

Q5.

- a. List three characteristics of an ideal operational amplifier. (3Marks)

- b. An operation amplifier circuit shown in figure-Q5.

 


Figure-Q5

- i. Derive a function relating V_{in} and I_L . (8Marks)
- ii. Name the operation of the circuit in figure-Q5, using the derived function in 5.b.i (4Marks)
- iii. If $\frac{R_1}{R_2} = \frac{R_3}{R_4}$, calculate the output signal, for $V_{in} = 2\text{ V}$. (5Marks)

Section B

Q6.

- a. Show how you use a JK flip flop to form a D flip flop and give its truth table. [4marks]
- b. Figure 6 shows a circuit forms of a D flip flop and combinational logic gates.

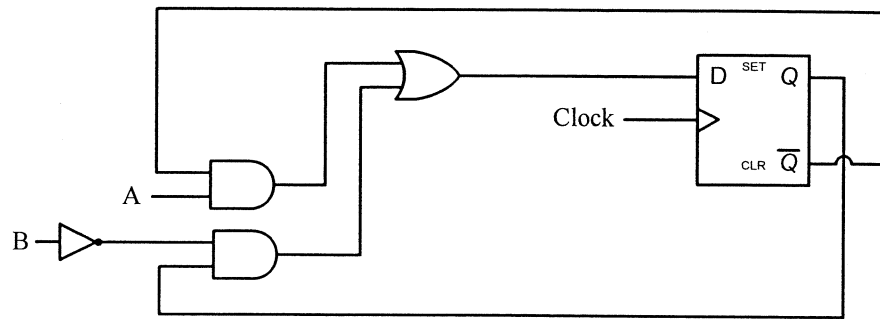


Figure 6

Derive truth table for this circuit (figure 6) and identify the operation. [6marks]

- c. Draw the state diagram for the 3 bit down counter using D flip flop.
- Write the truth table for the design. [5marks]
 - Draw the circuit using flip flop and logic gates. [5marks]

Q7.

- a. Simplify the following functions using Boolean algebra
- $F_1 = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC\overline{C}$ [2 marks]
 - $F_2 = \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + \overline{A}BCD + AB\overline{C}\overline{D} + AB\overline{C}D + ABC\overline{D} + ABCD$ [2 marks]
- b. Simplify the following logic function using Karnaugh map.
- $f(A, B, C, D) = (1, 5, 9, 10, 11, 13, 14, 15)$ [3 marks]
 - $f(A, B, C, D) = (0, 1, 2, 5, 6, 7, 8, 9)$ [3marks]
- c. Implement the simplified logic function obtained in
- (Q7.a.i) using two input NAND gates. [5 marks]
 - (Q7.a.ii) using two input NOR gates. [5 marks]

Q8. Design a synchronous binary counter that counts the sequence $0 \rightarrow 1 \rightarrow 3 \rightarrow 7 \rightarrow 5 \rightarrow 9 \rightarrow 0$.

Design the synchronous counter, considering all other values, other than those given in the sequence cannot occur. Draw the relevant circuit using JK flip-flops and any other required gates.

[20 marks]