



FINAL EXAMINATION - 2015/2016

ECX3150 – Electronics I

(Closed Book)

Answer any five questions.

Date 16.11.2016

Time: 09:30-12:30 hrs.

- Q1. (a) Considering the behavior of the P-N junction in reverse and forward biased modes derive the characteristic curve of a diode. (4Marks)
- (b) Consider the circuit in Figure Q1 where Z is a Zenner diode with a breakdown voltage of 5.7V and a D near-ideal Si diode with a forward voltage drop of 0.7V.

 


Figure Q1

- Let switch (S) be open initially. Calculate the voltage across the load resistance R_L . (4marks)
- Calculate the voltage across load resistance R_L when S is closed. (4marks)
- Calculate the current through R_L when S is closed. (2marks)
- Hence calculate the current flowing through the Zenner diode. (6marks)

Q2. Consider the DC power supply circuit in Figure Q2.

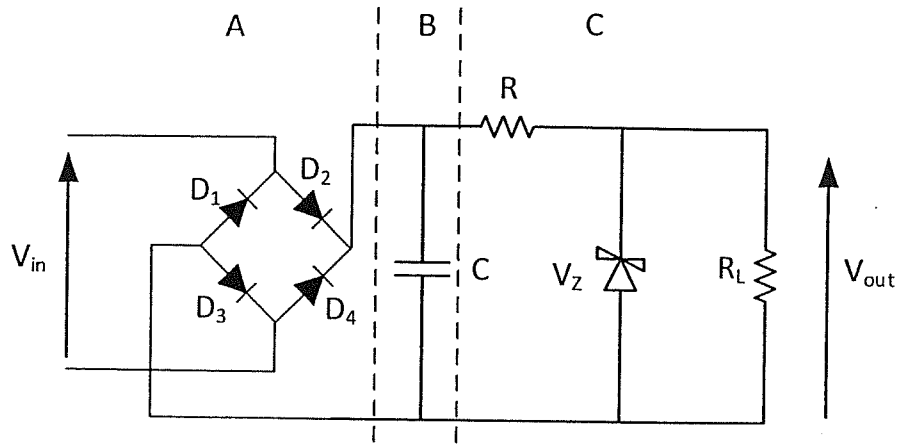


Figure Q2

Let $D_1 \sim D_4$ are identical Si diodes with a forward voltage drop of $0.7V$ in each. $R = 1k\Omega$, $R_L = 10k\Omega$, $C = 10\mu F$. Zener diode breakdown voltage $V_Z = 5.1V$. V_{in} is a sinusoidal voltage with a peak amplitude of $9V$.

- Identify the three distinct sub-circuits A, B and C. (3Marks)
- Assuming that minimum output value of the section B is $6.1V$, draw the output waveforms at the outputs of each A, B and C. (6Marks)
- Calculate the minimum and maximum currents flowing through the Zener diode. (8Marks)
- Hence calculate the minimum power rating of the Zener diode. (3Marks)

Q3. The single stage BJT transistor amplifier circuit shown in Figure Q3 consists of a Si transistor ($V_{be} = 0.7V$) with a current gain, $\beta = 100$.

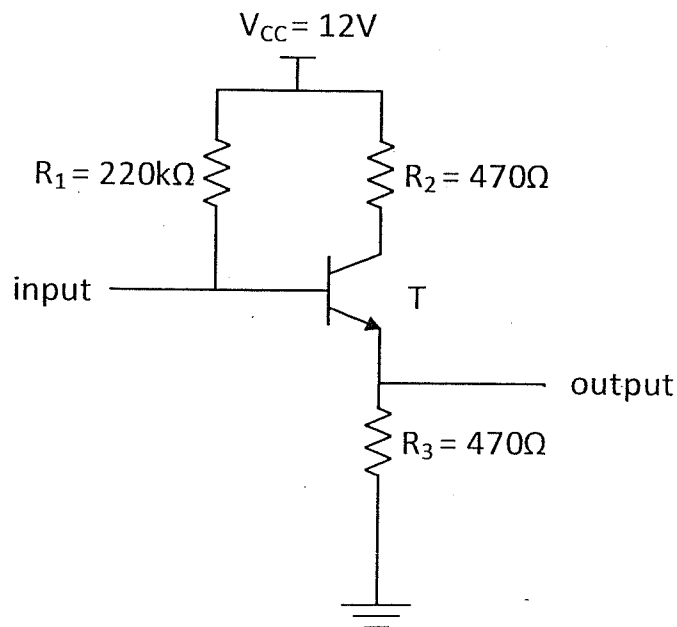


Figure Q3

- (a) Write the bias configuration of the circuit shown in Figure Q3. (2Marks)
 (b) Calculate the base, collector and emitter currents of the transistor. (6Marks)
 (c) Hence calculate the V_{CE} voltage. (4Marks)
 (d) Draw the DC load line for the circuit. (6Marks)
 (e) Hence, comment on the stability of the amplifier in Figure Q3. (2Marks)

Q4. Figure Q4 shows a FET based cooling fan motor (M) driver circuit. T is a thermistor which decreases its resistance when the temperature is increased and vise-versa.

 
 
 
 


Figure Q4

- (a) Using a clear diagram, explain the phenomena of *pinch-off* in a JFET. (5Marks)
 (b) What is the bias configuration used in this circuit in Figure Q4? (2Marks)
 (c) If the pinch-off voltage of the FET (Q) in Figure Q4 is 3V and $I_{DSS} = 12mA$, calculate the drain - source current through the FET for thermistor resistances of
 i. 100Ω
 ii. 333.33Ω
 iii. $1k\Omega$. (3x3marks)
 (d) Hence explain the behavior of the FET (Q) when the temperature changes from 30 to 60 degrees (as a result resistance changes from $1k\Omega$ to 100Ω) (4Marks)

**Figure Q5 (a)****Figure Q5 (b)****Figure Q5 (c)**

- (a) List four properties of an ideal operational amplifier. (4Marks)
- (b) Derive an expression for the $\frac{V_o}{V_i}$ in the ideal operational amplifier based circuit in Figure Q5 (a). (6Marks)
- (c) Let $R_1 = 2.2k\Omega$ and $R_2 = 4.7k\Omega$. Draw the output waveforms with respect to the input signals given in Figures Q5 (b) and Q5 (c). (2x5Marks)

Q6.

(a) Perform the following conversions.

- i. 9.75_{10} to binary
- ii. 0.2_{10} to binary
- iii. $CC.F_{16}$ to octal
- iv. -23 to 8 bit 2's complement

(4x2Marks)

(b) Find the addition of the two BCD numbers 10010011.0101 and 00110111.0001 .

(4Marks)

(c) Perform the calculation 12-15 in 8 bit 2's complement arithmetic.

(4Marks)

(d) Using binary division, divide 100011_2 by 110_2 .

(4Marks)

Q7.

(a) Using a truth table, prove the Boolean identity $ABC + AB\bar{C} + A\bar{B}\bar{C} + A\bar{B}C = A$

(4Marks)

(b) Using De Morgan's theorem prove following identities.

- i. $AB + \bar{B}C = \overline{(\bar{A} + \bar{B})(B + \bar{C})}$ (3Marks)
- ii. $(\bar{A} + \bar{C})(B + \bar{C})[A + B(\bar{B} + \bar{C})] = AC + \bar{B}C + \bar{A}(\bar{B} + BC)$. (4Marks)

(c) Implement the Boolean function $F = (A + \bar{B})(\bar{C} + D)$ using

- i. NOT, AND and OR gates
- ii. NAND gates only
- iii. NOR gates only.

(3x3Marks)

Q8.

(a) A three variable Boolean logic expression is given by $E = \prod M(2,4,6)$. Using Karnaugh maps find,

- i. minimum POS and
- ii. minimum SOP expressions.

(10Marks)

(b) Construct Karnaugh maps for the expression $F = ABC + \bar{A}BC + AB\bar{C}$ and find

- i. minimum SOP and
- ii. minimum POS expressions.

(10Marks)