



The Open University of Sri Lanka  
Department of Electrical and Computer Engineering

ECX3210 – Electro-Technique

Final Examination 2015/2016

Closed Book Test

Date: 22<sup>nd</sup> November 2016

Time: 13.30-16.30

Answer any 5 out of 8 questions provided. All questions carry equal marks. Show all relevant steps of calculation.

- 1)
  - a. What is the resistance range of a resistor displaying colour bands Violet, Green, Black, Gold?
  - b. The potential difference across the terminals of a battery is 8.4 V when there is a current of 1.5 A in the battery from the negative to the positive terminal. When the current is 3.5 A in the reverse direction, the potential difference becomes 9.4 V.
    - i. What is the internal resistance of the battery?
    - ii. What is the emf of the battery?
  - c. An electric teakettle has a multi-position switch and two heating coils. When only coil 1 is switched on, the well-insulated kettle brings a full pot of water to a boil in 1 minute. When only coil 2 is switched on, it requires 2 minutes to boil the same amount of water. Find the time interval required to boil the same amount of water if both coils are switched on
    - iii. in a parallel connection      and
    - iv. in a series connection.
- 2)
  - a. Describe briefly the two Kirchhoff's Laws of electric circuits, indicating the underlying conservation laws.
  - b. In the circuit of fig. Q2 find the magnitude and direction of the current flowing in wire between points **b** and **c**.

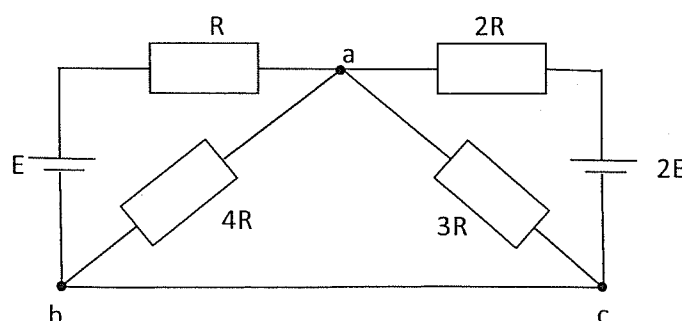



Figure Q2

$E = 250 \text{ V}$

$R = 1 \text{ k}\Omega$


- 3) a. Describe Lenz's Law of induction.
- b. Two small spheres, each of mass 2 g, are suspended by light strings 10 cm in length and a uniform electric field is applied as shown in Fig Q3. The spheres have charges equal to  $-5 \times 10^{-8}$  C and  $+5 \times 10^{-8}$  C. Determine the magnitude and direction of the electric field that enables the spheres to be in equilibrium at an angle of  $\theta = 10^\circ$  to the vertical.

Figure Q3

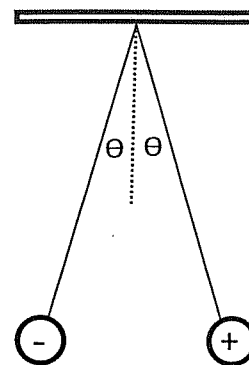

- c. A proton moving in a circular path perpendicular to a constant magnetic field takes 1 ns to complete one revolution. Determine the magnitude of the magnetic field. Neglect any gravitational effects. [ $m_p = 1.67 \times 10^{-27}$  kg,  $+p = 1.6 \times 10^{-19}$  C]
- 4) a. A capacitor has vacuum in the space between the conductors. If you double the amount of charge on each conductor, what happens to the capacitance?
- b. An isolated capacitor of unknown capacitance has been charged to a potential difference of 100 V. When the charged capacitor is then connected in parallel to an uncharged  $10 \mu\text{F}$  capacitor, the voltage across the combination is 30 V. Calculate the unknown capacitance.
- c. Two capacitors of  $9 \mu\text{F}$  and  $4 \mu\text{F}$  are connected in series with each other and with a DC source of 26 V. Then the charged capacitors are disconnected from the source and from each other, and then reconnected to each other with plates of **opposite** sign together. By how much does the energy of the system change?
- 5) a. A student using an ammeter comments that two AC branch currents, of 3 A and 5 A respectively, combine together at a point to give a total current of 6.6 A. She states that this is a violation of Kirchhoff's current law. What is your opinion? Explain.
- b. For circuit in fig Q5, with  $L = 100$  mH,  $C = 2.5 \mu\text{F}$ , and  $R = 200 \Omega$ , it was found that the admittances of capacitor C and the inductor L have the same magnitude at the angular frequency  $\omega_c$  provided by the sinusoidal source  $e(t)$ . The current  $I_{\text{rms}}$  through the resistor was measured as 12 mA.

Figure Q5

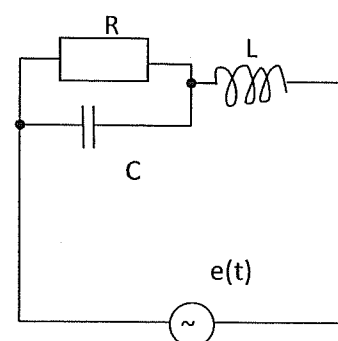

- Calculate the value of  $\omega_c$ .
- Calculate the currents through the other components, taking the current through the resistor as reference.
- State  $e(t)$  in  $E \sin(\omega t + \phi)$  form.
- Sketch the phasor diagram for the circuit to scale based on your calculations.
- What is the power factor of the circuit?

- 6) a. What is the characteristic of a (portion of a) circuit at resonance? Give the primary characteristic only.

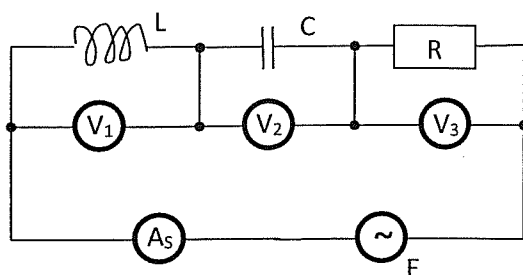


Figure Q6-i

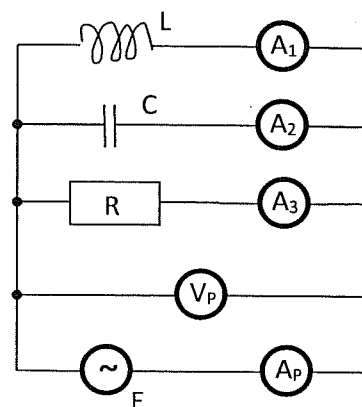


Figure Q6-ii

- b. To investigate series and parallel resonance, you are provided an inductor  $L = 100 \text{ mH}$ , a capacitor  $C = 10 \mu\text{F}$ , a resistor  $R = 200 \Omega$ , a source of variable frequency  $E = 17 \sin(\omega t)$ , and a selection of ideal AC ammeters (A), and voltmeters (V).

First you investigate series resonance by setting-up the circuit in fig Q6-i, and tune the source E to the series resonance angular frequency  $\omega_{SO}$ . Based on your knowledge of resonance calculate /deduce the following values:

- i.  $\omega_{SO}$  ii.  $V_1$  reading iii.  $V_2$  reading iv.  $V_3$  reading v.  $A_s$  reading  
vi. Draw to scale the phasor diagram for the circuit.

Now you investigate parallel resonance by setting-up the circuit in fig Q6-ii, and tune the source E to the parallel resonance angular frequency  $\omega_{PO}$ . Based on your knowledge of resonance calculate /deduce the following values:

- vii.  $\omega_{PO}$  viii.  $A_1$  reading ix.  $A_2$  reading x.  $A_3$  reading xi.  $A_P$  reading xii.  $V_P$  reading  
xiii. Draw to scale the phasor diagram for the circuit.

Show your calculations. In deductions state your justifications clearly.

- 7) a. Sketch and explain the principles of operation of a simple AC generator (dynamo).  
b. How can you transform this (without the help of electronic components/circuits) to a DC generator? Explain.  
c. What is a simple method of increasing the smoothness of the generated DC output? Describe.  
d. Go back to simple AC generator. What is the output of a simple half-wave rectifier when it is connected across the output terminals of the simple AC generator?  
e. Describe the functioning of the bridge rectifier, and compare this to the half-wave rectifier.
- 8) a. Sketch and describe behaviour of diode in a circuit using I-V curve.  
b. Sketch the design for a diode-clipper circuit that clips the input sinusoidal 12 V maximum at 8V at the positive half. Assume use of ideal diodes.  
c. Describe 3 types of common diodes.