

The Open University of Sri Lanka
Faculty of Engineering Technology



Study Programme	: Bachelor of Technology Honours in Engineering
Name of the Examination	: Final Examination
Course Code and Title	: MEX3274 – Electronics, sensors and actuators
Academic Year	: 2016/17
Date	: 25 th November 2016
Time	: 0930hr-1230hr
Duration	: 3 hours

General instructions

1. Read all instructions carefully before answering the questions.
2. This question paper has **eight** questions. All questions carry equal marks.
3. Answer **five** questions only, selecting **at least two** questions each from **part A** and **part B**.

PART A

Question 01

- a) What are the common rectification methods available to convert AC to DC? Briefly explain.
- b) A circuit is to give an output voltage of 5 V from an input voltage of 15 V as shown in the figure Q1-b. If $R_2 = 200\Omega$, calculate the resistance of R_1 .

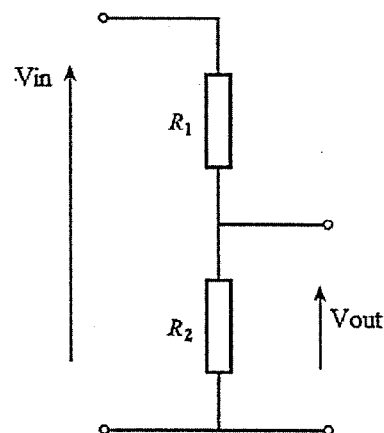


Figure Q1-b

- c) Determine V_X by finding V_{TH} and R_{TH} to the left of A-B using Thevenin's theorem.

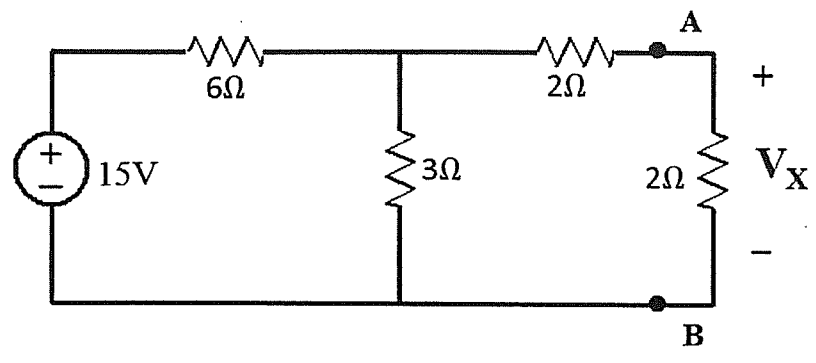


Figure Q1-c

- d) Derive the Norton equivalent circuit using the Thevenin's circuit drawn for the part (c)

Question 02

- a) An alternating voltage signal displayed on oscilloscope screen is shown in figure Q2-a. The signal amplitude control is set to 2 V/ division and time base setting is 5ms/division. Determine;
 - i. Frequency of the signal
 - ii. Peak to peak voltage

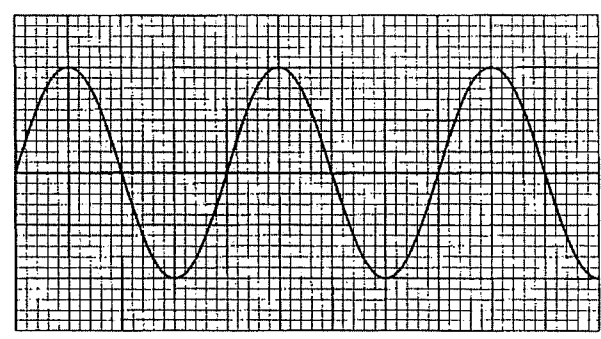


Figure Q2-a

- b) A step-down transformer is required to transform 240 V a.c. to 12 V a.c. If the primary coil has 1000 turns, how many turns should the secondary have? How you can identify the secondary coil using a multi-meter?
- c) An average of 120 kW is delivered to a city which is located 100 km away from the power station. The transmission lines have a total resistance of 4 Ω. Calculate the power loss if the transmission voltage is;
 - i) 230 V
 - ii) 33kV
- d) Determine I_1 and I_2 of the circuit shown in figure Q2-d

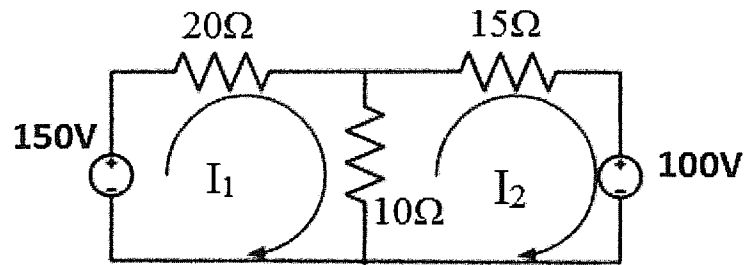


Figure Q2-d

Question 03

- a) Convert (note: clearly show the necessary steps);
- 100111_2 to hexa-decimal and decimal
 - 355_{10} to hexa-decimal and octal
 - $3E_{16}$ to binary and octal
 - 67_{10} to binary coded decimal(BCD)
- b) What is the main significance of two's complement representation of binary numbers?
- c) Determine sign-and-magnitude (8 bit) binary representation of the -43_{10}
- d) Explain how R-2R ladder network is used to convert digital signal to analog.

Question 04

- a) Determine V_B, V_E, I_C and V_C of the BJT circuit shown in figure Q4-a

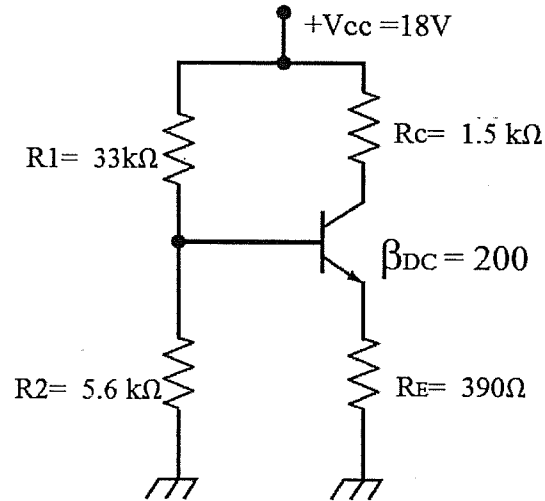


Figure Q4-a

- b) Determine the gain and output voltage of the operational amplifier shown in figure Q4-b, when $R_1 = 10k\Omega$, $R_2 = 100k\Omega$, $V_{in} = 0.2V$.

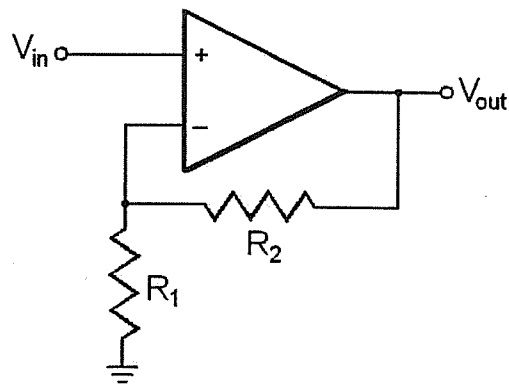


Figure Q4-b

- c) Determine the output voltage of the operational amplifier shown in figure Q4-c, when $R_1=R_2=R_3= 10\text{k}\Omega$, $R_F=20\text{k}\Omega$, $V_1= 1\text{V}$, $V_2=1.5\text{V}$ and $V_3=2\text{V}$.

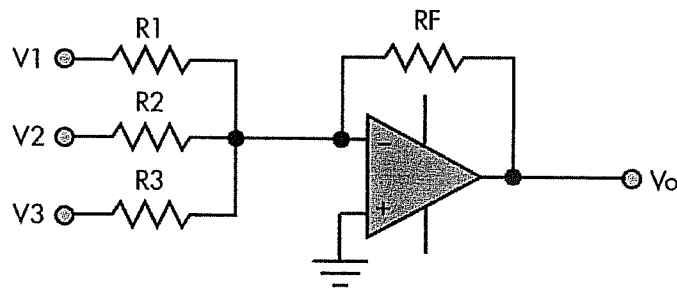


Figure Q4-c

PART B

Question 05

- Distinguish between active sensors and passive sensors. Elaborate with suitable examples.
- Explain the difference between accuracy and precision with respect to sensors with using suitable examples.
- What is a strain gauge? Briefly explain the applicability of such sensor in a practical situation.
- What are the parameters need to determine the resistance change of a strain gauge. Explain with a suitable example.

Question 06

- a) Discuss the advantages and disadvantages of a potentiometer and a linear variable differential transformer (LVDT) with respects to a displacement measurement application.
- b) Figure Q6-b illustrates a cutaway view of an encoder.

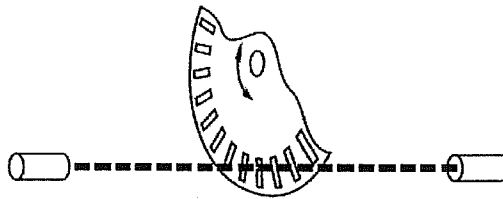


Figure Q6-b

- i. Identify the type of the encoder.
 - ii. State another type of optical encoder and mention the major differences compared to this encoder.
- c) Discuss the differences between inductive, capacitive and optical proximity sensors.

Question 07

- a) Discuss the differences between 'Permanent Magnet' and 'Variable Reluctance' stepper motors.
- b) What are the three step modes which use to operate the stepper motor?
- c) Briefly explain following dc motor types which are categorized according to the field windings.
 - i. Shunt connected
 - ii. Series connected
 - iii. Compound connected
- d) A three-phase, four poles induction motor is connected to AC source. The frequency of the power source is 40 Hz.
Determine;
 - i. the synchronous speed, and
 - ii. the speed of the rotor when the slip is 5%

Question 08

- a) Discuss the advantages and disadvantages of pneumatic systems.
- b) Draw symbols of following pneumatic components.
 - i. 3/2 way directional control valve
 - ii. 5/2 way directional control valve
 - iii. Air service unit
- c) Design a simple pneumatic circuit to operate a single acting cylinder.

- END -