

The Open University of Sri Lanka
 B. Sc. Degree program – Level 04
 Final Examination 2007
 CSU 2178: Digital Computer Fundamentals
Duration: Two and half hours (2 1/2)



Date: 20.06.2007

Time: 1.30 pm- 4.00 pm

Answer **FOUR** Questions ONLY.


Q1.

- a. Briefly describe the following
 - i. Master control block
 - ii. Direct memory access
 - iii. Magnetic tapes
- b. Discuss the advantages and disadvantages of using cache memory.
- c. Using D type flip -flop and suitable logic gates, show how to construct a RAM cell with read write and select facilities.
- d. Create four-word by eight bit RAM by using two four-word by four-bit RAMs.

Q2.

- a. Following table shows truth table of the BCD-to-7 Segment decoder.
 - i. Complete the following truth table.


value			7-segment display						
A	B	C	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
0	0	1	1	0	0	0	0	1	0
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1							

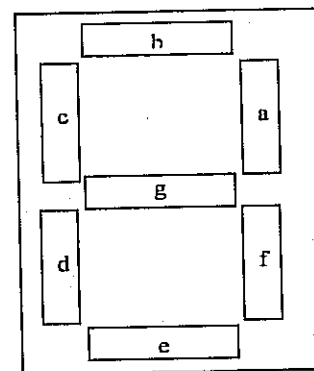

- ii. Design a circuit for any three values of BCD-to-7 Segment decoder.

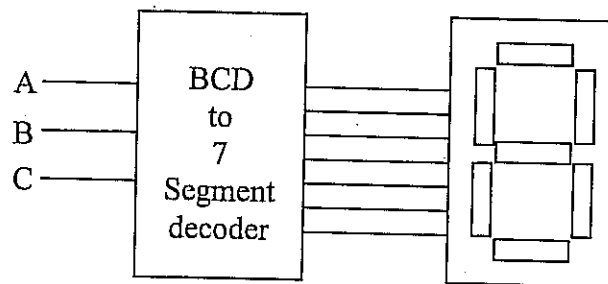- b. International Cricket Council (ICC) wants to develop special type of score board to display scores in the forthcoming World Cup cricket matches. A batsman can score 0 – 7 for a single ball. Assume that you have seven segments Display, BCD to 7-segment decoder and seven switches.
- Create a truth table for a circuit diagram to implement this.
 - Design the circuit diagram.

It will clear if the block diagram includes the circuit to be designed and the seven switches.



Q3.

- Using truth tables show that
 - $A+B+C = (A+B) + C$
 - $A + \bar{A} = 1$
 - $A.1 = A$
 - $\bar{A} . \bar{B} = \overline{(A+B)}$
- Using Boolean algebra and show that
 - $\bar{A} . \bar{B} . \bar{C} . \bar{D} + \bar{C} . \bar{A} . D + \bar{C} . \bar{A} . B = \bar{A} . \bar{C}$
 - $A.B.C.D + \bar{C}.D.B + \bar{A}.B.D = B.D$
- A Nuclear power controlling system contains four sensors to monitor temperature (A), pressure (B), Density (C) and Boron plates (D). Each A, B, C and D values represent high as '1' and low as '0'. Function of the controlling system as follows.


$$F = \bar{A} . \bar{B} . \bar{C} . \bar{D} + \bar{C} . D + A.B.C.D + \bar{A} . B$$
 - Using Boolean algebra and K-Map show that, $F = \bar{A} . \bar{C} + B.D + \bar{C}.D + \bar{A}.B$.
 - Implement above circuit using basic gates.

Q4.

- a. Briefly describe the following
 - i. Radix Number System
 - ii. The EBCDIC character set
 - iii. Unicode character set
- b. Convert following binary numbers into octal and hexadecimal
 - i. 101011001010_2
 - ii. 1000100.011_2
- c. Use Two's complement addition to perform the following calculation
 - i. $12_{10} + 33_{10}$
 - ii. $20_{10} - 27_{10}$
- d. Design a truth table for full adder.
- e. Implement Full Adder using basic logic gates.

Q5.

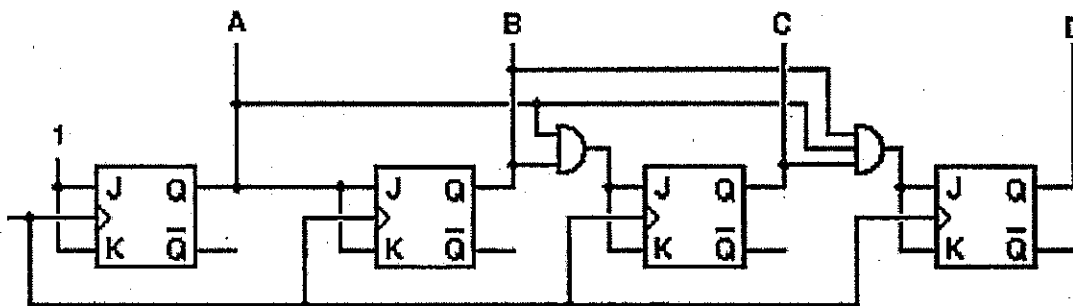- a. Briefly describe the following using suitable truth tables and Circuit diagrams
 - i. S-R Flip-flop
 - ii. J-K Flip-flop
- b. Develop a four-bit register using J-K flip flops
- c. What are the differences between synchronous and asynchronous counters
- d. Draw 4 bit up counter and a down counter.
- e. Explain the counter circuit given bellow.



Q6.

- a. Briefly describe the following using suitable truth tables and circuit diagrams
 - i. 4-to-1 Multiplexer
 - ii. Decoders
- b. Design 8-to-1 Multiplexer using two 4-to-1 Multiplexers
- c. Implement AND gate, an OR gate and a XOR gate using NAND gates.
- d. Find the minimal logic expression for the following truth table using the K-MAP method. Design a circuit to implement this truth table using 3-input NAND gates only.

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

*** All right reserved ***