

THE OPEN UNIVERSITY OF SRI LANKA

Faculty of Engineering Technology

Department of Electrical & Computer Engineering

Bachelor of Technology Honors in Engineering



Final Examination (2016/2017)

ECX3150: Electronics I

Date: 08th November 2017 (Wednesday)

Time: 9:30 am – 12:30 am

Answer only five questions

Q1. The circuit shown in Fig-Q1 consists of a Ge transistor ($V_{be} = 0.3V$) with a current gain, $\beta = 75$.

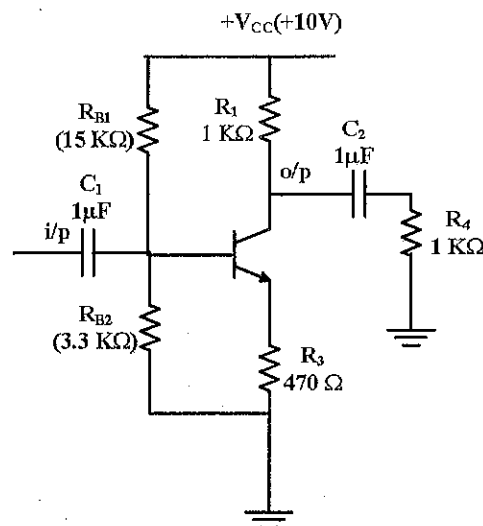


Fig-Q1

- Write the bias configuration of the circuit shown in Fig-Q1. [2 marks]
- Calculate the base current of the transistor. [4 marks]
- Calculate the collector and emitter currents. [4 marks]
- Hence calculate the V_{CE} voltage. [4 marks]
- Draw the DC load line for the circuit. [6 marks]

Q2.

Consider a power supply unit employed for generating a 15V constant DC voltage output from a sinusoidal input signal of 110V/60Hz. All the diodes and transistors are made of silicon.

- Explain the function of required circuit blocks for the given scenario. [4 marks]
- Draw the output waveform of the rectifier. Calculate and clearly mark the different voltage and time values. [3 marks]
- The output of the rectifier bridge is fed in to a simple capacitive smoothing filter. Let the capacitance of the capacitor be $10\ \mu\text{F}$. Draw the output waveform of the smoothing filter. Calculate and clearly mark the different voltages and time values. [3 marks]
- Consider the regulator circuit in Fig-Q2 which is fed with the output signal from the smoothing filter in part c). The transistor current gain is 50 and the minimum Zener current is 2mA,

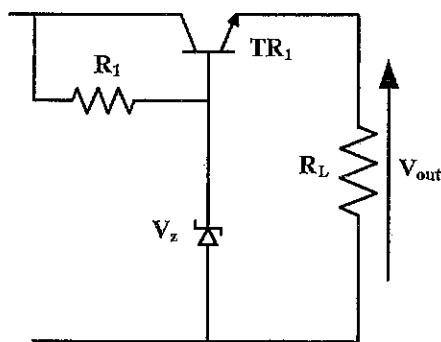


Fig-Q2

- What is the voltage of the Zener diode? [3 marks]
- If a 1A load current is required to operate the load, calculate the maximum power dissipation of the Zener diode and the Transistor TR_1 ? [7 marks]

Q3.

- Differentiate between bipolar and unipolar transistors. [5 marks]
- Name two applications of Junction Field effect transistors (JFET) [2 marks]
- A Junction Field effect transistor (JFET) amplifier is shown in Fig- Q3. The saturated drain current is 10mA and the pinch off voltage of the device is -6V.

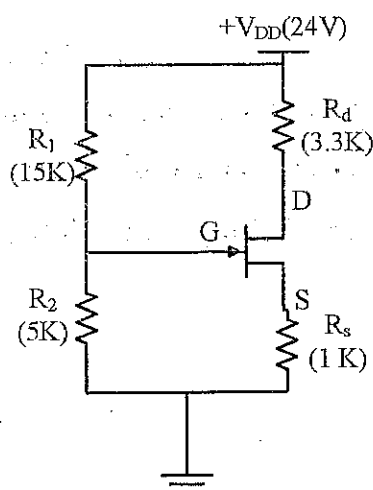


Fig- Q3

Calculate, the

(1) gate voltage.

[3 marks]

(2) drain current.

[5 marks]

(3) gate source voltage.

[5 marks]

Q4.

a) Show the conversion of the following

- i) 28_{10} to binary
- ii) 10101011_2 to decimal
- iii) 1101_2 to octal
- iv) 1111_2 to hexadecimal
- v) -42 in 1's complement
- vi) -45 in 2's complement

[6×1.5 marks]

b) Simplify the following logic functions using Boolean algebra.

- i) $X1 = \overline{ABC} + \overline{A}BC + \overline{AB}C + \overline{ABC} + \overline{ABC} + \overline{ABC}$
- ii) $X2 = [(AB + \overline{AB}) + \overline{AB}] + \overline{AB}$

[3 marks]

[3 marks]

c) Determine the output expression for the logic circuit shown in Fig-Q4.

[5 marks]

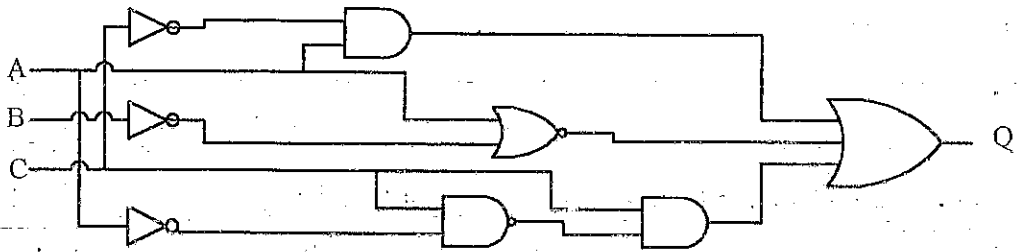


Fig-Q4

Q5.

- a) List the characteristics of an ideal operational amplifier. [3 marks]
 b) Fig-Q5 shows a Wien bridge oscillator circuit. Frequency of the oscillation is given by the equation $\frac{1}{2\pi RC}$.

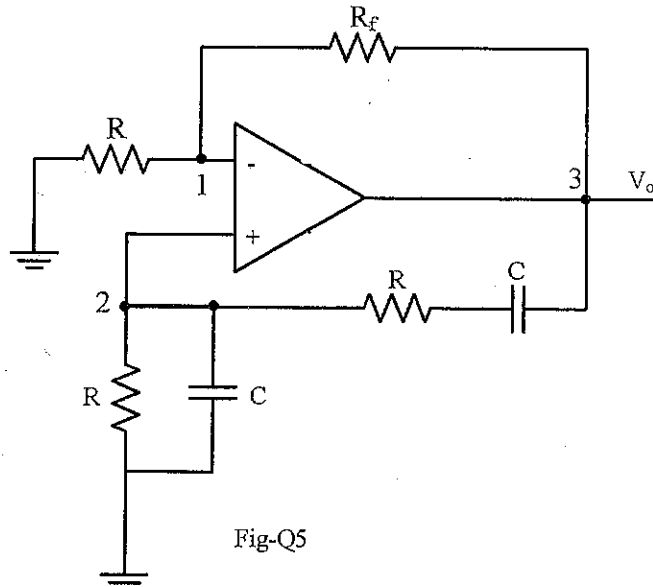


Fig-Q5

- a. Write the equations at node 1, 2 and 3 using kirchoff's current law. [6 marks]
 b. Obtain the transfer function of circuit shown in Fig-Q5 using the above equations. [7 marks]
 c. Calculate the amplitude and the frequency of oscillation of the Wien bridge circuit in Fig-Q5, if $R = 10K\Omega$ and $C = 0.001\mu F$. [4 marks]

Q6.

- a) Simplify the output functions using karnaugh maps.
 i) $F(P,Q,R) = 1,3,4,5,6$ [2 marks]
 ii) $F(P,Q,R,S) = 0,4,6,7,8,9,12,15$ [3 marks]

- b) Draw the logic circuit using only 2-input NAND gates for the simplified outputs given in Q6 part a). [6 marks]

c)

- i) What do you understand by a half adder and a full adder? [3 marks]
 ii) A full adder circuit is shown in Fig- Q6. Write the truth table for this circuit. [6 marks]

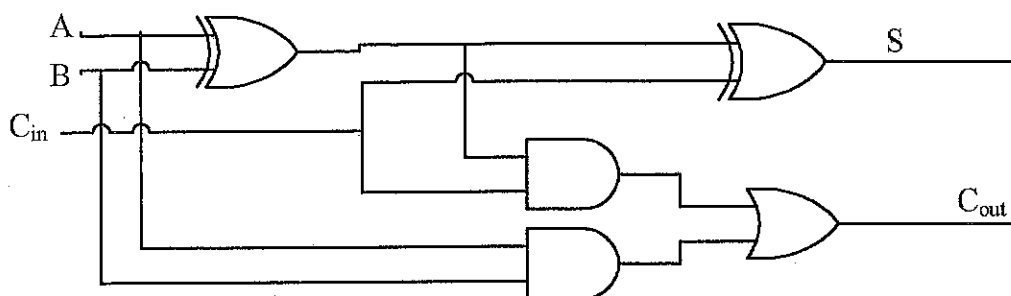


Fig-Q6

Q7.

- a) A Germanium diode when forward biased at 25°C carries a 3mA current at 0.2V. Assume V_T is 25mV at 25°C .
 i) Calculate the diode current when this diode is reversed biased by 10V. [3 marks]
 ii) Find the diode current when this diode is forward biased and at a temperature of 50°C . ($\eta=1$ for Ge) [3 marks]
 c) A certain PN junction was designed to use as a voltage controlled capacitor which is shown in Fig-Q7.1. The ohmic resistance and reverse resistance of the diode are negligible.

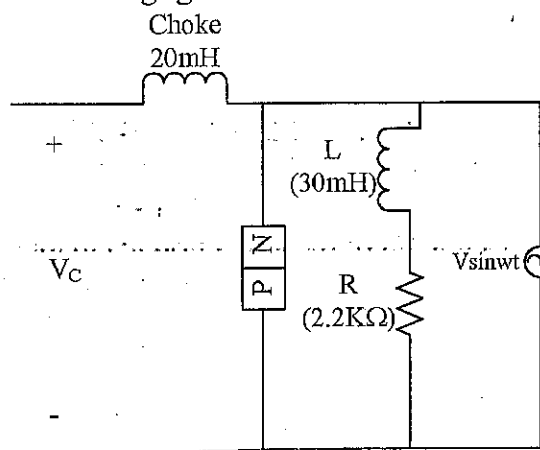


Fig-Q7.1

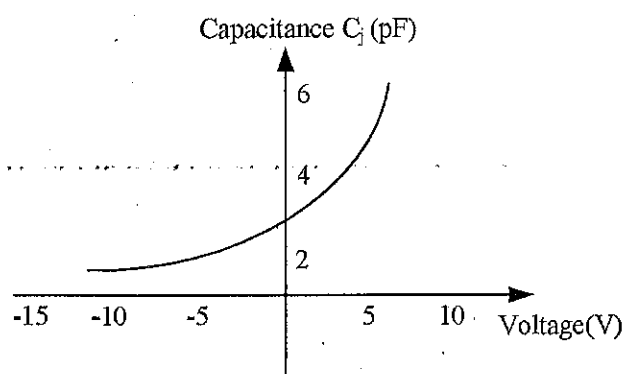


Fig-Q7.2

- i) Derive an expression for the resonant frequency of the circuit in Fig-Q7.1. [7 marks]
 ii) Calculate the capacitance of the diode if the circuit resonates at 30 MHz. [4 marks]
 iii) What is the required D.C voltage for this circuit to resonate at 30 MHz? [3 marks]

Q8.

- a) A 100 mH relay coil having a resistance of $10\ \Omega$ is connected in series with a $50\ \Omega$ resistance across a 12V battery. The relay operates at 20 mA.
- Derive an expression for the current - time relationship of the circuit. [5 marks]
 - Calculate the time taken to operate the relay after switching on the power. [5 marks]
- b)
- Explain the operation of clipper and clamper circuit including an example for each. [5 marks]
 - If the signal voltage (V_s) is $10\sin(1000t)$ V, sketch the output waveform of the circuit shown in Fig-Q8. [5 marks]

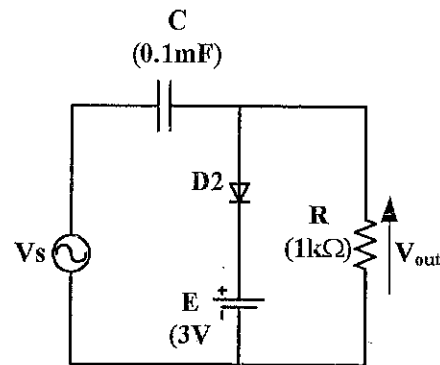


Fig-Q8