

The Open University of Sri Lanka

B.Sc. Degree Program: Level 04

Final Examination 2008/2009

CSU 2178-Digital Computer Fundamentals

Duration: Two and a Half Hours



117

Date: 10. 07. 2009

Time: 1.30 pm – 4.00 pm

Answer **FOUR** questions only.

Q1.

ChemSoft chemical company uses a chemical machine to produce a new chemical. The chemical machine uses two chemicals and produces a new product. You need to design and develop a security system to control the above chemical machine. The machine has four controls such as pressure of the machine (A), concentration of chemical 1 (B), Temperature of the machine (C) and concentration of chemical 2 (D).

The dangerous situations are listed below. All controls have two states such as Hi or Low. (Assume that Hi = 1 and Low = 0)

The following stage are harmful (Use these conditions as TRUE (1))

- All control values are low ($\bar{A} \bar{B} \bar{C} \bar{D} = 1$)
- Pressure of the machine and concentration of chemical 1 is Hi and other values are low ($A \cdot B \cdot \bar{C} \cdot \bar{D} = 1$)
- Only the pressure is Hi ($A \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} = 1$)
- All control values are Hi ($A \cdot B \cdot C \cdot D = 1$)
- Only the concentration of Chemical 2 is Low ($A \cdot B \cdot C \cdot \bar{D} = 1$)
- Pressure of the machine and Temperature are Hi and other values are Low ($A \cdot \bar{B} \cdot C \cdot \bar{D} = 1$)

The following states are NOT harmful (Use these conditions as DO NOT CARE)


- Only the concentration of Chemical 1 is Hi and other values are low
 - Only the concentration of Chemical 1 is Low and other values are Hi
 - The temperature is Hi and other values are Low
- a. Construct a TRUTH table for the above security system
 - b. Get the minimum expression for the above system Using the K-MAP Method.
 - c. Prove that the above expression is the minimum expression by using the Algebraic method.
 - d. Design a digital circuit for the above expression by using basic gates.
 - e. Design a digital circuit for the above expression by using NAND gates only.

Q2.

a. Briefly describe the following:

- i. 7 segment Display
- ii. 8 to 3 encoder

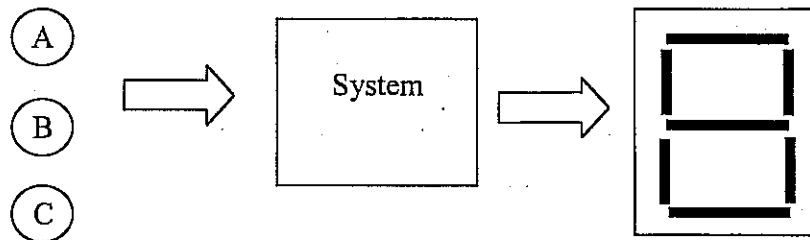b. International Cricket Council (ICC) needs to design a new display board to display runs in the next ICC cricket tournament. There are 3 buttons available on the board. User needs to press a combination of the buttons, and then the system shows the appropriate runs on the board.



Button number	Display number
No button pressed	-
A only	1
B Only	2
A and B Only	3
C only	4
A and C Only	5
B and C Only	6

i. Create a truth table for each button.

A	B	C	a	b	c	d	e	f	g
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							

ii. Construct the function for each output(a to g)

iii. Implement the circuit by using basic gates.

iv. ICC noted that multiple key press event (Example; Press B and C) has some troubles. Therefore they introduced 7 buttons that are used to display these display numbers. How would you improve the existing system by using 8 to 3 encoder, Explain briefly?

Q3.

- Briefly explain the following terms.
 - File System
 - Character, number and image representation in a computer
- Following diagram shows a Sinhala UNICODE character map. Answer the following question using this Sinhala UNICODE character map. [25]

	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0D8	අ	ආ	ඇ	ඈ	ඉ	ඊ	උ	ඌ	ඍ	ඎ	ඏ
0D9	ඐ	එ	ඒ	ඓ	ඔ	ඕ	ඖ	඗	඘	඙	ක	ඛ	ඛ	ඝ	ඞ	ඟ
0DA	ච	ඡ	ජ	ඣ	ඤ	ඦ	ට	ඨ	ඩ	ඪ	ණ	ඬ	ත	ථ	ඵ	ද
0DB	ඩ	න	.	ඳ	ඵ	ඹ	භ	ඹ	ඹ	ය	ර	.	ල	.	.	.
0DC	ඵ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ
0DD	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ	ඹ
0DE
0DF

- What is the value range of the Sinhala Unicode?
 - What are the Unicode values for Sinhala letters අ, උ ?
 - By using 16 bit registers, store the above values (Q3.b.ii).
- Convert the following numbers into Binary(base 2), Octal(Base 8) and hexadecimal(Base 16)
 - 79_{10}
 - 37_{10}
 - Use Two's Complement addition to perform the following calculations
 - $79_{10} + 37_{10}$
 - $79_{10} - 37_{10}$
 - $-79_{10} + 37_{10}$
 - $-79_{10} + -37_{10}$

Q4.

- Briefly describe the following
 - The Von-Neuman Computer model
 - The System bus model
 - Fetch-execute cycle
 - The memory hierarchy of a computer
- What are the advantages and disadvantages of the Assembly Language?
- Consider the following simple Assembly language program (The program has 5 lines)

1. ! This program add two numbers

2. .begin

3. .org 2048

4. Pro1:ld [r1], %x1

Ld [r2], %x2

Addcc %x1, %x2, x3

St %x3, [r3]

5. .end

Explain the task of the each line





Q5

- a. Write short notes for the following
 - i. Multiplexer
 - ii. Counters
 - iii. Registers
- b. Draw a circuit diagram and a truth table for the S-R Flip-flop.
- c. Using the S-R basic Flip-flop implement the following
 - i. Clocked S-R Flip-flop
 - ii. D Flip-flop
 - iii. J-K Flip-flop
- d. Draw a 2 bit register with Enable(EN), Clock(CLK) and Write(WR) controls

Q6.

- a. Describe the following terms used in computer Hardware:
 - i. HD – 160GB, 7200RPM, SATA
 - ii. DDR II 2GB, 800MHz
 - iii. DVD +RW
- b. "PORTs can be used to communicate with the computer". Do you agree with this statement? Explain briefly.
- c. What are the differences between CMOS and TTL IC Types?

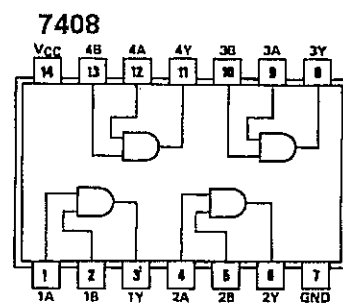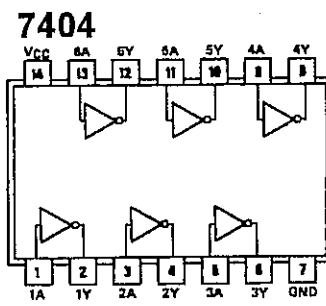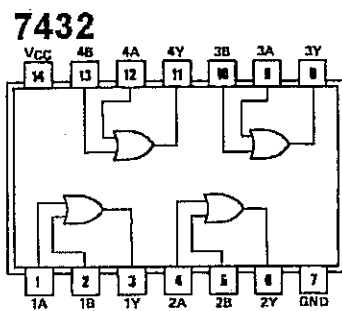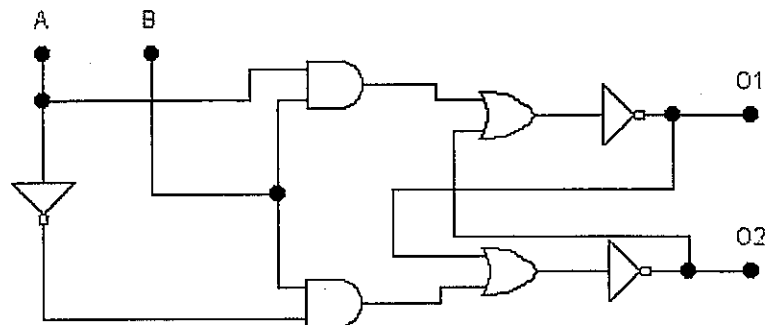d. Draw a IC circuit for the following Digital circuit (A, B inputs & O1,O2 are outputs)



All Rights Reserved

