



Date: 09th July, 2010

Time: 1.30 pm – 4.00 pm

Answer FOUR Questions ONLY.

Q1.

- a) Briefly describe the following:
 - i. Radix number system
 - ii. Two's complement addition
- b) Draw the truth table of a full adder circuit.
- c) Implement the full adder circuit using basic logic gates.
- d) Convert the following decimal numbers into binary (base 2) and hexadecimal (base 16) numbers.
 - i. 45
 - ii. 67
- e) By using 12-bit registers, store the above values in part (d).
- f) Use two's complement addition to perform the following calculations.
 - i. $45 + 67$
 - ii. $67 + (-45)$
 - iii. $45 + (-67)$
 - iv. $-67 - 45$

Q2.

- a) Implement the following gates using 2 input NAND gates only.

- i. OR
- ii. AND
- iii. XOR

- b) Consider the following function:

$$F = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}C.D + B.C.D + A.B.\overline{C}.D \text{ and}$$

$$A.\overline{B}.\overline{C}.\overline{D} = \overline{A}\overline{B}.C.D = A.\overline{B}.C.\overline{D} = \overline{A}.B.\overline{C}.D = X \text{ (Don't care)}$$

- i. Draw the truth table for the above function.
- ii. Find the minimal expression for the above function, by using the K-MAP method.
- iii. Draw a circuit diagram for the above function,
 - a) by using basic gates. (NOT, 2 input AND, 2 input OR)
 - b) by using 2 input NAND gates only.

Q3.


- a) What is a multiplexer? Describe briefly.
- b) Implement 8-to-1 multiplexer by using only two 4-to-1 multiplexers and the basic logic gates.
- c) Implement 8-to-1 multiplexer by using a 16-to-1 multiplexer.
- d) Consider the following truth table.



A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

- i. Write an algebraic expression for F.
- ii. Implement the above truth table by using 16-to-1 multiplexers only.

Q4.

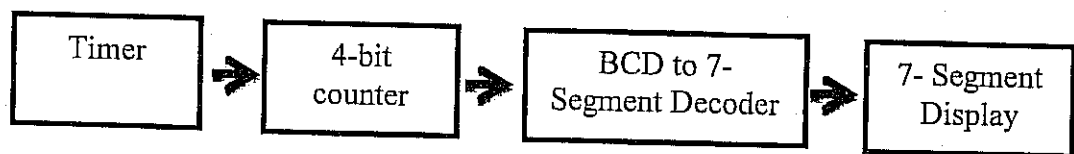- a) Briefly describe the following:
 - i. 7-segment display
 - ii. J-K flip-flop
 - iii. BCD to 7-segment decoder
- b) You need to design a timer circuit which shows time (0 – 9). Functional diagram of the complete circuit, circuit diagram of the timer and the layout of the BCD to 7-segment decoder are given below.



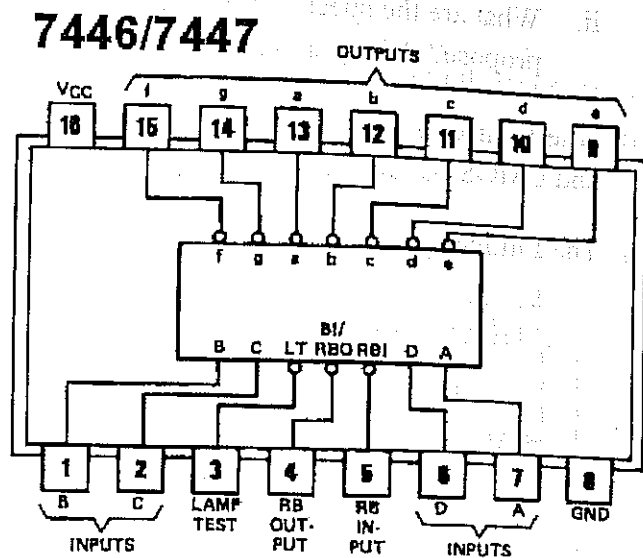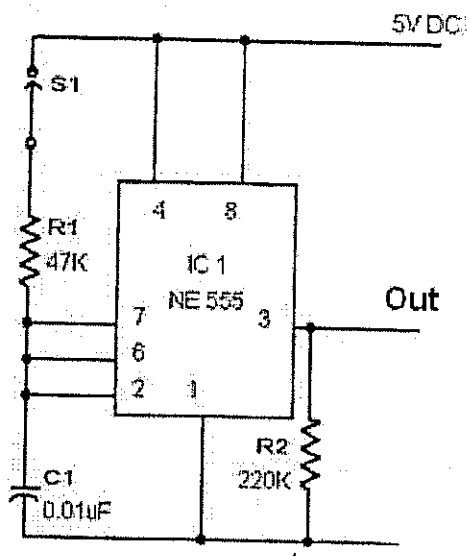

- Draw the complete circuit diagram (draw a 4-bit counter by using J-K flop-flops and connect all other components such as timer, BCD to 7- segment decoder and the 7- segment display).
- Draw the frequency waveforms for the 4-bit counter designed above.

Q5.


- Write short notes on the following:
 - Direct mapped cache and associative mapped cache
 - The memory hierarchy
 - Disk file system
 - Level of a machine
- Using a D type flip-flop, implement the following:
 - Single memory element (with Select, Read and Data in/out)
 - 4 bit register (with WR, CLK and EN)

Q6.

- Suppose you need to buy a Personal Computer (PC) for the graphics design propose.
 - Create a specification sheet with the following information.

Specification for the PC	
Processor	Type, clock speed, bus speed , other relevant information
Memory	Type, capacity, bus speed, etc.
Hard Drive	Type, capacity, speed, etc.
Optical device	Type, speed, other options
Graphics	Capacity, type

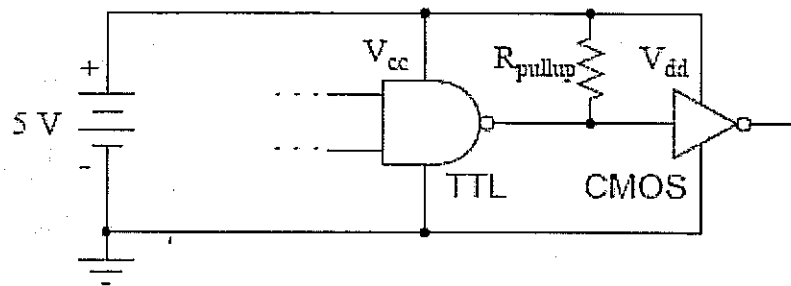
- ii. What are the special options/features you have to consider for graphics designing propose? Briefly describe.
- b) Briefly discuss the differences between working speed and the output power of TTL and CMOS IC families.
- c) The following figure shows the connection between TTL gate and the CMOS gate.



Considering the input and output voltage levels, briefly describe the process of the R_{pullup} resistor.

- d) Draw an IC circuit for the following digital circuit. (A, B and C are inputs & F is the output)


(Hint: use the given Data Sheet.)

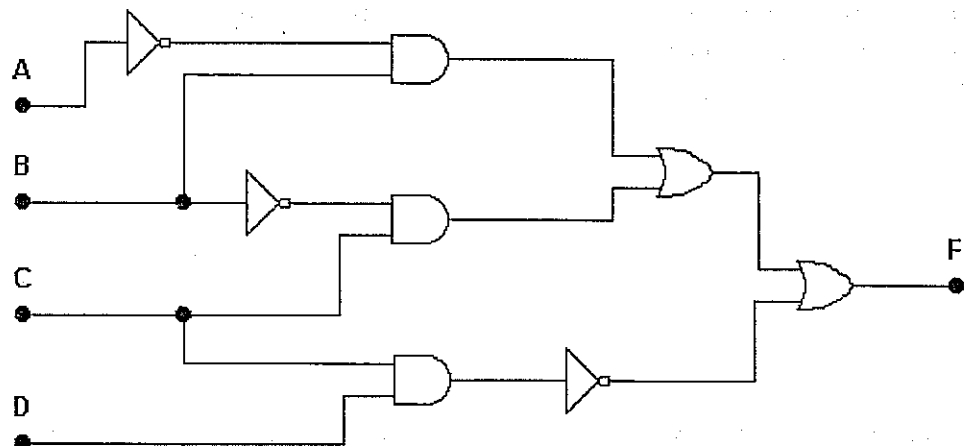


Data Sheets

7404 Hex inverters, 7400 Quad 2-input NAND gates, 7432 Quad 2-input OR gates and 7408 Quad 2-input AND gates.


7404

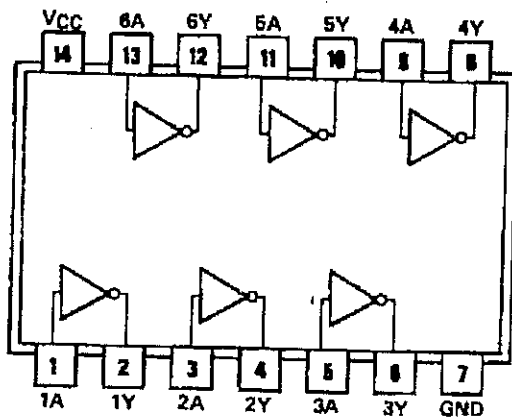


7400

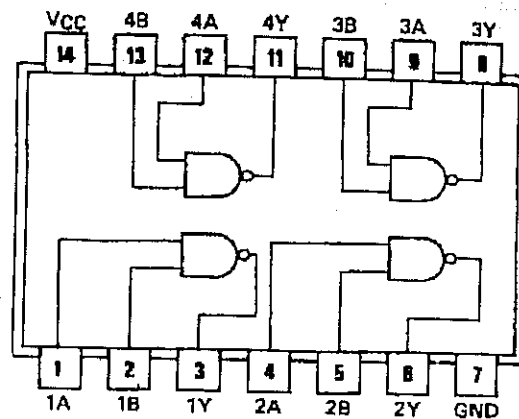

7432

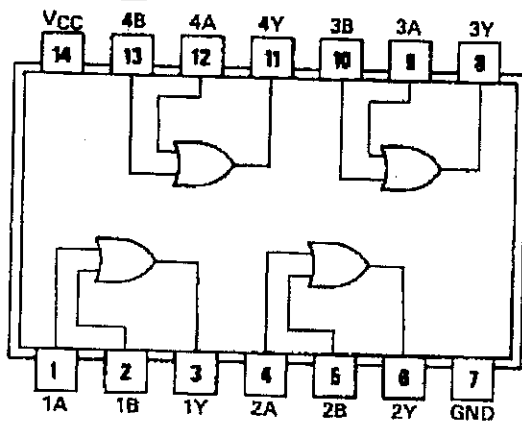

7408

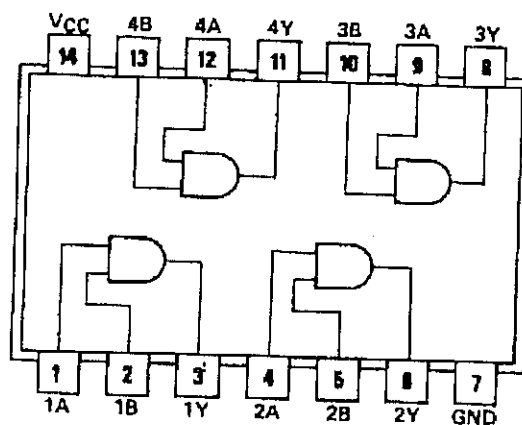

*** All Rights Reserved ***