

THE OPEN UNIVERSITY OF SRI LANKA  
B. SC. DEGREE PROGRAMME 2010/2011  
FINAL EXAMINATION – 2011  
PYU2262- ELECTRONICS  
DURATION: THREE HOURS (3 HRS)




ANSWER 06 QUESTION ONLY INCLUDING QUESTION NO 01 (Question No 01 is compulsory).

Date : 11-07-2011


Time : from 1.30 pm to 4.30 pm

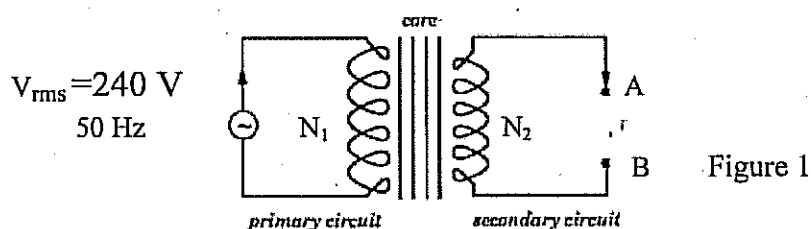1. (a) Figure 1 shows the transformer having a turn ratio of  $N_1 : N_2 = 20:1$ ,  $V_{rms} = 240\text{ V}$ ,  $50\text{ Hz}$ .



- Find the R.M.S. Voltage and Peak voltage across the AB
- Draw the wave form across AB
- Using the above transformer you are going to construct a low voltage power supply. Sketch the circuit diagram for full wave rectification using four (04) rectification diode.
- Draw the output wave pattern after connecting the four (04) rectifier diode and Find DC voltage of the output.
- Now you are given a capacitor  $C = 0.2\text{ }\mu\text{F}$  and a Load Resistor  $R_L = 1\text{ k}\Omega$ . Rearrange the circuit diagram drawn in Question (iii).
- Find the ripple factor of the output wave form
- Finally if you are given a zener diode with  $V_Z = 9.0\text{ V}$ , connect this zener diode to the circuit drawn in Question (v)

(b)

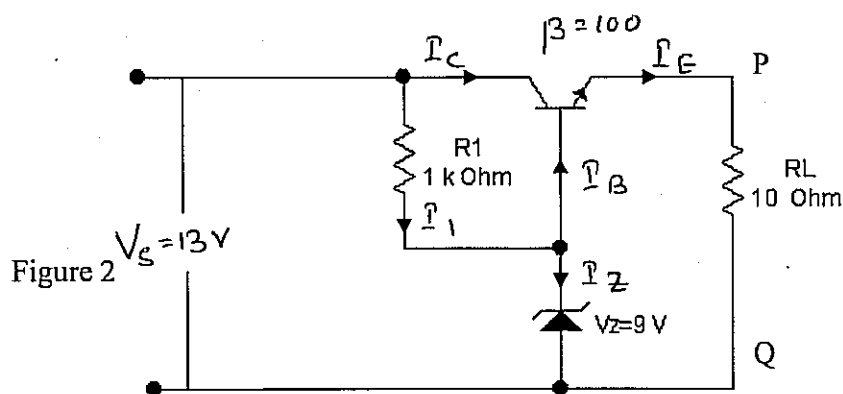

- Explain the function of the voltage regulator in figure 2
- Find the voltage across PQ ( $V_L$ )
- Calculate the currents  $I_1$ ,  $I_B$ , and  $I_Z$  in the above circuit
- Find the power dissipation of the Zener diode and the transistor

(20 Marks)

2. (a)

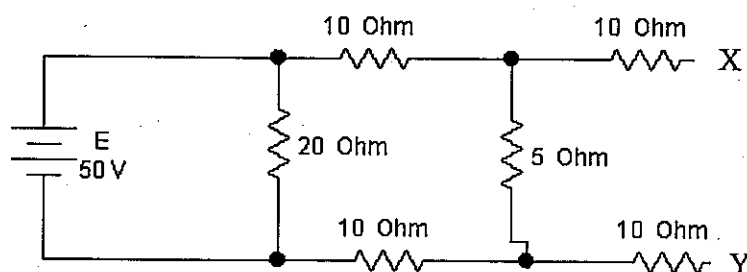


Figure 3

- (i) Write down the procedure for applying the Thevenin's theorem
  - (ii) Find the current through the  $5\Omega$  (Ohm) Resistor
  - (iii) Hence calculate the open circuit voltage across XY
  - (iv) Find the closed loop resistance  $R_O$
  - (v) Draw the reduced circuit diagram
  - (vi) Calculate the power dissipation of the  $10\Omega$  resistor which would be connected across XY in the network shown in figure 3
- (b) In the circuit shown in figure 4, the operating point is chosen such that  $I_c = 2\text{ mA}$ ,  $V_{CE} = 3\text{ V}$ . If  $R_C = 2.2\text{ k}\Omega$ ,  $V_{CC} = 9\text{ V}$  and  $\beta = 50$ , Determine the values of  $R_1$ ,  $R_2$  and  $R_E$ . Consider  $V_{BE} = 0.7\text{ V}$  and  $I_1 = 10\text{ I}_B$ .

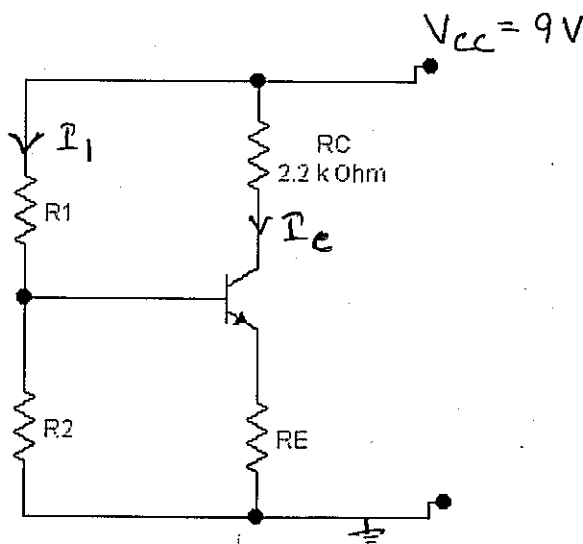


Figure 4

(16 Marks)

3. (a)

- (i) What do you understand by a semi-conductor? Discuss some important properties of semiconductors.
- (ii) Give the energy band description of semiconductors.
- (iii) Discuss the effect of temperature on semiconductors.
- (iv) What do you understand by intrinsic and extrinsic semiconductors?
- (v) Explain the formation of potential barrier in a  $pn$  junction.
- (vi) Draw and explain the V-I characteristics of a  $pn$  junction.
- (vii) What is the importance of Peak Inverse Voltage?

- (b) Calculate the current through  $48\ \Omega$  resistor in the circuit shown in figure (5). Assume the diode to be of silicon and forward resistance of each diode is  $1\ \Omega$ .

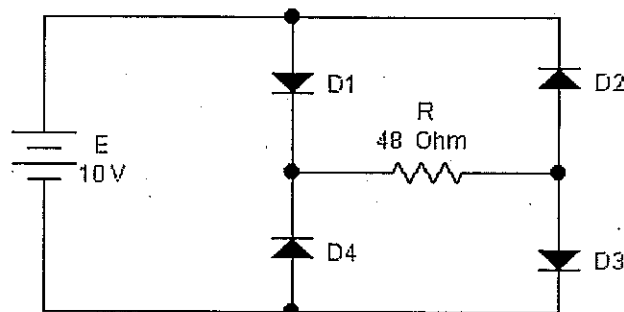


Figure 5

- (c) For the circuit shown in figure (6). Find the maximum and minimum values of current through Zener diode.

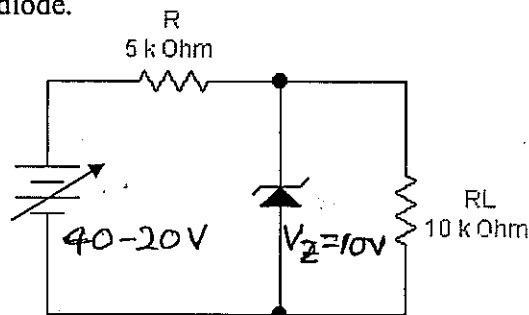


Figure 6

(16 Marks)

4. (a) Discuss the biasing and the stability of a Transistor in the following biasing methods

- (i) fixed biased circuit
- (ii) collector to base biased circuit
- (iii) emitter biased circuit

(b) In the small-signal amplifier of figure 7,  $h_{fe} = 100$ ,  $h_{ie} = 560 \Omega$ ,  $R_C = 2 \text{ k}\Omega$ ,  $R_E = 1 \text{ k}\Omega$ ,  $R_B = 600 \text{ k}\Omega$  and  $h_{re}$  and  $h_{oe}$  are negligible.

- (i) Draw the h- parameter equivalent circuit for the amplifier shown in figure 7.
- (ii) Calculate the input and the output impedances and voltage gain of the amplifier
- (iii) Sketch the DC load line and mark the Q point for the circuit given in figure 7.

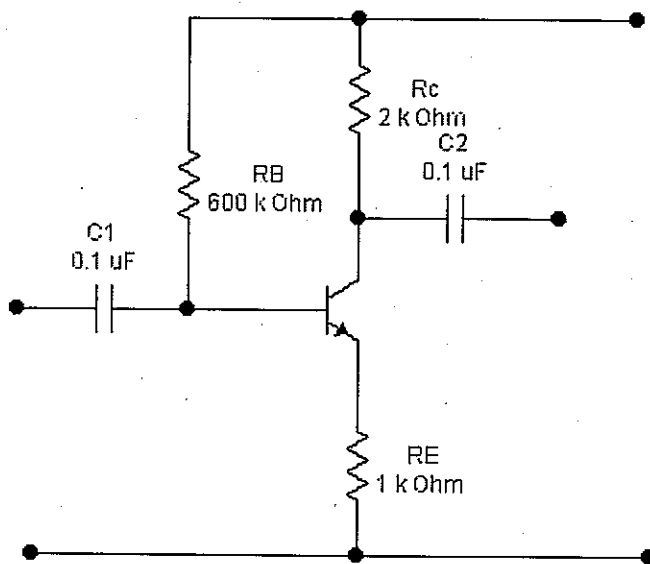


Figure 7

(16 Marks)

5.

(a)

- (i) Discuss advantages and disadvantages between class A amplifier and class B amplifier with the wave form diagram
- (ii) If the output wave form of an amplifier is given in the following form.

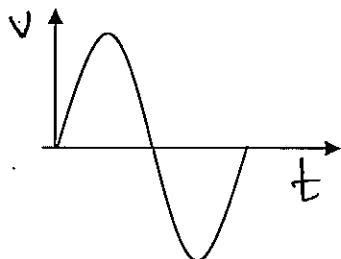


Figure 8

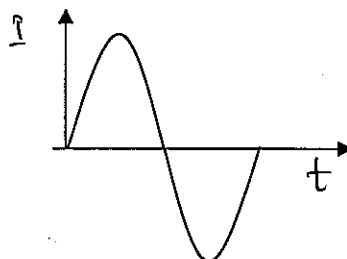


figure 9

Find the following parameters

1. Average power output
2. Average dc current
3. Average input power. Hence find the efficiency of the amplifier

- (b) Explain the operation of a Wien-bridge oscillator using a circuit diagram. Find an expression for the frequency of oscillation.
- (c) Discuss the amplitude stability of the Wien-bridge oscillator.

(16 Marks)

6.

- (i) Discuss the term negative feedback and positive feedback using circuit diagrams
- (ii) What do you mean by connecting the feedback network either in shunt with the output or in series with the output
- (iii) After introducing the negative feedback comment on the following modifications of amplifier characteristics
  - (a) Stability of gain
  - (b) Decrease in distortions
  - (c) Effect on input and output impedances
- (iv) Figure 10 shows a current feedback block diagram with current and resistances

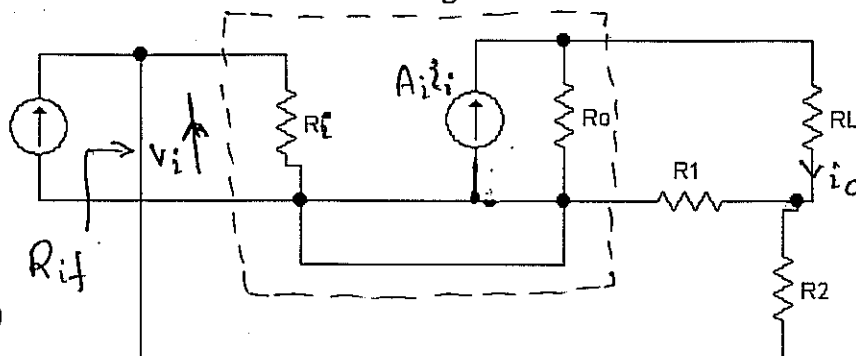


Figure 10

- (a) Prove that the feedback current can be written as  $i_f = \beta i_o$

$$\text{Where } \beta = \frac{R_1}{R_1 + R_2 + R_i}$$

- (b) Hence prove that current gain with feedback is

$$A_{if} = \frac{A_i}{1 - \beta A_i}$$

Where  $A_i$  current gain without feedback

- (c) Find the input impedance  $R_{if}$  of the amplifier.

(16 Marks)

7.

- (i) Draw the following gates using only NAND gates  
 (a) NOT  
 (b) AND  
 (c) OR  
 (ii) Write down the advantages and disadvantages of Digital Electronics  
 (iii) Verify the following Boolean identities

- (a)  $AB + \bar{A}C + BC = AB + \bar{A}C$   
 (b)  $ABC + A\bar{B}C + AB\bar{C} = AC + AB\bar{C}$   
 (c)  $A + \bar{A}B = A + B$   
 (d)  $AB + AC + B\bar{C} = AC + B\bar{C}$

- (iv) A pump is to operate (P), when water level of any two or all three reservoirs X, Y and Z goes below a certain mark. A level detector fitted with each reservoir produces a high voltage signal whenever the water level in the reservoir falls below the desired mark. If a high voltage switches on the pump, design a logic circuit to operate the pump  
 (v) Prove that using any map method, it can be simplified to  $P = XY + YZ + ZX$ .

(16 Marks)

8. (a) Convert  $99_{10}$  to (i) standard binary (ii) hexadecimal (iii) BCD binary

- (b) What is multiplexer? Explain the operation of 4-to-1 multiplexer

- (c) Implement the Boolean function given by the equation  $f(P, Q, R) = \sum 2, 4, 7$  using 4-to-1 multiplexer with two selection lines.

(16 Marks)

9. (a)

(i) How can a flip flop be categorized as a memory element?

(ii) The S R latch initially is in the set state. If inputs are changed such that  $S = 1$  and  $R = 1$ , what happens to the next state of the flip-flop?

(iii) Why is a D-type flip flop called as a delay flip flop?

(b) Consider the circuit below which uses D-type flip flops


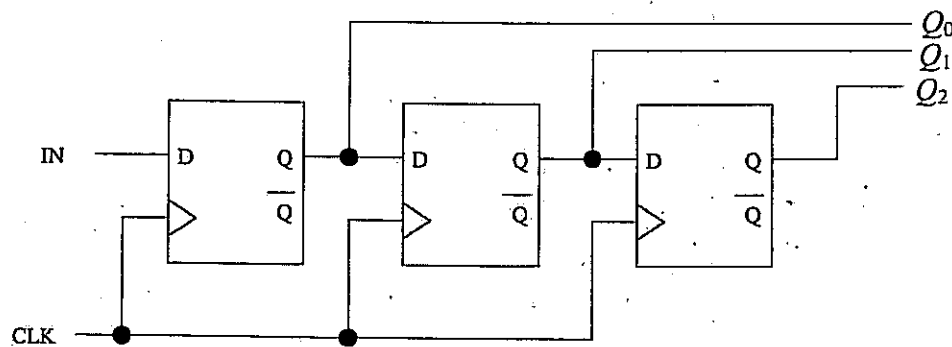


Figure 11

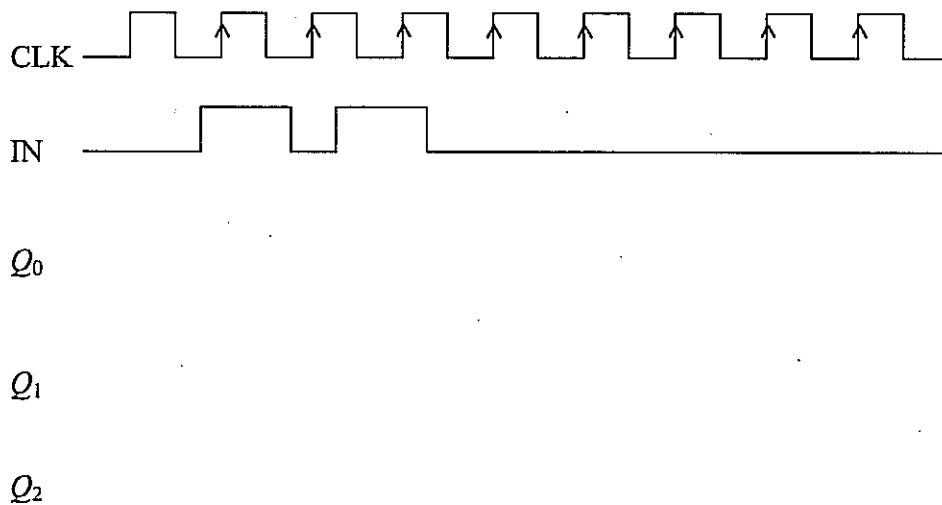Complete the timing diagram by including the signals  $Q_0$ ,  $Q_1$  and  $Q_2$ . (Assume that they are all initially LOW, as indicated.)



(16 Marks)

\*\*\*\*\*