



Duration: **One and Half hours only (1.5 hrs)**

Date: **01.03.2012**

Time: **04.00 pm – 05.30 pm**

**Answer ALL Questions.**

**Q1.**

- a. Prove the following rules by considering A, B and C as boolean parameters.
  - i. Distributive Law
  - ii. Associative Law
  - iii. Commutative Law
- b. Prove **DeMorgan's Theorem**.
- c.
  - i. Get the Boolean expression for the output of the following truth table.

Inputs			Output
C	B	A	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- ii. Minimize the expression for Y using Boolean rules. State the rules.
  - iii. Draw the Logic circuit for Y.
- d. Minimize the following truth table using **K-map** method.

Inputs				Output
D	C	B	A	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0

1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

## Q2.

- What are the functions of the following digital components?
  - Multiplexer
  - Demultiplexer
  - Decoder
  - Encoder
- Draw the **Block diagram** and **Circuit diagram** of 1 to 4 **Demultiplexer** where ;  
 $F_0 = DA'B'$  ,  $F_1 = DA'B$  ,  $F_2 = DAB'$  ,  $F_3 = DAB$
- Describe the function of the **Multiplexer**.
- Convert the following base 10 numbers into base 2.
  - 27.25
  - 101.02
  - 302.222
- Represent following numbers in **One's complement** and **Two's complement**.  
 (Consider 8 bit representation)
  - +15
  - 15
- Draw the **Adder circuit** for 3 bit binary addition operation.

## Q3.

- What are the differences between **Sequential Logic** and **Combinational Logic**?
- Draw the Block diagrams to represent Combinational Logic and Sequential Logic.  
 Describe the function of both logics.
- Briefly describe **Circuit Hazard** using an example circuit.
- Draw the truth table for the output of **S-R Flip-Flop**.
- Draw the Circuit diagram and Timing diagram for **Clocked S-R Flip Flop**.

\*\*\*All Rights Reserved\*\*\*