



Duration: **One and Half hours only (1.5 hrs)**

Date: **01.03.2012**

Time: **04.00 pm – 05.30 pm**

Answer ALL Questions

Q1.

- a. Prove the following rules. Consider A, B and C as boolean parameters.
 - i. Distributive Law
 - ii. Associative Law
- b.
 - i. Get the Boolean expression for the output of the following truth table.

Inputs			Output
C	B	A	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- ii. Minimize the expression for Y using Boolean rules. State the rule.
 - iii. Draw the Logic circuit for Y.
- c. Minimize the following truth table using **K-map** method.

Inputs				Output
D	C	B	A	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0

1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Q2.

- What are the uses of following digital components?
 - Demultiplexer
 - Decoder
- Describe the function of the **Multiplexer**.
- Convert following base 10 numbers into base 2.
 - 27.25
 - 101.02
- Represent following numbers in **One's complement** and **Two's complement**.
(consider 8 bit representation)
 - +15
 - 15
- Draw the **Adder circuit** for 3 bit binary addition operation.

Q3.

- What are the differences between **Sequential Logic** and **Combinational Logic**?
- Draw the block diagrams to represent **Combinational Logic** and **Sequential Logic**.
Describe the function of both the logics.
- What are the classes of **Sequential Logic**?
- What is known as a **Circuit Hazard**? Give an example circuit.
- Draw the circuit diagram and Timing diagram for **Clocked S-R Flip Flop**.

All Rights Reserved