

THE OPEN UNIVERSITY OF SRI LANKA
 FACULTY OF NATURAL SCIENCES
 B. SC. DEGREE PROGRAMME 2012/2013
 DEPARTMENT OF PHYSICS
 FINAL EXAMINATION
 DURATION: - 3 HOURS



PYU2262- ELECTRONICS

DATE:- 14-12-2013


FROM 1.30 P.M. TO 4.30 P.M.

ANSWER 06 QUESTIONS ONLY, INCLUDING QUESTION No. 01 IN PART A

(Question No. 01 is compulsory)

PART A

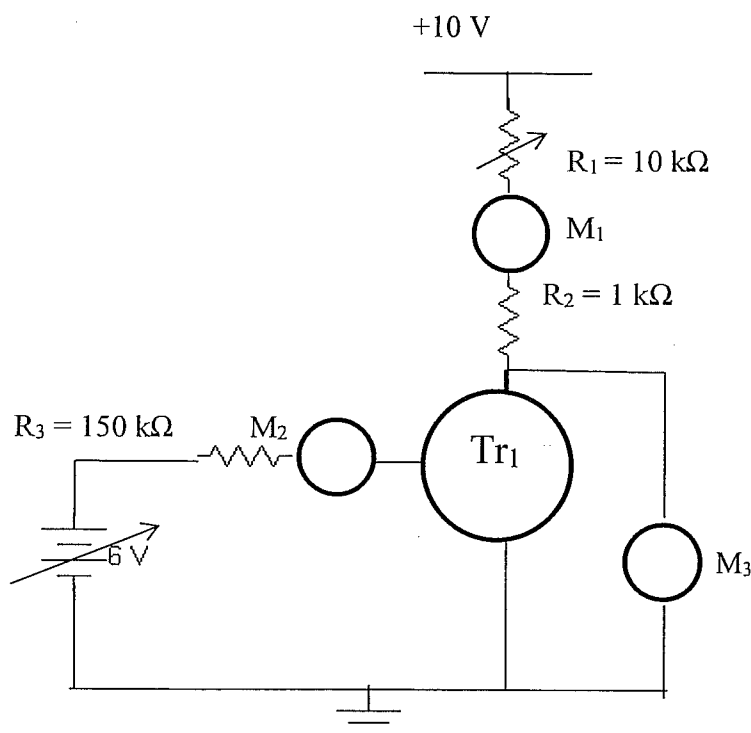
1. Figure shows a sketch diagram of the circuit to measure the output of a transistor




- Redraw the circuit diagram with a suitable transistor
- List the apparatus and components that you may use in this experiment.
- Describe the type of the transistor that you may use in this experiment with reasons.
- Identify the meters M_1 , M_2 and M_3 used in this circuit.
- Write down the initial adjustment that you may do in this experiment.
- Describe the function of the variable resistor R_1 .
- Write down the steps that you may follow to take readings from M_1 and M_3 ?
- Write down the steps that you may make in order to identify the operating point.
- Sketch the expected output characteristics of the transistor with labeling the relevant axes.

PART B (ANSWER ANY 05 QUESTIONS FROM PART B)

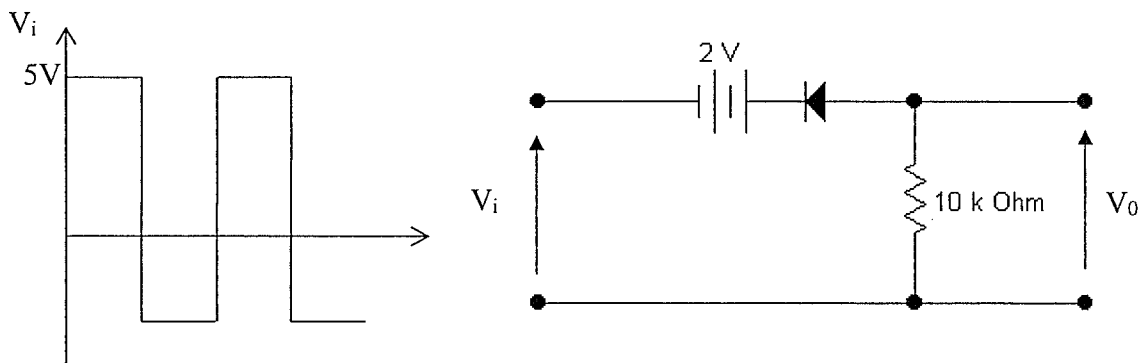1. a. (i) Write down advantages of semiconductor device in electronic industries.
- (ii) If a student claims that "An extrinsic semiconductors contains equal numbers of electrons and holes" discuss this statement.
- (iii) Discuss the differences between the Light Emitting Diode (LED) and Photo Diode
- (iv) Explain changes occurs in the depletion region when the PN junction is in
 (a) forward biased
 (b) Reverse biased
- b. Plot output wave form (V_o) for the circuit in the following figure for the input (V_i) shown. Assume that forward voltage of the given diode is 0.7 V.



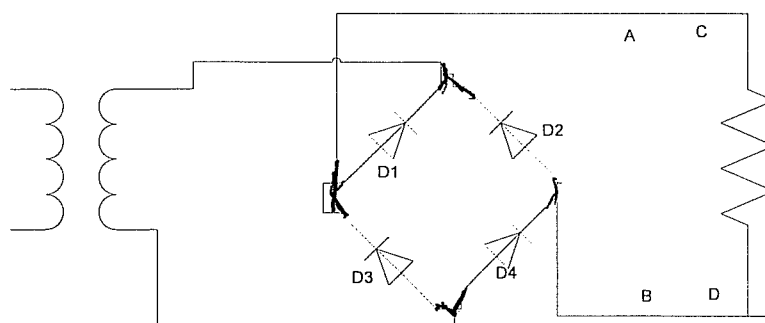2. a. Figure shows an incorrect full wave bridge rectifier circuit drawn by a student.
- (i) Redraw the correct circuit diagram in your answer sheet.




- (ii) Draw the smoothing capacitor in the correct position of your circuit diagram in order to get the smoothed output wave form.
- (iii) Sketch the variation of the output wave forms for different capacitor values one high and one low.
- (iv) Output wave of the transformer is $V_m \sin 2\pi ft$ where V_m is peak voltage and f -frequency of the wave


Show that dc value of the output voltage (V_{dc}) is given by

$$V_{dc} = \frac{2V_m}{\pi}$$

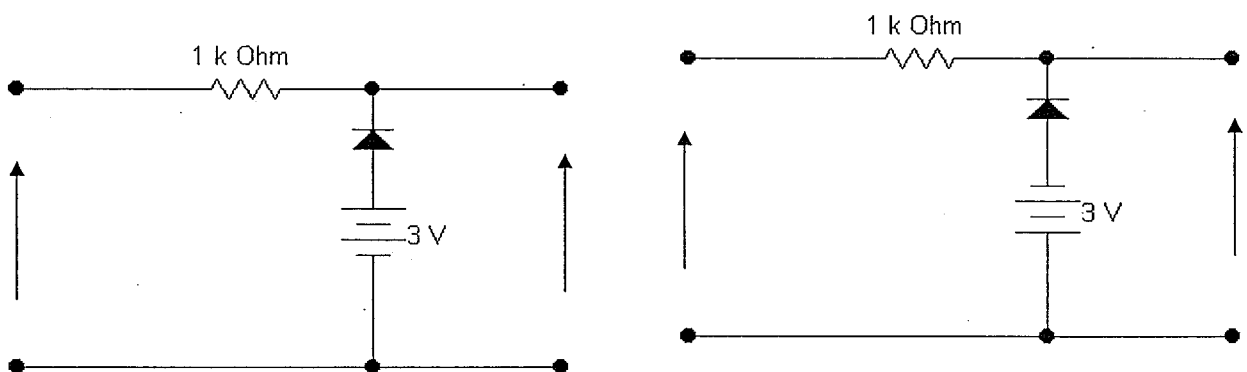- (v) If you are given a zener diode having $V_Z = 9$ V, modify and redraw the given circuit to obtain a regulated voltage supply.
- b. i. What do you understand by a Clipper circuit and a Clamper Circuit?
- ii. Draw the output wave form for the following circuit diagrams when the input wave form is sinusoidal with $V_m = 10$ V.



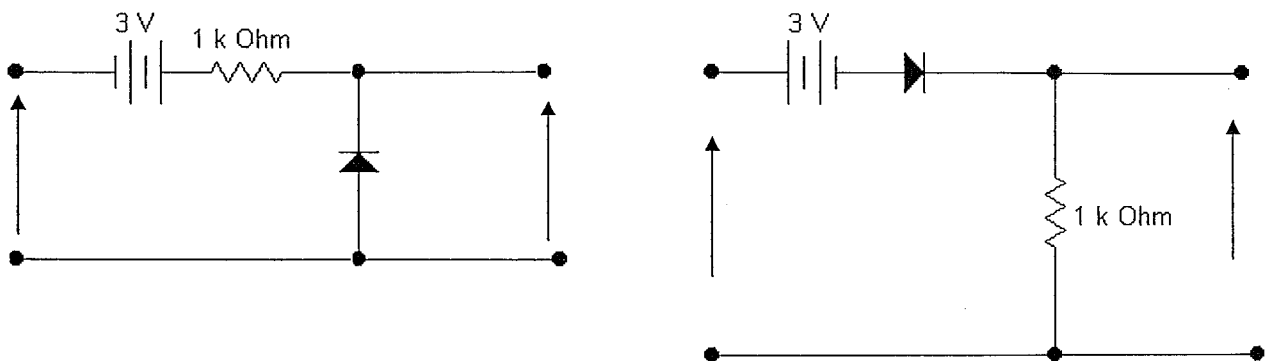- iii. Draw the output wave form for the following clamping circuits when the input wave form is a sinusoidal with $V_m = 10$ V.




3. a. i. Define the hybrid parameters h_{fe} and h_{ie} for a basic transistor circuit in CE configuration.
- ii. Voltage gain (A_V) of a transistor amplifier is given by the following expression.


$$A_V = -\frac{h_f R_L}{(1 + h_o R_L) h_i}$$

When $\frac{1}{h_o} \gg R_L$ show that for practical purposes the above expression can be reduced to $-\frac{h_f R_L}{h_i}$ (Here Symbols have their usual meanings)

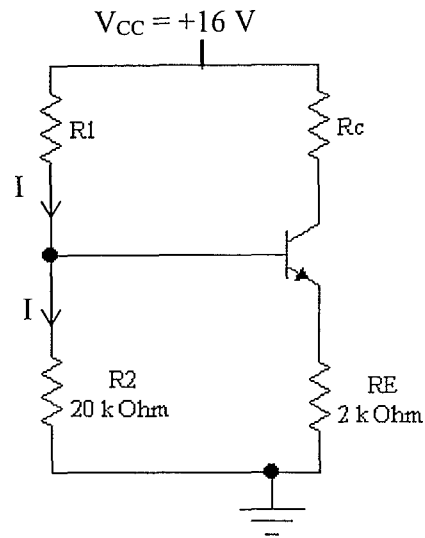- b. A CE configuration transistor amplifier with self-bias or voltage-divider bias is required to have a voltage gain of about -200. An *npn* silicon transistor with $h_{fe} = 100$, $h_{ie} = 1 \text{ k}\Omega$ and maximum collector power dissipation of 75 mW is available. (Neglecting h_{re} and h_{oe} and using $V_{CC} = 12 \text{ V}$)
- i. Draw the circuit diagram with R_1 , R_2 , R_L and R_E (Here Symbols have their usual meanings)
- ii. Find the value of R_L
- iii. Determine the current I_C through R_L assume that $V_{CG} = V_{CC} / 2$ where G is the ground terminal.
- iv. Assuming power dissipation of the collector and emitter (CE) junction as 15 mW. Show that $V_{EG} = 1.2 \text{ V}$, hence find the R_E
4. a. i. Discuss the fundamental differences among class A, class B and class C amplifiers
- ii. Discuss the differences between the parallel and series tuned circuits
- iii. What is a tuned amplifier?
- iv. Explain with a circuit diagram the operation of a single-tuned amplifier
- b. An *npn* transistor circuit given below has $\alpha = 0.985$ and $V_{BE} = 0.3 \text{ V}$. and $R_2 = 20 \text{ k}\Omega$, $R_E = 2 \text{ k}\Omega$ and $V_{CC} = 16 \text{ V}$. Answer the following questions placing Q point at $I_C = 2 \text{ mA}$ and $V_{CE} = 6 \text{ V}$
- i. Determine the current gain β
- ii. Show that the voltage across R_2 is 4.3 V
- iii. Determine the R_C and R_1 assuming current passing through R_1 and R_2 are same.




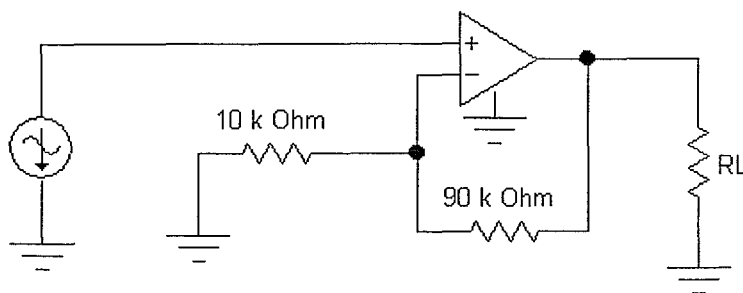5. a.
- i. Discuss the concept of feedback in amplifiers with a proper diagram.
 - ii. Explain what do you understand by the positive and negative feedback
 - iii. To an amplifier without a feedback circuit, if you introduce a negative feedback what changes you will obtain in the output of the amplifier.
 - iv. Show that the output impedance (R_{of}) of the feedback amplifier circuit can be written as $R_{of} = \frac{R_o}{1-A_V\beta}$ Where R_o - output impedance without feedback, A_V - Voltage gain without feedback, β - feedback factor
 - v. Figure shows the circuit of a negative voltage feedback amplifier. If without feedback, Voltage gain $A_V = 10,000$, input impedance $R_i = 10 \text{ k}\Omega$ and output impedance $R_o = 100 \Omega$, Determine
 - a. the feedback fraction (β)
 - b. gain with feedback (A_{vf})
 - c. the output impedance with feedback (R_{of})




6. a. i. Determine the binary equivalent of 13.875
 ii. Find the decimal equivalent of 101.1101
 iii. Determine the binary equivalent of the hexadecimal number A5D
 iv. Find the hexadecimal equivalent for the decimal number of 581
 v. Perform the binary addition $11000.11 + 101.111$
- b. Prove the following expressions using Boolean Algebra
- i. $ABC + A\bar{B}C + AB\bar{C} = A(B + C)$
 ii. $(A+B)(A+C) = A+BC$
 iii. $(A + B)(A + \bar{B})(\bar{A} + C) = AC$
 iv. $(\bar{A} + B)(A + B) = B$
- c. Find the complement (\bar{Y}) of the expressions given below
- i. $Y = ABC\bar{C} + A\bar{B}C$
 ii. $Y = \bar{A} + (B\bar{C} + \bar{B}C)$

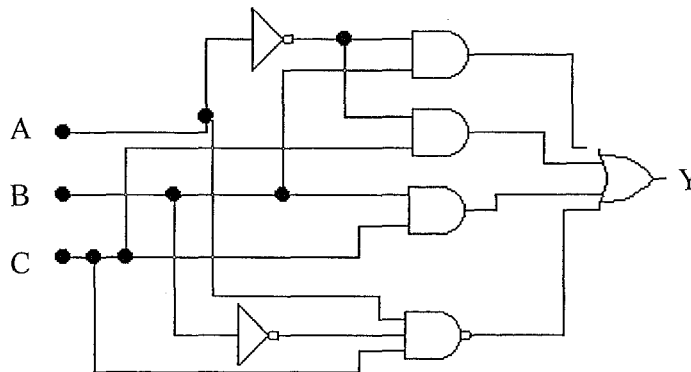7. a. i. Obtain the Boolean expressions for the output Y in the logic circuits given below.
 ii. Simplify the Boolean expressions that you have written in part (i)
 iii. Draw the logic circuit diagrams for the simplified Boolean expressions.



Circuit diagram 1

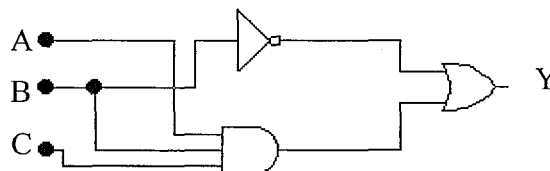

Circuit diagram 2

b. Simply the following function by using K map method.

i. $X = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C}$

ii. $X = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$

iii. $X = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + AB\bar{C}$

iv. $X = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$

c. A burglar alarm should be activated when the two conditions given below are simultaneously satisfied

(a) The main entrance door of the building is open, and

(b) The bed room door and /or the kitchen door is open.

Write the truth table and construct the logic expression to operate the alarm using one AND gate and one OR gate.

8. a. How is an *RS* flip-flop converted into a *JK* flip-flop? Give its truth table and explain how it is obtained
- b. Explain use of preset and clear inputs in a flip-flop
- c. What is a De-multiplexer? How can a decoder circuit be used as a De-multiplexer? Give the block diagram of a 4-to-16 line De-multiplexer