

THE OPEN UNIVERSITY OF SRI LANKA  
 DEPARTMENT OF MATHEMATICS AND COMPUTER SCIENCE  
 B. SC. DEGREE PROGRAMME 2014/2015



**FINAL EXAMINATION**

**CPU3141: DIGITAL COMPUTER FUNDAMENTALS**

DURATION: TWO HOURS (2 HOURS)

**Date: 15.10.2015**

**Time: 1.30 pm – 3.30 pm**

**Answer All Questions.**

**Q1.**

(i)

a) Convert the following **decimal** number into **binary**.

345<sub>10</sub>

b) Convert the following **binary** number to **hexadecimal**.

1011001001111011101<sub>2</sub>

c) Convert the following **decimal** number into **octal**.

674<sub>10</sub>

(ii) Solve following using **binary arithmetic**.

a)  $1101_2 + 1100011_2$

b)  $100100_2 - 11111_2$

c)  $1101101101_2 / 110_2$

d)  $1101_2 * 1000011_2$

(iii) **Simplify** the following Boolean expression using **Boolean algebra rules**.

$$(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + C)(\bar{A} + \bar{B} + \bar{C})$$

**Mention the rules used in the simplification.**

(iv) Draw the **logic circuit** for the reduced Boolean expression in Q1 (iii).

(v) Implement the circuit of Q1(iv) using **NAND** gates only.

**Q2.**

- (i) What is a **Binary Code**? and describe the **use** of binary codes in digital systems.
- (ii) Briefly describe **Error Detection Codes**.
- (iii) Convert following **Gray code** value into **binary**.


11010110

**Q3.**

- (i) Describe the **function** of a **flip flop** using a **logic circuit** of a SR latch.
- (ii) What is known as **clocking**? Describe the **clocked SR flip flop** using a **circuit diagram**.
- (iii) Derive the **Truth Table** of a **JK Flip flop** and draw the corresponding **circuit diagram**, (Consider a NAND implementation)
- (iv) What is the **difference** between **combinational** logic and **sequential** logic? Give an example application for each.

**Q4.**

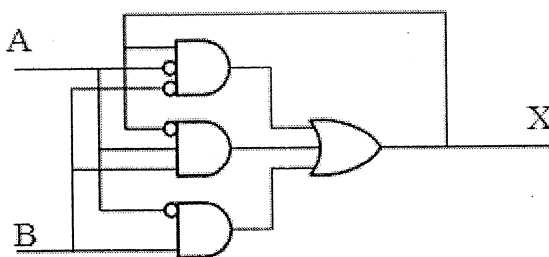- (i) What is a **Register**? Briefly describe **three (03)** types of Registers.
- (ii) Draw the **block diagram** of a **positive edge triggered asynchronous counter** that counts from 0 to 9 and draw the **timing diagram**.
- (iii) **Analyze** the following **asynchronous sequential circuit**. (Clearly indicate the steps)



- (iv) Identify the race conditions in the asynchronous circuit in Q5 (iii) and mention the steps you take to remove the race condition.

\*\*\* All Rights Reserved \*\*\*