

The Open University of Sri Lanka
Faculty of Engineering Technology
Department of Electrical & Computer Engineering



| | |
|------------------------------|---|
| Study Programme | : Bachelor of Technology Honours in Engineering |
| Name of the Examination | : Final Examination |
| Course Code and Title | : EEX4350 / ECX4150 Electronics II |
| Academic Year | : 2017/18 |
| Date | : 14 th January 2019 |
| Time | : 13.30-16.30hrs |
| Duration | : 3 hours |

General Instructions

1. Read all instructions carefully before answering the questions.
 2. This question paper consists of **Eight (8)** questions in **Five (5)** pages.
 3. Answer any **Five (5)** questions only. All questions carry equal marks.
 4. Answer for each question should commence from a new page.
 5. Relevant charts/ codes are provided.
 6. This is a Closed Book Test (CBT).
 7. Answers should be in clear hand writing.
 8. Do not use Red colour pens.
-

00099

1

2

1

1

- Q1. An impedance matching circuit is shown in Figure-Q1, where the transistor is having h_{ib} and h_{fb} 25Ω and 0.99 respectively. Neglect the effect of h_{rb} and h_{ob} .

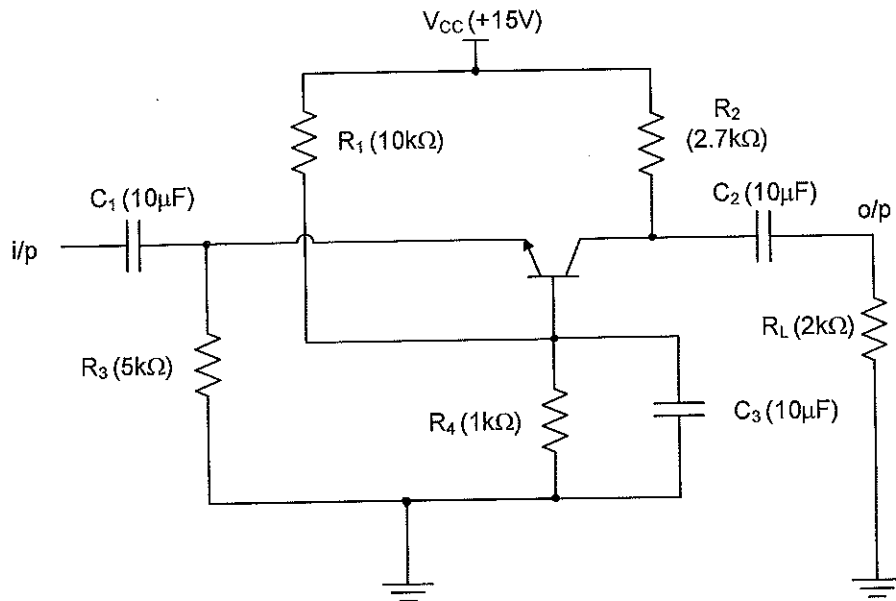


Figure-Q1

- (a) Draw the low frequency hybrid parameter equivalent circuit. **(6 Marks)**
- (b) Calculate the following.
- Voltage gain. **(4 Marks)**
 - Current gain. **(4 Marks)**
 - Input impedance. **(3 Marks)**
 - Output impedance. **(3 Marks)**

Q2.

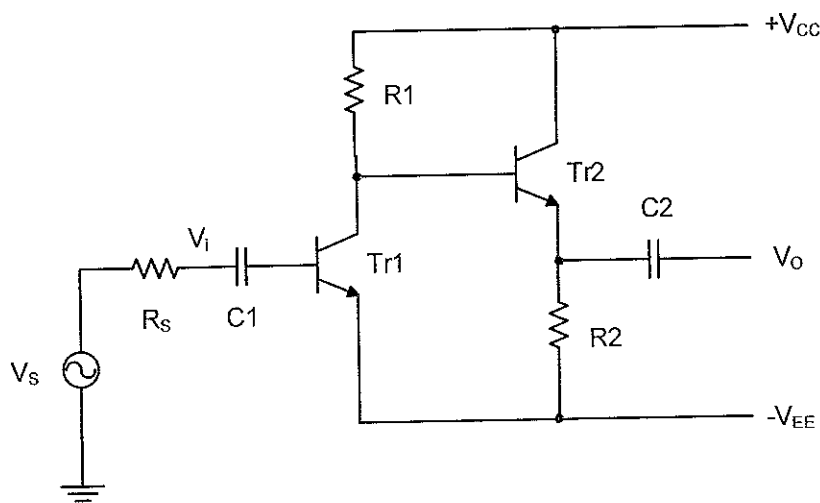


Figure -Q2

Consider the cascading amplifier setup in the circuit diagram shown in Figure-Q2, where Tr1 and Tr2 are identical.

Here,

$$R_s = 1k\Omega, R_1 = R_2 = 5k\Omega, h_{ie} = 2k\Omega, h_{fe} = 50, h_{re} = 6 \times 10^{-4}, h_{oe} = 25\mu A/V,$$

$$h_{ic} = 2k\Omega, h_{fc} = -51, h_{rc} = 1, h_{oc} = 25\mu A/V.$$

- (a) Draw the low-frequency equivalent circuit using the h-parameter model of the transistors.
(You may assume the effect of some parameters to be negligible. Clearly state all your assumptions made) **(8 Marks)**
- (b) Write down three equations to depict the relationships between base currents of the two transistors, V_s and V_o . **(3x2 Marks)**
- (c) Hence calculate $\frac{V_o}{V_s}$. **(6 Marks)**


Q3.

- (a) Compare class A, B, C and D power amplifiers in terms of their efficiency and output distortion. **(8 Marks)**
- (b) A complementary push-pull class-B power amplifier is to be designed to deliver an average power of 16W to a 8Ω load. The power supply voltage V_{CC} is to be 5V greater than the peak output voltage.
 - i. Compute the average power drawn from the supply. **(4 Marks)**
 - ii. Compute the power conversion efficiency of the amplifier. **(3 Marks)**
 - iii. Determine the maximum power each transistor should be able to dissipate. **(3 Marks)**
 - iv. Why is the supply voltage selected 5V greater than the peak output voltage? **(2 Marks)**

Q4.

- (a) Describe the operation of the SCR, DIAC and TRIAC with the help of their I-V characteristic curves. **(4 Marks)**
- (b) Explain how half wave power control can be obtained using a TRIAC. **(4 Marks)**

(c)

 **Figure-Q4**


In the circuit shown in Figure-Q4, $v_{in} = 60V$ rms and $R_L = 15\Omega$. Let the rms load current be given by $I_{rms} = \frac{I_p}{\sqrt{2}} \sqrt{\left(1 - \frac{\theta}{180}\right) + \left(\frac{\sin 2\theta}{2\pi}\right)}$, where I_p is the peak load current and θ is the firing angle. Neglecting the drop across the TRIAC, calculate,

- the maximum possible power that can be delivered to the load while conducting; **(6 Marks)**
- the maximum percentage load power delivered when the conduction angle is 45° . **(6 Marks)**


Q5.

- List three characteristics of a practical operational amplifier and compare them with the ideal approximations. **(6 Marks)**

- Consider the circuit arrangement in Figure-Q5 (b). Show that $V_o = \frac{R_2}{R_1} (V_2 - V_1)$ if $\frac{R_2}{R_1} = \frac{R_4}{R_3}$. **(6 Marks)**

 **Figure-Q5 (b)**

(c)

 **Figure-Q5 (c)**

Derive the transfer function for the circuit in Figure Q5 (c) in terms of the frequency of the input signal. **(8 Marks)**

Q6.

- (a) Draw the truth table and derive the Boolean expression for the sum and carry outputs in a single bit full adder. [You should clearly show the steps including the truth table and minimization]

(5 Marks)

- (b) Carry-look-ahead adder is a concept used in modern microprocessor ALUs to generate all carry bits required in adding two multi bit numbers using a combinational circuit. This eliminates the need for long waiting in order to receive the rippled carry bits. Let $A = a_4a_3a_2a_1$ and $B = b_4b_3b_2b_1$ are two 4 bit numbers for addition. Consider the addition of a single bit position with a full adder.

- i. Using the results of Q6 (a), show that the Boolean expression for the carry at the n -th bit ($n = \{1,2,3,4\}$) can be expressed in the form $C_n = G_n + C_{n-1}P_n$ where G_n and P_n are Boolean functions of a_n and b_n .

(5 Marks)

- ii. Hence show that C_n can be expressed in terms of c_0 , a_n and b_n only ($n = \{1,2,3,4\}$).

(5 Marks)

- iii. Draw the complete carry generation combinational logic circuit with standard logic gates.

(5 Marks)

Q7. A line following robot has to be designed with the following specifications.

- Robot has four sensors in a fixed linear array with the spacing between the sensors such that at most 2 sensors will be on the line at a time. On the other hand, there can be instances with a minimum of only one outer sensor on the line.
- Whenever the two center sensors are on the line, the robot should be moved forward; otherwise turning should be carried out to align the robot with the line. When the robot meets end of the line it should stop.
- Robot has two independent motors (connected to wheels) to generate motion.
 - Both motors on → Forward motion
 - Left motor on, right motor off → Right turn
 - Left motor off, right motor on → Left turn
 - Both motors off → No motion.

A digital combinational control circuit takes the sensor outputs' logical values as inputs and outputs logic signals to the motors.

- (a) Define the different inputs and outputs with suitable logic values. Hence, draw the truth table. **(10 Marks)**
- (b) Derive the simplified logic expressions using Karnaugh maps. **(8 Marks)**
- (c) Implement the circuit using common logic gates. **(2 Marks)**

Q8. Design a synchronous up-counter to produce the output sequence 0, 3, 6, 9, 12, 15, 0, ... using J-K flip flops. Clearly show the following design steps in your design.

- (a) State diagram. **(2 Marks)**
- (b) State transition table. **(6 Marks)**
- (c) Karnaugh map simplification of Boolean expressions. **(6 Marks)**
- (d) J-K flip flop based logic circuit diagram. **(6 Marks)**

