

The Open University of Sri Lanka
Faculty of Engineering Technology
Department of Electrical & Computer Engineering



Study Programme	: Bachelor of Technology Honours in Engineering
Name of the Examination	: Final Examination
Course Code and Title	: EEX4530 Fault Diagnosis in Electronic Circuits / <i>ECX4230</i>
Academic Year	: 2017/18
Date	: 18th January 2019
Time	: 0930-1230hrs

General Instructions

1. Read all instructions carefully before answering the questions.
 2. This question paper consists of Eight (8) questions in **Eight (08)** pages.
 3. Answer any **Five (5)** questions only. All questions carry equal marks.
 4. Answer for each question should commence from a new page.
 5. This is a Closed Book Test (CBT).
 6. Answers should be in clear hand writing.
 7. **Do not** use Red colour pen.
-

1. A single stage amplifier circuit is shown in figure 1. $I_{DSS} = 10\text{mA}$, and $V_{GS(off)} = -3\text{V}$.

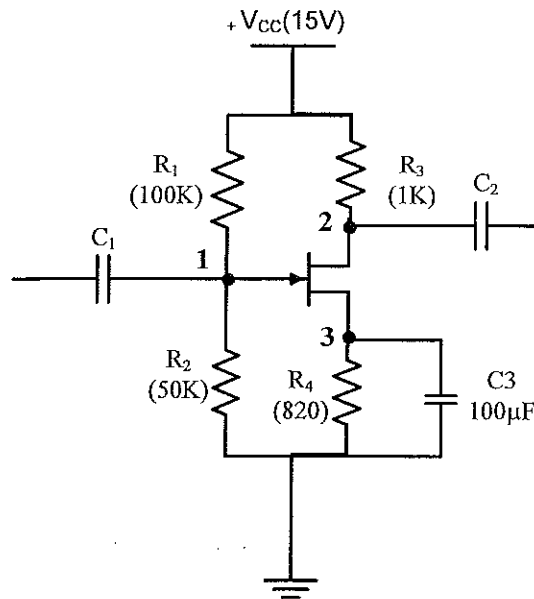


Figure 1

- a. Calculate,
 - i. Gate voltage [02 Marks]
 - ii. Drain current [02 Marks]
 - iii. Gate source voltage [02 Marks]
- b. Calculate the test point voltages at no signal. [08 Marks]
- c. Find the type of the fault with the faulty component/s in each case giving reason. [06 Marks]

Case	T.P 1(V)	T.P 2(V)	T.P 3(V)	Output
A	5	7.91	5.81	Low gain
B	5	15	0	No output
C	5	7.91	5.81	No output

2. A transistor amplifier is shown in figure 2.

The drain current of the transistor Tr1 is given by $I_D = 0.3(V_{GS} - V_P)^2$, where I_D is in mA, V_{GS} is in volts and $V_P = -4\text{V}$. You may assume usual notation. The current gain of the transistor Tr2 can be considered as high.

- a. Calculate the current I_P and then find out the voltages at the test points when no signal is applied. **Do not assume** maximum swing at the output. [08 Marks]
- b. Find out the amplitude of the input signal that will produce an output amplitude of 1V at 1 kHz. What is the phase relationship between the input and the output? [04 Marks]

 


Figure 2

c. The test point voltages under fault conditions are shown in the following table. Identify the faulty component/s and fault type with reasons. [08 Marks]

Case	1	2	3	4	5	Output response
A	0	11.40	6.000	0.270	0.261	No output
B	0	11.40	11.80	3.139	0.201	Output clipped
C	0	11.40	0.012	3.077	0.197	No output
D	0	12.00	0	0	0	No output

3.

- a. Draw a block diagram of an oscillator circuit. You should clearly show all the sub modules in your answer. [04 Marks]
- b. The circuit of a Wien bridge oscillator producing sine wave output is shown in figure 3. All transistors are high gain, and RT is a thermistor.
 - i. Identify the components, which determines the output frequency. [01 Marks]
 - ii. What is the phase relationship of the signal at test point 5, with the signal at the base of Tr1? Also state the function of RT. [02 Marks]
 - iii. Estimate the frequency range of this oscillator. [02 Mark]
 - iv. Calculate the DC voltages at test points. [03 Marks]

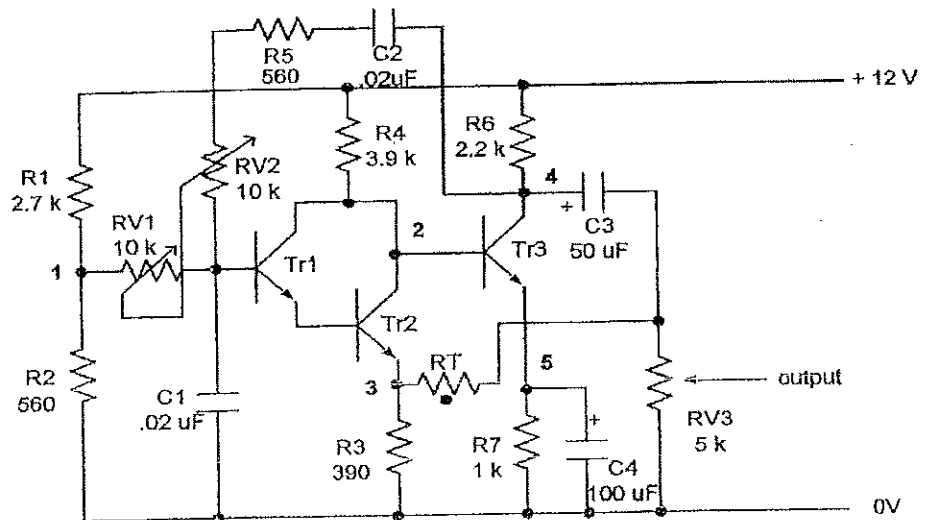


Figure 3


- v. Following table shows the DC voltages at test points, under faulty conditions. Identify the faulty components indicating the relevant reasons. [08 Marks]

Fault	1	2	3	4	5	output
A	1.9	0	9.5	8.9	9.0	No output
B	1.9	0.7	6.7	6.5	15.0	No output
C	0	0	9.5	8.9	9.0	No output
D	1.9	0.7	6.6	6.0	10.9	Square wave


4. A Schmitt trigger circuit, used in a signal processing system is shown in figure 4 (a).

- Calculate the input threshold voltages of this circuit. Find the test point voltages when the input is given 4V and 1V respectively. [06 Marks]
- What is the hysteresis of this circuit? [02 Marks]
- The shown in figure 4 (b) is given as an input to the circuit. Sketch the output waveform, clearly showing voltage and time values. [04 Marks]
- Under fault conditions, this circuit is tested with a multi-meter and the voltages observed on the test points are given below. Identify the faulty component/s giving fault type, with reasons. [08 marks]

Case	input	TP1	TP2	TP3	TP4
A	0.00	12.00	0.00	0.00	12.00
B	0.00	7.96	0.23	0.83	12.00
C	4.00	8.52	1.80	2.40	3.33
D	4.00	3.60	3.40	3.60	12.00

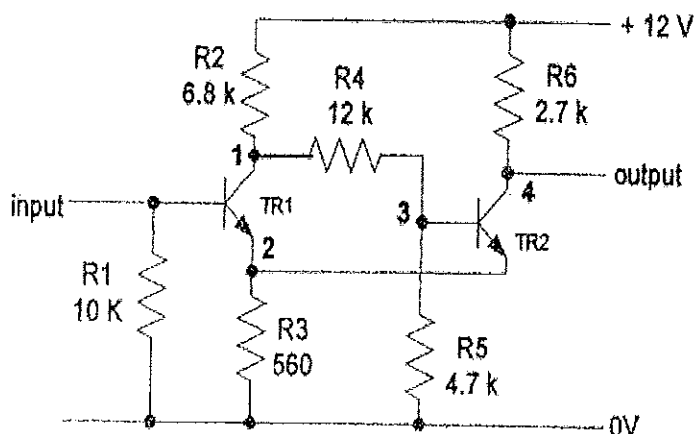

(a)

 

(b)

Figure 4

5. Consider the DC voltage regulator circuit shown in Figure 5.

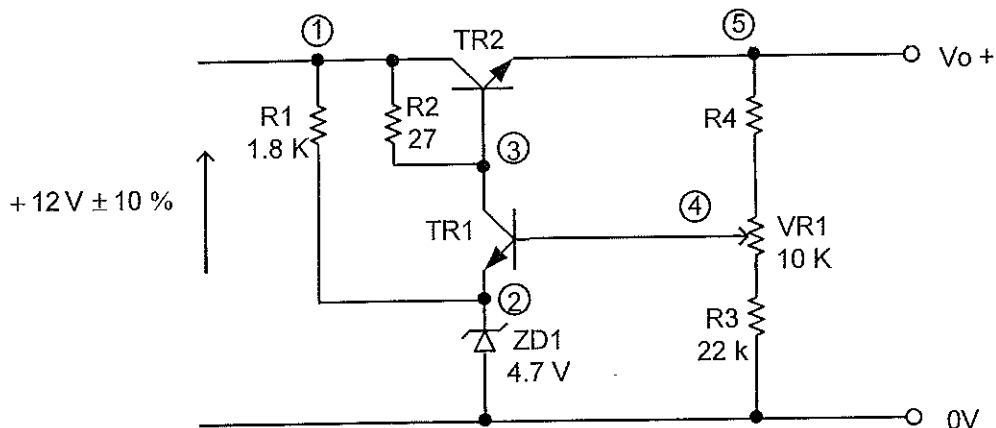


Figure 5

Assume that the current gain of Tr2 and V_{CE} (min) is 30 and 1V respectively. The transistor Tr1 is of high gain type.

- (i) Find a suitable value for R4 to obtain maximum guaranteed output voltage and calculate it for this value of R4. [04 Marks]
- (ii) Find the minimum output voltage. [01 Mark]
- (iii) Calculate the guaranteed maximum load current. [02 Marks]
- (iv) Calculate the maximum power dissipation in Tr2, R2 and ZD1. [03 Marks]
- (v) Show the implementation of an active current limit circuit for this power supply and find the component values for the worst case of a maximum load current. [02 Marks]
- (vi) Following table shows the test point voltages under fault conditions. Determine the faulty component/s with fault type giving reasons. Assume VR1 is set for the maximum output voltage. [08 Marks]

Case	1	2	3	4	5	Output
A	12.00	4.700	11.82	6.140	11.22	No regulation
B	12.00	4.700	10.28	5.300	9.680	Max. load current = 0.9A
C	12.00	4.700	5.900	5.300	5.300	No regulation
D	12.00	4.700	12.00	0	0	No output

6. Consider the circuit shown in figure 6.

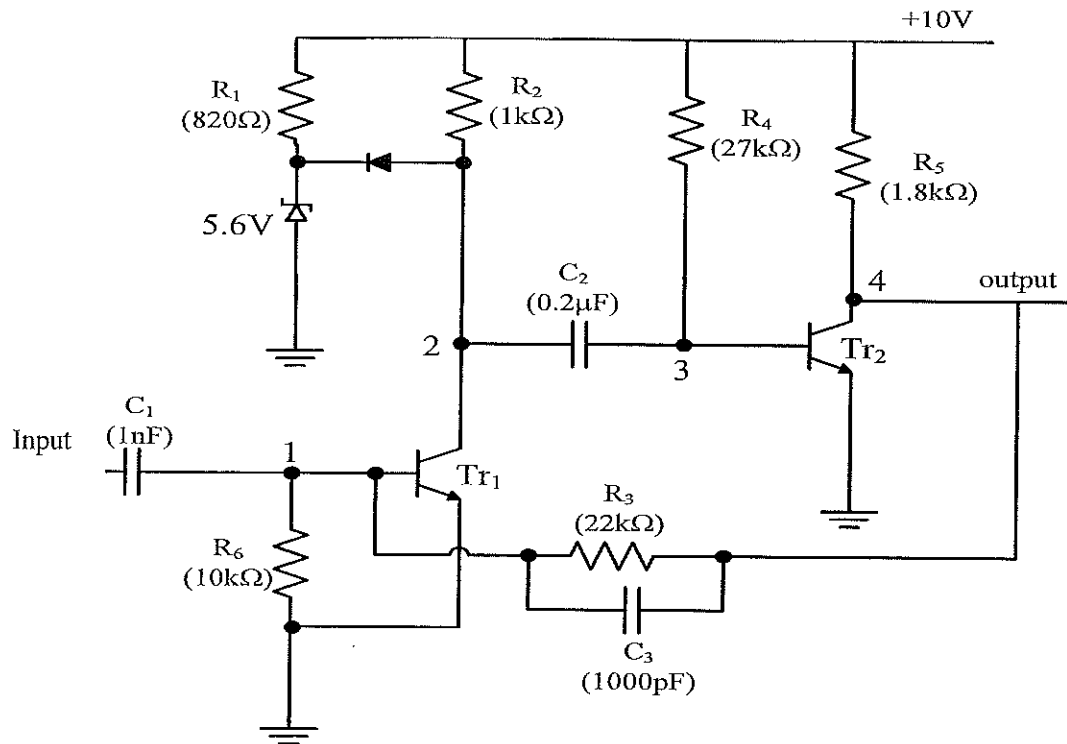


Figure 6

A narrow width pulse train of 250 Hz frequency and +2V height is applied to the input.

- Draw the waveforms at each test point to a common scale with the input. [04 Marks]
- Calculate the parameters of the output waveform. [04 Marks]
- Calculate the voltages at test points, when no signal is applied. [04 Marks]
- The output is not available under the following fault conditions. State which component is faulty with fault type giving reasons. [08 Marks]

Case	TP1	TP2	TP3	TP4
P	0.2	6.2	0.7	0.2
Q	0.6	0.2	0.7	10
R	0.2	0.6	0.7	0.2
S	0.2	0	0.7	0.2

7. Consider the amplifier, shown in figure 7. The transistors Q1, Q2 and Q3 are of high gain type, while the current gain of Q4 is 50.

- Calculate I_x and the test point voltages at no signal. Do not assume any voltage for a test point. [08 Marks]

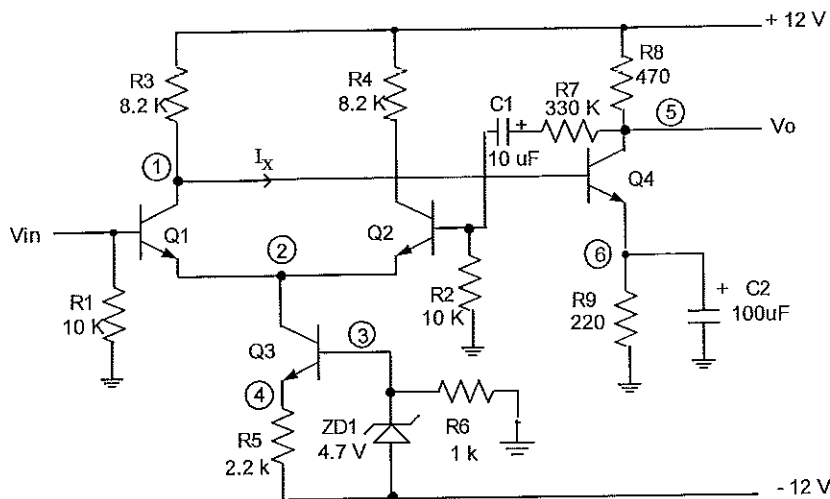


Figure 7

- b. A sine wave signal of 1 kHz with 145mV amplitude is applied to the input. Sketch the output signal with the input to a common time scale. Mark the time and voltage values, where necessary. [04 Marks]
- c. Following table shows the test point voltages under faulty conditions. Identify the faulty component/s with fault type, giving reasons. [08 Marks]

Case	1	2	3	4	5	6
A	4.56	0	-7.30	-12.0	4.00	3.96
B	0.50	-0.60	-7.30	-7.90	12.0	0
C	0.70	-0.60	-7.30	-7.90	12.0	0.10
D	0.70	-0.60	-7.30	-7.90	0	0.10

- 8. (a) State the use and limitations of a logic probe. [02 Marks]
- (b) Consider the digital circuit shown in figure 8.

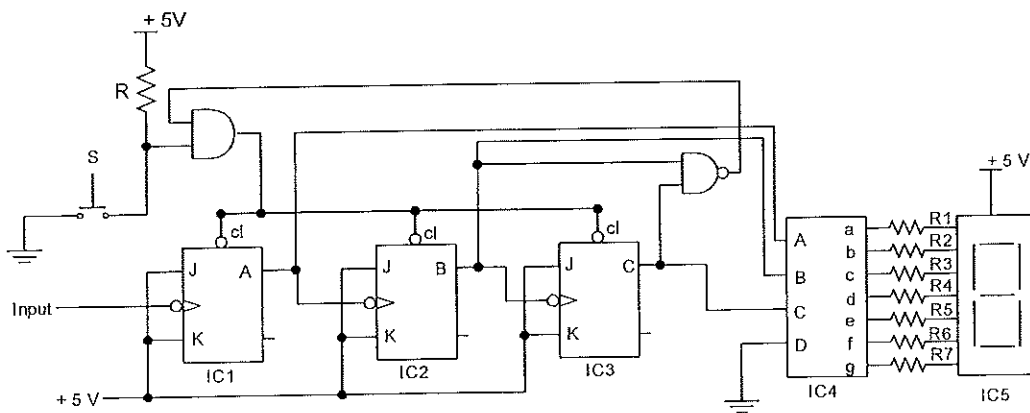


Figure 8

- (i) Show the operation of the components IC1, IC4 and IC5, with the aid of tables, using inputs and outputs. [04 Marks]
- (ii) After 'S' is pressed, positive pulses of 5V are given to the input. Tabulate the binary states of A, B, C, D and the output of IC5 with each clock pulse. [02 Marks]
- (iii) State the faulty component/s for the following fault cases, giving fault type with reasons. [06 Marks]

Case	output of IC5
A	2, 3, 2, 3, 2, 3,
B	4, 5, 4, 5, 4, 5,
C	0, 1, 2, 3, 4, 5, 6, 7, 0, 1, 2,

- (iv) In a fault case, a logic probe blinks at A, B and C while the output of IC5 is always '3'. State how the logic probe can be used further to determine the exact faulty component. [04 Marks]
- (v) If the resistor R is open, explain the operation of the circuit. [02 Marks]

-END-