

The Open University of Sri Lanka
Faculty of Engineering Technology
Department of Electrical & Computer Engineering



Study Programme	: Bachelor of Science Honours in Engineering
Name of the Examination	: Final Examination
Course Code and Title	: EEX4331 Circuit Theory and Design
Academic Year	: 2022/2023
Date	: 13 th February 2024
Time	: 13:30 – 16:30hrs
Duration	: 3 hours

General Instructions

1. Read all instructions carefully before answering the questions.
 2. This question paper consists of **Six (6)** questions in **Four (4)** pages.
 3. Answer any **Five (5)** questions. All questions carry equal marks.
 4. Answer for each question should commence from a new page.
 5. This is a Closed Book Test (CBT).
 6. Answers should be in clear handwriting.
 7. Do not use Red colour pen.
-

Question 01 – Answer both part A and B.

Part A

Consider the circuit shown in Figure Q1.1

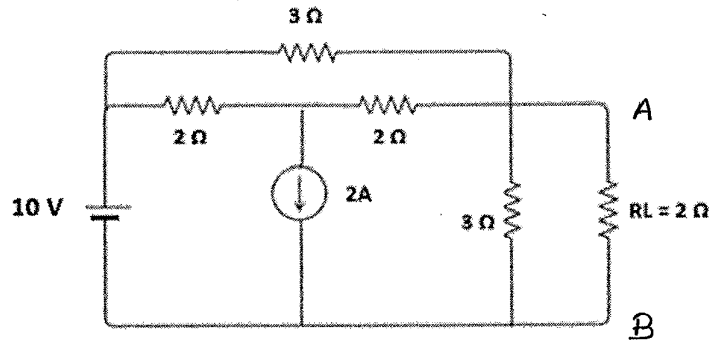


Figure Q1.1

- I. Calculate the Thevenin's equivalent voltage and impedance at points A and B of the circuit shown in figure Q1.1 (03 marks)
- II. Using the calculations made in part I, draw the Thevenin's equivalent circuit of the network. (02 marks)
- III. Calculate the value of R_L to deliver the maximum power. (02 marks)
- IV. Hence or otherwise find the maximum power delivered to R_L . (03 marks)

Part B

Consider the circuit shown in Figure Q1.2

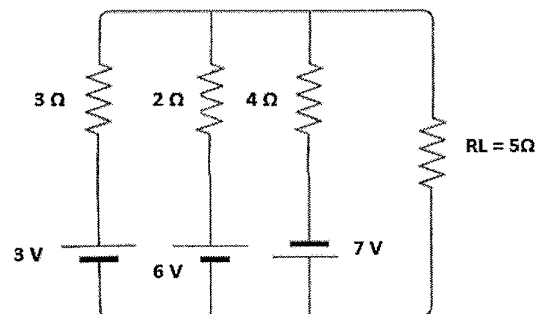


Figure Q1.2

- I. Use Millman's theorem to determine the current through the resistor R_L . Include a sketch of the simplified circuit in your answer. (10 marks)

Question 02

The RL circuit shown in figure Q2 is excited with a square wave $[v_s(t)]$ voltage signal

- $v_s(t) = \frac{12}{\pi} \sum_{n=1}^{\infty} (-1)^{n+1} \frac{1}{(2n-1)} \cos(2n-1)\pi t$
- $L1 = \frac{2}{\pi} \text{ H}, R1 = 4\Omega$

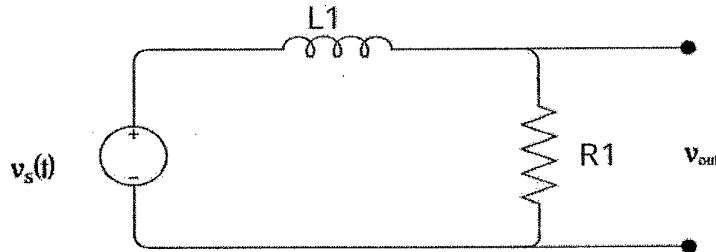


Figure Q2

- Express the periodic excitation (input) in terms of Fourier expansion for the first three frequency components. ($n=1,2,3$) (05 marks)
- Write an expression to the output of the circuit (V_{out}) in the complex frequency domain (s-domain). (05 marks)
- Using the results of part II, derive an expression for V_{out} in the time domain. (10 marks)

Question 03

Consider the RLC circuit shown in Figure Q3. At $t = 0$ the switch is closed.

- $E1 = 10 \text{ V}, L1 = 4 \text{ H}, R1 = 8 \Omega, C1 = 0.125 \text{ F}$

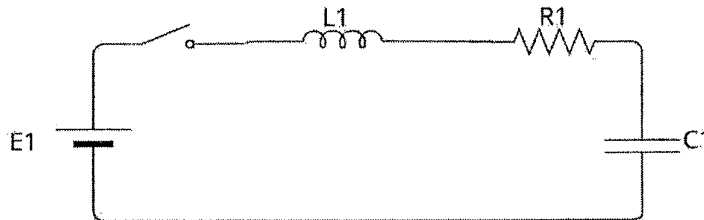


Figure Q3

- Write a differential equation relating voltages across each element using Kirchhoff's voltage law. Assume the capacitor is initially fully discharged and the inductor does not contain any stored magnetic energy. (04 marks)
- Solving the differential equation, you have written in 'I', obtain an expression to the current through the circuit for $t > 0$. (10 marks)
- Sketch the variation of current in the circuit against time. (Start from $t = 0$) (04 marks)
- State the type of the response of this circuit. (02 marks)

Question 04

- I. Realize the following LC impedance function using Foster 1st and 2nd forms.

(14 marks)

$$Z(s) = \frac{3(s^2 + 1)(s^2 + 16)}{s(s^2 + 9)}$$

- II. Realize the following LC impedance function using Cauer 1st form.

(06 marks)

$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$$

Question 05

Part A

Figure Q5.1 shows a T-Network.

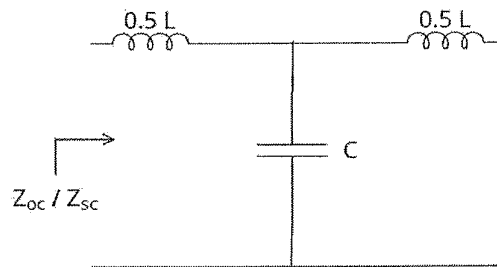


Figure Q5.1

- I. Calculate the Z_{oc} (Open circuit impedance) and the Z_{sc} (Short circuit impedance) of the above T network. (04 marks)
- II. If the two inductor values are equal to 6 H and the capacitor value is equal to 1.5 μ F, find the type of filter and the cutoff frequency of it.

(Hint: Refer to the chart and table given in figure Q5.2 and Table Q5) (06 marks)

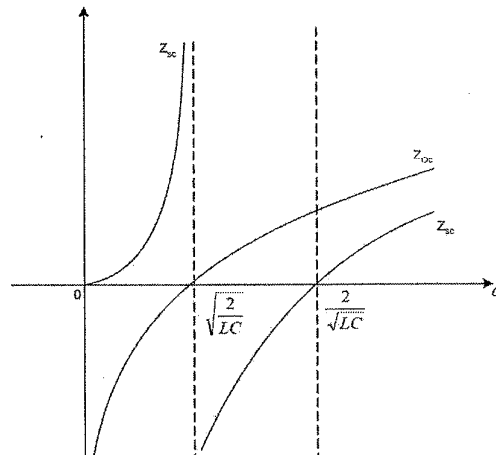


Figure Q5.2

X_{oc}	X_{sc}	Z_o	$\tanh \gamma$	Band	α
>0	>0	Imag.	real	stop	$\neq 0$
>0	<0	real	Imag.	pass	$=0$
<0	>0	real	Imag.	pass	$=0$
<0	<0	Imag.	real	stop	$\neq 0$

Table Q5

Part B

- I. State one key advantage in Butterworth filter (02 marks)
- II. The magnitude function of a certain filter needs to be determined using Butterworth approximation. Specifications of the filter are as follows,
 - Pass Band = 0 to 5 MHz
 - Pass Band tolerance = 0.25 dB
 - High frequency attenuation(minimum) 20 dB at 7.5 MHz
 - Attenuation, $A_{db} = 10\log_{10}(1+\epsilon^2 X^{2n})$

Find the magnitude function of the above filter. (08 marks)

Question 06

- I. Write the terminal characteristic equations of a general two port network in matrix form using, (04 marks)
 - a. Open circuit impedance (Z) parameters.
 - b. ABCD Transmission parameters.
- II. Determine the ABCD parameters of the circuit shown in figure Q6. (08 marks)

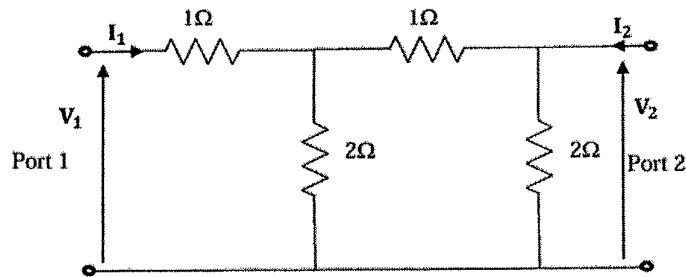


Figure Q6

- III. Is the network shown in figure Q6 reciprocal? Justify your answer using the results obtained in part II. (04 marks)
- IV. Calculate the image impedance at port 1 and port 2. (04 marks)

-End of Paper-